

(3 Hours)

[Total Marks: 80]

- N.B.: (1) Question No. 1 is compulsory.  
(2) Solve any **three** questions out of remaining **five**.  
(3) Figures to **right** indicate **full** marks.  
(4) Assume suitable **data** where **necessary**.

- Q1. Solve any four 20  
a) State ideal and Practical Characteristics of an Op-amp  
b) Explain Multiplexer and Demultiplexer.  
c) Convert following decimal number to Binary ,Octal, Hexadecimal and Gray code  
i)  $(128)_{10}$  ii)  $(73)_{10}$   
d) Explain working of LCD.  
e) Covert D flip flop to S-R flip flop.
- Q2. a) a) Implement following using only one 8:1 Multiplexer and few gates. 10  
 $F(A,B,C,D) = \sum m(0,1,3,4,5,8,9,10,12,15)$   
b) Explain Fixed Biasing Circuit with its stability factor. 10
- Q3. a) Draw and Explain Instrumentation Amplifier using Op-amp. 10  
b) Draw circuit diagram and explain the operation of Monostable Multivibrator using IC555. 10
- Q4. a) Minimize the following four variable logic function using K-map and design 10  
by using basic gates  
 $f(A,B,C,D) = \sum m(0,1,2,3,4,7,8,9,11,15)$   
b) What are the different methods used to improve CMRR in Differential Amplifier.  
Explain one in brief. 10
- Q5. a) Design a Mod 12 asynchronous counter using J-K-flip flop 10  
b) Design 4-bit binary to gray code conversion 10
- Q6 Write short notes on any four 20  
a) Explain the working of a Non-inverting amplifier using Op-amp  
b) Explain working of a transistor.  
c) Write VHDL program for NAND gate.  
d) Explain working of Current Mirror Circuit.  
e) Explain block diagram of op-amp.

\*\*\*\*\*