

SE Sem. III | I.T.  
(CBSGS)

Analog & digital  
circuits. 01/06/15

**Q.P. Code : 4929**

**(3 Hours)**

**[Total Marks : 80**

- N.B. (1) Q.No.1 is compulsory  
(2) Attempt any three out of remaining questions.  
(3) Assume suitable data wherever required but justify them.  
(4) Draw appropriate waveforms wherever required.

- Q.1. (a) Convert D Flip-Flop to T Flip-Flop. (04)  
(b) Draw the Truth Table and excitation Table for S-R Flip-Flop. (04)  
(c) Explain the working of LCD. (04)  
(d) Convert the following octal numbers to binary, decimal and hexadecimal number.  
(i)  $(6673)_8$  (ii)  $(7466)_8$  (04)  
(e) Compare BJT with JFET. (04)
- Q.2. (a) Draw the Truth Table for Full adder and realize using 3:8 Decoder (10)  
(b) Explain the working of Astable Multivibrator using IC- 555. (10)
- Q.3. (a) Explain in brief different biasing circuits for BJT (10)  
(b) Design a Modulo 5 ripple up counter and draw the waveforms for the same. (10)
- Q.4. (a) Realize the following expression using only one 8:1 MUX and few Logic gates.  
$$F(A,B,C,D) = \sum m(0, 3, 6, 8, 11, 13, 15)$$
 (10)  
(b) Explain Differential amplifier and elaborate any one method to improve CMRR. (10)
- Q.5. (a) Design a synchronous counter which goes through following states using J-K Flip-Flop.  
0-2-4-6-0 (10)  
(b) Write a note on Shift Register. (10)
- Q.6. Write short notes on the following. (20)  
(a) Universal Gates  
(b) 4-bit Binary to gray code converter  
(c) Inverting and Non-inverting operational amplifier.