

Analog and Digital
Circuits.

QP Code : 30720

(3 Hours)

[Total Marks : 80]

- N.B. :** (1) Question No.1 is compulsory.
 (2) Attempt any three out of remaining questions.
 (3) Assume suitable data wherever required.
 (4) Draw appropriate waveforms wherever required.

1. Solve any five :

- | | |
|--|----|
| (a) CE configuration is popular in amplifier circuits. Justify. | 4 |
| (b) Explain the working of zener diode as voltage regulator. | 4 |
| (c) State ideal and practical characteristics of Op-amp. | 4 |
| (d) Add $(83)_{10}$ and $(34)_{10}$ in BCD. | 4 |
| (e) Convert S-R flip-flop to D flip-flop. | 4 |
| (f) Explain parallel i/p, serial o/p shift register. | 4 |
| 2. (a) Explain in brief different biasing circuits of BJT. | 10 |
| (b) Explain how Op-amp can be used as summing, scaling and averaging amplifier in inverting configuration. | 10 |
| 3. (a) Design and implement one digit BCD adder using IC-7843. | 10 |
| (b) Implement the following logic function using 4:1 mux
$f(A, B, C) = \pi M(0, 1, 3, 5, 7)$. | 5 |
| (c) Explain the working of LCD. | 5 |
| 4. (a) Design a 2-bit comparator using minimum number of gates. | 10 |
| (b) Explain the working of Astable multivibrator using IC-555. | 10 |
| 5. (a) Design a synchronous counter which goes through following states using JK flip-flop,
0 - 2 - 4 - 6 - 0 | 10 |
| (b) With the help of neat diagram, explain the functioning of a 4-bit bidirectional shift register. | 10 |

TURN OVER

FW-Con. 11494-16.

6. Write short notes on the following :

- (a) VHDL program format
- (b) Universal gates. Implement EX-OR gate using NAND gate
- (c) Integrator using Op-amp
- (d) Current mirror circuit
