

(3 Hours)

[Total Marks: 80]

- N.B.: (1) Question No. 1 is **compulsory**.
 (2) Solve any **three** questions out of remaining **five**.
 (3) Figures to **right** indicate **full** marks.
 (4) Assume suitable **data** where **necessary**.

Q1. Solve

- a) i) Convert $(13.078125)_{10}$ to binary.
 ii) Convert $(B73D)_H$ into octal.
 iii) Convert $(436)_8$ into hexadecimal.
 iv) Convert $(845)_{10}$ into gray code. (4)
- b) Sketch typical illumination characteristics for a photodiode and explain the theory of device. (4)
- c) Derive the equation of stability factor for voltage divider bias circuit. (4)
- d) Implement a full adder using 8:1 Demultiplexer. (4)
- e) Write truth table and excitation table of JK flip flop. (4)
2. a) Explain inverting summing amplifier using op-amp. Derive the expression for output voltage. (8)
- b) What are different methods used to improve CMRR in differential amplifier. (8)
- c) Draw circuit diagram & waveforms of monostable multivibrator using IC555. (4)
3. a) Design 2 bit magnitude comparator. (10)
- b) Using K-map realize the following expression
 $Y = \sum m(1, 3, 4, 5, 7, 9, 11, 13, 15)$ (5)
- (c) Convert JK FF to D FF. (5)
- 4.a) With the help of neat circuit diagram explain the operation of Zener diode regulator for variable input voltage and variable load. (8)
- b) Explain dataflow modeling style with suitable example. (6)
- c) Compare schottky diode with PN junction diode (3 points) (6)
5. (a) Design a MOD-12 Asynchronous down counter. (8)
- (b) What do you mean by operational amplifier? Explain the block diagram of opamp. (8)
- (c) Write VHDL for full adder. (4)
- 6.(a) Write a short note on ASCII code and Excess-3 code. (8)
- (b) What do you mean by universal gate? Implement NOT,AND,OR gates using NAND gates only. (8)
- (c) Explain the difference between the integrator & differentiator .Give one application of each. (4)
