

( 3 Hours )

( Total Marks : 80 )

Please check whether you have the right question paper.

- N.B.:
- 1) Questions No. 1 is compulsory.
  - 2) Solve any three question out of remaining five questions.
  - 3) Assume suitable data if necessary.
  - 4) Figures to the right indicate full marks.



- 1 Solve any four out of five : (20)
  - a) Explain Input and Output characteristics of CE configuration of BJT.
  - b) Convert following decimal number to Binary, Octal, Hexadecimal and Gray code  $(154)_{10}$ .
  - c) Design EX-OR gate using only NOR gates.
  - d) Draw two truth tables illustrating the outputs of a full-adder, one table for the sum output
  - e) Convert S – R flip-flop to D flip-flop.
  
2. a) Implement following using only one 8: 1 Multiplexer and few gates : (10)  
 $f(A, B, C, D) = \sum m(1, 2, 3, 5, 6, 9, 10, 11, 14)$
- b) Using Quine McCluskey Method determine Minimal SOP form for (10)  
 $f(A, B, C, D) = \sum m(1, 3, 5, 6, 8, 9, 12, 14, 15) + \sum d(4, 10, 13)$
  
3. a) Explain Collector to base bias Circuit with its stability factor. (10)
- b) With neat diagram explain operation of ALU IC74181. (10)
  
4. a) Design a Mod 10 synchronous counter using S-R Flip-flop. (10)
- b) Minimize the following four variable logic function using K-map : (10)  
 $f(A, B, C, D) = \sum m(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15)$  and design using only NAND gates.
  
5. a) Simplify following equation using Boolean algebra and Design using basic gates (10)  
 $f(A, B, C) = A'B + BC' + BC + AB'C'$ .
- b) Explain Entity in VHDL and Write VHDL program for half subtractor circuit. (10)
  
6. Solve the following (Any Four) : (20)
  - a) Explain working of Universal Shift Register.
  - b) Working of T flip flop.
  - c) Explain working of Differential Amplifier.
  - d) Write VHDL program for EX-NOR gate.
  - e) Explain working of Encoder and Decoder.