

Q. P. Code : 723803

(3 Hours)

Max marks 80

N.B. : 1) Question no. 1 is compulsory

2) Attempt any three questions out of the remaining five

3) Assume suitable data wherever necessary, with proper justification

1. Solve any four (All subparts carry 5 marks each)
 - a) Explain resolution, accuracy and settling time with respect to DAC
 - b) State the important ideal characteristics of an op-amp, compare it with the values of IC 741 op-amp.
 - c) Explain Barkhausen criterion.
 - d) Explain Schmitt trigger. Draw its VTC.
 - e) What do you understand by Input Bias current of an op-amp, How it can be measured practically. What should be its ideal value.

2.
 - a) Design a 15KHz generator with IC 555 using 47 μ F capacitor for a 60% duty cycle. Draw the waveforms 10
 - b) Draw and explain OPAMP based square wave and triangular wavegenerator. How is duty cycle modulation achieved? 10

3.
 - a) Explain in detail R-2R ladder DAC. 10
 - b) Explain narrow band, band pass RLC filter with circuit diagram and derive its transfer function. Also find expression for its Q factor and cutoff frequency.

4.
 - a) Explain RC phase shift oscillator and derive the relation for its frequency of oscillation. 10
 - b) What are different possible IC 723 based voltage regulator. Design voltage Regulator to give $V_o = 9V$ at 600 mA using IC 723. . Draw the circuit diagram of the designed circuit. 10

5.
 - a) Explain OPAMP based sample and hold circuit. 5
 - b) Explain current to voltage converter. 5
 - c) Design an infinite gain high pass filter having cutoff frequency of 2KHz. Draw the circuit diagram of the designed circuit. 10

6.
 - a) Explain 3 OPAMP Instrumentation amplifier. List its features and applications. 10
 - b) Write short notes on
 - (i) PLL and its application 5
 - (ii) VCO and its features 5