

(3 hours)

Total Marks: 80

- N.B:
- (1) Question No. 1 is compulsory.
 - (2) Solve any three questions from remaining five questions.
 - (3) Draw neat diagrams and assume suitable data wherever necessary. Justify your assumptions.

- Q 1 (a) Explain the characteristics of an ideal operational amplifier. (5 marks)
- (b) State difference between inverting and non-inverting amplifiers. (5 marks)
- (c) What are the different methods for A-D and D-A conversion? Explain any one for each. (5 marks)
- (d) What is Schmitt trigger? (5 marks)
- Q-2 (a) Write a short note on (10 marks)
- i) Wave generator XR 2206
 - ii) Power amplifier LM380
- (b) Explain Binary Weighted register DAC. (10 marks)
- Q-3 Write a short note on the following (5 marks)
- (a) Square wave generator
 - (b) Logarithmic and antilog converters (5 marks)
 - (c) Window and level detector (5 marks)
 - (d) LM337 voltage regulator (5 marks)
- Q 4 (a) Compare Successive Approximation ADC with Dual slope ADC (10 marks)
- (b) i) Describe the working of Wein bridge Oscillator (10 marks)
- ii) Explain the application of op-amp as a subtractor and integrator.
- Q-5 (a) How are filters classified? Explain a second order infinite gain band pass filter and derive the relation of its cut off frequency. (10 marks)
- (b) Design a Second order KRC low pass filter with cut off frequency $f_0 = 1\text{KHz}$ & $Q=5$ (10 marks)
- Q 6 (a) Explain 3 op-amp instrumentation amplifier in detail (10 marks)
- (b) Design a 15KHz generator with IC555 using $47\mu\text{F}$ capacitor for a 60% duty cycle. Draw the waveforms. (10 marks)