

Lib
04

Q.P. Code :18507

[Time: Three Hours]

[Marks:100]

Please check whether you have got the right question paper.

- N.B:
1. Question.No.1 is compulsory.
 2. Attempt any three questions from the remaining five.
 3. Assume suitable data wherever necessary.

- Q.1
- a) Explain the need of dual power supply in OP-AMP. 04
 - b) What is the difference between normal rectifier and precision rectifier? Explain half wave precision rectifier. 04
 - c) Compare IC 78XX with IC 723. 04
 - d) State various methods to achieve analog to digital conversion. 04
 - e) Implement $v_o = 3v_a - 5v_b - 6v_c$ 04
- Q.2
- a) Design a 2nd order KRC low pass filter with a cutoff frequency $f_o = 1$ KHz and $Q = 5$. 10
 - b) Derive the output frequency relation for RC phase shift oscillator. 10
- Q.3
- a) Explain R/2R ladder DAC. 10
 - b) Design voltage regulator using IC 723 for $V_o = 10V$ and $I_L = 200$ mA. 10
- Q.4
- a) Explain monostable multivibrator using IC 555. Hence design it for a output delay of 10 ms. 10
 - b) Explain PLL and VCO. What are their applications? 10
- Q.5
- a) Explain triangular wave generator using OPAMP. 10
 - b) How are filters classified? Explain a second order infinite gain band pass filter and derive the relation of its cut off frequency. 10
- Q.6
- a) Explain IC 723 with the help of its functional block diagram. What are the different modes in which a voltage regulator using IC 723 can be designed? 10
 - b) Explain 3 OPAMP instrumentation amplifier. List its applications. 10