

[3 Hours]

[Marks: 80]

Please check whether you have got the right question paper.

- N.B:
1. Question No. 1 is compulsory.
 2. Solve any three questions out of remaining three questions.
 3. Figures to the right indicate full marks.

1. (a) Draw and explain V-I characteristics of SCR. **05**
(b) Draw and explain equivalent circuit of an OP-AMP. **05**
(c) State and prove Demorgan's Theorems. **05**
(d) Enlist all important features of logic family circuit. **05**
2. (a) Draw and explain slip-torque characteristics of AC motor. **07**
(b) What is GTO? Explain switching characteristics of GTO. **07**
(c) Compare DIAC and TRIAC. **06**
3. (a) Draw and explain full controlled rectifier with R load. Draw waveforms. **07**
(b) Explain with neat diagram MSP 430 architecture. **07**
(c) Draw and explain second order low pass filter. **06**
4. (a) Draw circuit diagram and waveforms of single phase full bridge inverter with R load. **07**
(b) Compare CMOS logic family with TTL logic family. **07**
(c) What is servo speed? Explain working principle of servo motor. **06**
5. (a) Derive the relation per voltage gain in inverting mode in operational amplifier and compare it with non inverting mode. **07**
(b) Draw and explain R triggering method of SCR. **07**
(c) Draw and explain astable mode of operation of IC 555. **06**
6. (a) Explain the application of piezo-electric activator drive. **07**
(b) Compare DC series motor and DC shunt motor. **07**
(c) Explain different applications of microcontroller. **06**