

20

Q. P. Code : 25080

Instructions:

Total Time: **3 Hrs**

Total Marks: **80**

1. Question No: **1** is **compulsory**.
2. Answer any **three** from the **remaining five** questions.
3. Figures to the right indicate full marks.

- 1 Solve **any four**:- (20)
- a) Draw application circuit of triac-diac and associated waveforms.
 - b) Enlist applications of inverter?
 - c) Draw buffer, integrator and Schmitt trigger circuit.
 - d) Define and describe logic operation, power dissipation and propagation delay in digital circuits.
 - e) Draw and explain generic microcontroller.
- 2
- a) Describe speed torque characteristics of dc and ac motors. (07)
 - b) Explain three phase inverter operation with waveforms. (07)
 - c) Describe in detail instrumentation amplifier. State its need and applications. (06)
- 3
- a) Explain an ac to dc converter supplying resistive load. Derive equation for calculating dc voltage. (07)
 - b) Explain procedure to select a motor for an application and describe with the speed torque characteristics. (07)
 - c) Explain in detail low pass active filter (06)
- 4
- a) Explain need of digital to analogue conversion. How the ADC in MSP430 works? (07)
 - b) Compare analogue and digital circuits. Enlist some of them. (07)
 - c) Describe closed loop speed control of DC motor. (06)
- 5
- a) Draw and explain architecture MSP 430 microcontroller? (07)
 - b) What is MOSFET? Explain its working. What are similarities between MOSFET and IGBT? (07)
 - c) Explain IC 555 timer as Monostable Multivibrator. (06)
- 6
- a) Explain with circuit diagram any forced commutation method of SCR. (07)
 - b) Compare microprocessor and microcontroller. (07)
 - c) Explain Demultiplexer and Decoder. (06)