



Time: 3 Hours

Marks: 80

◀ Please check whether you have got the right question paper.

- N.B. :**
1. Q.No.1 is compulsory.
 2. Answer any three out of remaining questions.

1. Attempt any four of the following:

20M

- a) What is an operational amplifier? Write the characteristics of an ideal Op-Amp.
 - b) Explain the working of dc motor and derive the condition for back emf.
 - c) Why single phase induction motor is not self-starting. How it is self-started?
 - d) Convert the following
 - i) 1001.0010 binary number to decimal equivalent.
 - ii) 7777 hexadecimal to its decimal equivalent.
 - e) Draw the v-i characteristics of SCR and TRIAC.
-
2. a) Explain the speed control of dc motor with necessary equation and diagram. **10M**
b) Define starter. Explain 3 point starter with neat diagram. **10M**
 3. a) Explain the working of 3phase induction motor with neat diagram. **10M**
b) Explain the principle of operation as well as working of stepper motor with neat diagram **10M**
 4. a) Define efficiency and voltage regulation of transformer. **10M**
b) What is multiplexer and de multiplexer. Design 8:1 MUX and 1:4 D-MUX. **10M**
 5. a) Explain the working of phase shift oscillator with neat diagram. **10M**
b) Explain single phase half – wave circuit with R-L load and freewheeling diode with neat waveform. **10M**
 6. **Write short notes on** **20M**
 - a) Barkhausen criteria
 - b) Circuit breaker and fuse
 - c) Application of stepper motor
 - d) Emf equation of transformer
