

Q.P.Code: 50590

[Time: Three Hours]

[Marks:80]

Please check whether you have got the right question paper.

- N.B:
1. Question no.1 is compulsory.
 2. Solve any three questions from remaining questions.

- Q1 Attempt the following (any4) 20
- a) Explain working principle of transformer
 - b) Draw and explain VI characteristics of SCR
 - c) Explain various ideal characteristics of OPAMP741
 - d) Explain why single phase induction motor is not self starting.
 - e) State and prove Demorgan theorems
- Q2 A) Explain speed control of DC motor with neat diagram using 10
- 1) Field control method
 - 2) Armature control method
- B) Explain construction and working principle of DC motor. 10
- Q3. A) Derive Torque equation for induction motor and explain Torque- speed characteristics 10
- B) Define power system. Explain distribution transformers and its types with neat diagram. 10
- Q4 A) Explain inverting and noninverting amplifier using OPAMP. 10
- B) Explain construction and working of Triac in detail. 10

- Q5 A) Explain Hartley oscillator with neat circuit diagram. Also discuss Barkhausen criteria for sustained Oscillations. 10
- B) Explain Full wave controlled rectifier using SCR with output waveforms and RL load. 10
- Q6 Write note on (any3) 20
- a) Multiplexer and Demultiplexer
 - b) Tuned oscillator
 - c) Circuit breaker
 - d) Efficiency and regulation of transformer
