

(3 Hours)

[Total Marks :80

- N.B. : (1) Question No.1 is compulsory.
 (2) Attempt any three questions from remaining.
 (2) Assume suitable data wherever necessary.

1. (a) Explain monostable multivibrator as a missing pulse detector. 5
 (b) Explain regenerative action of SCR with help of two transistor analogy. 5
 (c) Explain frequency to voltage convertor. 5
 (d) Explain different types of analog switches. 5
2. (a) Draw and Explain functional diagram of IC 555 as Astable multivibrator. Derive the expression for T_{on} , T_{off} , T and Duty cycle. Design for output frequency = 5KHz with duty cycle = 65%. 12
 (b) Draw and Explain Low pass KRC filter along with derivation for Q & F. 8
3. (a) Explain working of voltage control oscillator. 5
 (b) Explain working of optocouplers in detail. 5
 (c) Design a voltage regulator using IC723 for following specifications. Output frequency = 7V and $I_m = 150mA$. 10
4. (a) Explain construction and working of basic stepper motor. 10
 (b) Design a 2nd order High pass Butterworth filter with cutoff frequency of 1.5KHz. Also plot its frequency response. 10
5. (a) Explain UJT as a relaxation Oscillator. 10
 (b) Explain functional block diagram of IC 8038. 6
 (c) Design IC 8038 function generator with 50% duty cycle and output frequency $f_o = 10KHz$. Assume, $V_{cc} = 15V$, Assume the suitable value for R_p & R_{THD} . 4
6. (a) Design Instrumentation Amplifier using AD620 for gain of 1200 and Explain its application. 10
 (b) Draw and Explain Bipolar driver system for stepper motor. 10

