

9/06/17

TE / Sem V / BM / CBSGS / AD CD

Q.P. Code : 564500

(KT) MAY - 2017 (16)

(3 Hours)

[Total Marks : 80]

- N.B.**
- 1) Question No.1 is compulsory.
  - 2) Attempt any 3 questions from remaining.
  - 3) Assume suitable data wherever necessary.

1.
  - a) Explain the working of Power MOSFET, its structure and characteristics. 05
  - b) Draw a neat labelled functional diagram of IC 555 timer. 05
  - c) What is linear voltage regulator and switching regulator? 05
  - d) Explain generalised impedance convertors and state a few applications. 05
  
2.
  - a) Explain low pass KRC filter and derive the equation for Q. 08
  - b) Explain the regenerative action of SCR with the help of two transistor analogy. 04
  - c) Design an Instrumentation Amplifier using AD620 for gain of 800 and list its applications and explain any one in detail. 08
  
3.
  - a) Compare AC and DC motors. Explain different applications of both motors. 06
  - b) Explain IC 723 with its functional diagram. Design a voltage regulator using IC 723 for the following specifications: 10  
 $V_o = 5\text{V}$ ,  $I_o = 10\text{mA}$ ,  $V_{in} = 15 \pm 20\text{V}$ ,  $I_{sc} = 150\text{mA}$  &  $V_{sense} = 0.7\text{V}$ .
  - c) Design a Wide Band Pass filter for  $F_L = 500\text{Hz}$  and  $F_H = 2.5\text{KHz}$ . 04
  
4.
  - a) Design a circuit using IC 555 timer to divide the input frequency by 3. 05
  - b) Draw and explain the functional block diagram of PLL in detail. Explain Lock range, Capture range and pull in time related to PLL along with its applications. 10
  - c) Explain DIAC and TRIAC and explain its characteristics. 05
  
5.
  - a) Explain the construction and working of a stepper motor. 10
  - b) Explain the functional block diagram of IC 8038 and list its applications. Explain any one application in detail. 10
  
6. Write short notes on any four:- 20
  - a) FSK
  - b) UJT relaxation Oscillator.
  - c) Various types of switches.
  - d) VCO.
  - e) Capacitor filters.

\*\*\*\*\*