

Q.P. Code :13160

[Time: Three Hours]

[Marks:80]

Please check whether you have got the right question paper.

- N.B:
1. Question.No.1 is compulsory.
 2. Solve any three questions from remaining.
 3. Assume suitable data if necessary.
 4. Figures to the right indicate marks.

- Q. 1 a) Design a differentiator to differentiate the input signal that varies in frequency from to 10 Hz to 1 k Hz. 05
b) Compare ego crossing detector with Schmitt trigger circuit. 05
c) Explain Resolution, Accuracy and settling time with respect to DAC. 05
d) Explain Inverting mode current amplifier circuit using OPAMP. 05
- Q. 2 a) Define the following 10
i) Slew Rate iv) Outpt offset voltage
ii) CMRR v) PSRR
iii) Input offset voltage
b) Draw neat diagram of Instrumentation amplifier using op-amp and hence derive the equation of output voltage. 10
- Q. 3 a) Explain Waving of R/2R ladder D/A converter. 10
b) Design voltage regulator to give $V_o = 9V$ at 600 mA using IC 723. 10
- Q. 4 a) Explain Astable multibrator using op-amp. 10
b) Design a 2nd order KRC low pass filter with cutoff frequency to =1kHz and Q=5 10
- Q. 5 a) Design Monostable multivibrator using IC 555 to generate output delay of 10 ms. 10
b) Explain Internal diagram of power amplifier LM380. 10
- Q. 6 a) Explain function of each block of PLL. 10
b) Design a triangular wave generator circuit to get the output frequency at 1.5 kHz and $V_{o(p-p)}=7.5$ v using op-amp. 10