

N.B. (1) Question No. 1 is compulsory.

(2) Solve any **three** questions from **remaining** questions.

(3) Assume **suitable** data if **necessary**.

1. Solve any **four** :-

(a) What is the need of Input offset voltage compensation and how it can be achieved. 5

(b) Design RC phase shift oscillator to produce sinusoidal output of 5KHz. 5

(c) Design schmitt strigger circuit to achiev upper and lower threshold voltage as 1.5 volts. 5

(d) Explain Resolution, Accuracy and settling time with respect to DAC. 5

(e) Design a Flasher circuit using IC 555, in which lamp should remain on for 4 sec and off for 2 sec. 5


2. (a) Derive closed loop parameters for Inverting opamp. 10

(b) Design a second order KRC low pass filter with a cut off frequency $f_0 = 2\text{KHz}$ and $Q = 5$. 10

3. (a) Design a triangular wave generator to get the ouput frequency of 1.5 KHz and $V_{o(p-p)} = 7.5\text{V}$ using IC 741. 10

(b) Explain counter type ADC with neat diagram. 10

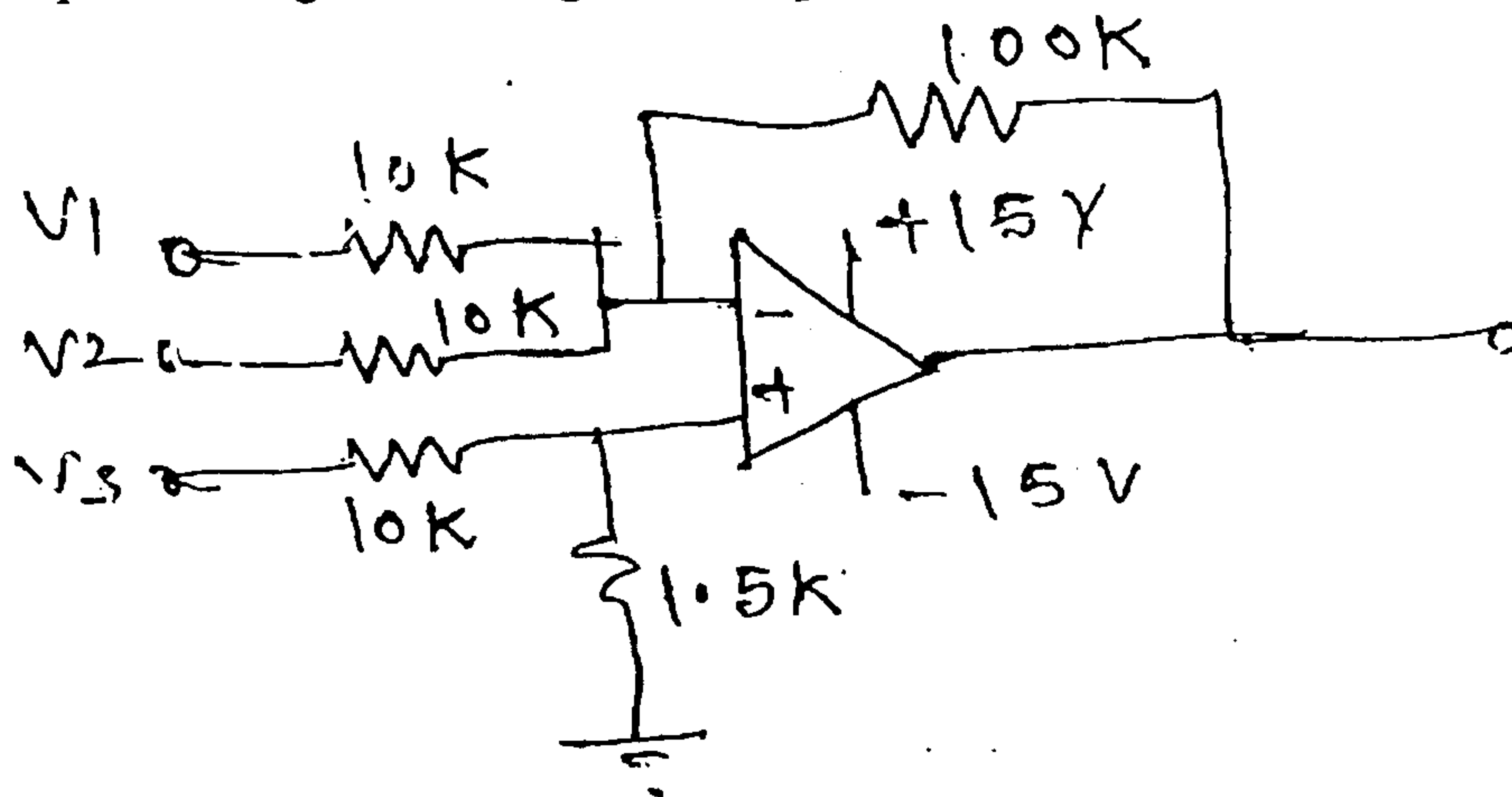4. (a) Calculate output voltage for the given amplifier. 10



$$V_1 = 1.5\text{V}$$

$$V_2 = 3\text{V}$$

$$V_3 = 4\text{V}$$

- (b) (i) Prove that opamp can be used as current to voltage converter. 4
- (ii) Compare normal rectifier with precision rectifier. 3
- (iii) Define different parameters of PLL. 3
5. (a) Explain different comparators, state different applications and suggest 10
modifications for practical comparator.
- (b) What are different possible IC 723 based voltage regulators. Design voltage 10
regulator to achieve $V_o = 12V$ and $I_o = 1$ Amp.
6. (a) Explain function of each block of PLL. 10
- (b) Design voltage Regulator using IC LM317 for the given specifications. 10
 $V_o = 12 \pm 3$ volts and $I_L = 100mA$.
-