

Duration: 3 Hours


Marks:80



- 1] Question no.1 is compulsory
- 2] Attempt any **three** questions out of remaining questions
- 3] Assume **suitable data** if **required**

Q. No. 1) Attempt any four from the following [20]

 - a) Calculate the voltage at the output node  $V_o$  if  $V_{DD}=5V$  and  $V_{th}=1.5V$



- b) Implement 2:1 multiplexer circuit using pass transistor logic and state its drawback. Draw the circuit using CMOS transmission gates.
- c) State the conditions required for the symmetric static CMOS inverter.
- d) Compare ion implantation with diffusion stating its advantages and disadvantages.
- e) In 2-input CMOS NAND gate all PMOS transistors have  $(W/L)_p = 20$  and all NMOS transistors have  $(W/L)_n = 10$ . Draw its equivalent CMOS inverter for simultaneous switching of all inputs and find size of PMOS and NMOS transistor in the equivalent inverter circuit.

Q. No. 2)

- a) A CMOS inverter has following parameters

$$V_{DD} = 3.3V \quad V_{t0,n} = 0.6V \quad V_{t0,p} = -0.7V$$

$$K_n = 200\mu A/V^2 \quad K_p = 80\mu A/V^2$$

Calculate the noise margin of the circuit. Is the inverter symmetric? [10]

- b) Implement  $Y = \overline{A(B+C)} + DE$  [10]

- (i) static CMOS logic
- (ii) Dynamic logic
- (iii) Depletion load logic
- (iv) Pseudo NMOS logic

Q. No. 3)

- a) Explain in detail the fabrication sequence of PMOS transistor with cross sectional view of each step. [10]

Q. P .Code: 36647

- b) Draw schematic and layout diagram of six transistor SRAM cell and explain Read and write operations. [10]

Q. No. 4)

- a) Compare constant field scaling with constant voltage scaling and state advantages and limitations in both the methods. Show the effect of scaling on power density and current density. [10]
- b) Design a 3- bit carry generator block of carry look ahead adder using multiple output domino logic (MODL) style. Explain how it achieves better speed compared to ripple carry adder. [10]

Q. No. 5)

- a) Draw layout diagram of two input CMOS NAND gate using lambda design Rules with  $(L/W)_p=1/2$  and  $(L/W)_n=2/1$ . (Indicate scale in terms of lambda on layout). [10]
- b) Draw transistor level CMOS negative edge triggered master slave D flip flop. [5]
- c) What are the limitations of single phase clock? Explain with neat diagram two phase clock system. [5]

Q. No. 6) Write short notes on any four [20]

- i) ESD protection circuit.
- ii) 4x4 Barrel shifter
- iii) MOSFET Capacitances
- iv) Design rules and their necessity
- v) Clock skew and clock jitter

\*\*\*\*\*