

Q.P. Code : 24936

[Time: Three Hours]

[ Marks:80]

Please check whether you have got the right question paper.

- N.B:
1. Question.No.1 is compulsory.
  2. Attempt any 3 Questions from remaining 5 Questions.
  3. Assume suitable data whenever necessary.

- Q.1** Answer any 04 out of the 05 questions given below: 20
- a) Explain the working of Zero crossing detector with diagram.
  - b) Explain in brief, the concept of loading and method of reducing it.
  - c) Explain in brief, data acquisition system.
  - d) Draw and explain sample and hold circuit.
  - e) Explain the characteristics of digital data.
- Q.2**
- a) Draw and explain 3 op-amp instrumentation amplifier, giving its applications. Explain any one application in detail. 10
  - b) Explain with circuit diagram, the working of ideal integrator. Give the problems associated with it and show how it is overcome in practical integrator. 10
- Q.3**
- a) Give the advantages of precision rectifier over traditional diode rectifier. Explain with a circuit diagram the working of absolute value circuit using op-amp. 10
  - b) Give the advantages of active filters over passive filters. Design a second order low pass Butterworth filter with a high cut-off frequency of 3 KHz. 10
- Q.4**
- a) Draw and explain, principle and working of RTD. What is the signal conditioning associated with it. 10
  - b) Using an RTD with  $\alpha = 0.0034 / ^\circ\text{C}$  and  $R = 100 \Omega$  at  $20^\circ\text{C}$ , design a bridge and op-amp circuit to provide 0 V to 10.0 V output for  $20^\circ\text{C}$  to  $100^\circ\text{C}$ . The RTD has  $P_D = 28 \text{ mW}/^\circ\text{C}$  and maximum  $\Delta T = 0.05^\circ\text{C}$  10
- Q.5**
- a) Design and explain the operation of Astable multivibrator using IC555. 10
  - b) Draw and explain the signal conditioning circuit used in strain gauges. 10
- Q.6** Write short notes on (any four): 20
- a) Phase locked loops
  - b) SMPS
  - c) V to F Converter
  - d) Flash type ADC
  - e) All pass filter