

em.V / signal Conditioning
Circuit Design

QP Code : 3335

/ 25-05-15

Duration : 03 Hours

Total Marks : 80

- Note:
- 1) Question No. 1 is compulsory.
 - 2) Answer any **three** questions from the remaining **five** questions.
 - 3) Assume **suitable data** wherever **necessary**.

1. Answer the following: 20
 - a) What are precision rectifiers? How are they superior to traditional rectifiers.
 - b) Briefly explain the concept of Loading with example.
 - c) Explain V-F convertor.
 - d) What are the four characteristics of three terminal IC regulators.
2.
 - a) Explain Dual slope Analog-to-Digital Convertor with diagram and waveform. 10
 - b) Explain operation of Astable Multivibrator using IC 555 with a neat circuit diagram and waveforms. 10
3.
 - a) Explain the construction and working of 3-opamp Instrumentation amplifier. Give any one of its applications in detail. 10
 - b) What the advantages of Active filters. Design a second order High Pass Butterworth filter with a cut-off frequency of 2 KHz. 10
4.
 - a) A CdS cell has a dark resistance of 100 k Ω and a resistance in a light beam of 30 k Ω . The cell time constant is 72 ms. Devise a system to trigger a 3-V comparator within 10 ms of the beam interruption. 10
 - b) Explain Optical encoder signal conditioning for linear displacement and linear velocity applications with suitable diagram. 10
5.
 - a) An RTD has $\alpha_0 = 0.005 / ^\circ\text{C}$; $R = 500 \Omega$ and Dissipation constant of $P_D = 30 \text{ mW}/^\circ\text{C}$ at 20°C . The RTD is used in a bridge circuit with $R_1 = R_2 = 500 \Omega$ and R_3 is a variable resistor used to null the bridge. If supply voltage is 10 V and RTD is placed in bath at 0°C , find the value of R_3 to null the bridge. 12
 - b) A Solid-state pressure sensor that outputs 25 mV/kPa for a pressure variation of 0.0 to 25 kPa will be used to measure the level of a liquid with a density of $1.3 \times 10^3 \text{ kg/m}^3$. What voltage output will be expected for level variations from 0 to 2.0 m? What is the sensitivity for level measurement expressed in mV/cm? 08
6. Write short notes on : 20
 - a) Sample and Hold circuit
 - b) Phase Locked Loops
 - c) Power supply design using 78xx
 - d) SMPS