

3 Hours

[Total Marks : 80]

Note : 1. Question no. 1 is compulsory

2. Attempt any **three** questions from remaining **five** questions
3. Assume suitable data whenever necessary



- Q.1. a. Draw and explain circuit diagram of peak detector. 20
- b. Explain lead compensation in bridge.
- c. A bridge circuit has $R_1 = R_2 = R_3 = 2k\Omega$ and $R_4 = 2.05\Omega$ resistances and a 5V supply. If a galvanometer with a 50Ω internal resistance is used for a detector, find the offset current.
- d. Explain the significance of all-pass filters.
- Q.2. a. What is the need for 3 op-amp instrumentation amplifier? Mention the applications of instrumentation amplifier. Explain any one in detail. 10
- b. Draw and explain circuit diagram of precision rectifier circuit using op-amp. Discuss its advantages over traditional diode rectifier. 10
- Q.3. a. Draw and explain circuit for ideal differentiator with waveforms. Discuss the problems associated with ideal integrator and draw the circuit diagram for practical differentiator. 10
- b. What are the advantages of active filters over passive filters. Design a second-order high pass filter at a high cut-off frequency of 1kHz. 10
- Q. 4. A CdS cell has a dark resistance of $100k\Omega$ and a resistance in a light beam of $30k\Omega$. The cell time constant is 72ms. Devise a system to trigger a 3-V comparator within 10ms of the beam interruption. 10
- b. Draw and explain the principle and construction of metal strain gauges. What is the signal conditioning associated with it. 10
- Q.5. a. Explain the following terms : 10
- (i) Signal level and bias changes
 - (ii) Filtering and impedance matching
 - (iii) Linearization
 - (iv) Concept of loading
- b. A sensor outputs a voltage ranging from -2.4 to -1.1V. For interface to an analog-to-digital converter, this needs to be 0 to 2.5V. Develop the required signal conditioning. 10

[TURN OVER]

Q.6. Write short notes on : (any four)

20

- a. Sample and hold circuit
- b. Phase Locked loop
- c. IC 555 timer
- d. Data Acquisition System
- e. A to D converters
- f. SMPS