



NB. Q.1 is Compulsory .

Solve any three questions from the remaining

- Q1** 20
- Explain SCR characteristics
  - Write advantages of IGBT and MOSFET
  - Explain need of synchronizing circuit in converters
  - Draw the circuit of Jones Chopper and explain the commutation of main SCR
- Q2.** 20
- Design a converter to give output voltage 150 V at 1A load current. The input is 230 V 50 Hz ac supply. Use UJT 2N2646.
- $V_{BBmax} = 35$  V for  $V_{bb} = 16$  V,  $C = 0.1 \mu F$ ,  $\beta_{min} = 0.56$ ,  $\beta_{max} = 0.75$ ,  $\eta_{type} = 0.63$   
 $I_v = 4$  mA,  $I_p = 25 \mu A$  Consider temperature compensation.
- Q3 a)** with the help of a neat diagram and associated waveforms discuss the operation of Buck-Boost converter. Also list the advantages and disadvantages of this type of converter.
- b)** Explain variable frequency I.M. drive. 10
- Q4**
- Describe the working of 1phase fully controlled bridge converter in the following two modes.  
 Rectifying mode 10  
 Inversion mode.  
 Also sketch the following waveforms for  $\alpha = 45^\circ$ , &  $\alpha = 120^\circ$
  - Write a short note on reduction of harmonic distortion. 5
  - Briefly explain the V-I characteristic of IGBT. 5
- Q5**
- Explain the application of power electronics in industrial heating process. 10
  - A 1-phase HW ac regulator feeds power to resistive load of  $6 \Omega$ , from 230 V, 50 Hz source. 10  
 The firing angle of SCR is  $\pi/2$ . Calculate  
 1) The rms value of output voltage  
 2) average input current.
- Q6**
- Explain the current fed ac drives & state its applications 10  
 State the significant features of traction drives 05  
 Explain any one type of forced commutation 05