

[3 Hours]

[Total Marks: 80]

NB. Q.1 is Compulsory.Solve any three questions from the remaining
Assume suitable data if required and justify it.**Q.1** Solve the following 20

- a) Explain UJT characteristics
- b) Write advantages of IGBT and MOSFET
- c) Explain need of synchronizing circuit in converters
- d) Draw the circuit of Jones Chopper and explain the commutation of main SCR

Q.2 a) What is the difference between series and parallel inverter? Explain series inverter. 10
 b) Explain the current fed ac drives & state its applications 10

Q.3 a) With the help of a neat diagram and associated waveforms discuss the operation of Buck-Boost converter. Also list the advantages and disadvantages of this type of converter. 10
 b) Explain variable frequency I.M. drive 10

Q.4 a) Describe the working of 1phase fully controlled bridge with RL load. 10
 b) Write a short note on reduction of harmonic distortion. 05
 c) Briefly explain the V-I characteristic of IGBT. 05

Q.5 a) Explain the induction heating process with examples. 10
 b) Explain Step-up chopper with neat waveforms. 10

Q.6 a) Draw the block diagram of brushless DC motor and explain it. 10
 b) State the significant features of traction drive 05
 c) Explain any one type of forced commutation 05
