

T-EC (Instan) SEM-VI
CBGS

26/11/18
(1/1)

[3 Hours]

[Total Marks: 80]

- NB.** Q.1 is Compulsory.
Solve any three questions from the remaining
Assume suitable data if required and justify it.
- Q.1** Solve the following 20
- Explain dynamic characteristics of SCR.
 - Write advantages of IGBT and MOSFET
 - Explain need of synchronizing circuit in converters
 - Explain the effect of source inductance
- Q.2** 10
- What is the difference between series and parallel inverter? Explain the working of series inverter.
 - Explain the current fed ac drives & state its applications
- Q.3** 10
- With the help of a neat diagram and associated waveforms discuss the operation of Buck-Boost converter. Also list the advantages and disadvantages of this type of converter.
 - Explain variable frequency I.M. drive 10
- Q.4** 10
- Describe the working of 1 phase fully controlled bridge with RL load.
 - What are the different PWM techniques. Explain with neat waveforms 10
- Q.5** 10
- Explain the induction heating process with examples.
 - Explain Step-up chopper with neat waveforms. 10
- Q.6** 20
- a) Design a dc power control circuit for input of 250V, 50 Hz, ac supply using SCRs and UJT trigger circuits for following requirements.
- Dc output voltage variable = 75 to 110 V
Load resistance = 10Ω
The minimum supply voltage used for trigger circuit with temperature compensation is

C _{μf}	0.07	0.1	0.2	0.3
V _{BB}	18	16	14	13

UJT specifications are

$$\eta_{\min} = 0.56 \quad \eta_{\max} = 0.75 \quad V_{BB\max} = 35V$$

$$I_p = 5\mu A \quad I_v = 4mA \quad V_v = 2V$$