

T.E.(INSTRUMENTATION)(SEM VI) (CBSGS) / DEC 2019/05.12.2019

Time: 3 Hours



Total Marks :80

NB. Q.1 is Compulsory.
Solve any four questions from the remaining.

- Q1** 20
- Explain SCR ratings
 - compare IGBT & MOSFET
 - Explain Commutation in Thyristor circuit
 - Differentiate between series & parallel inverter
- Q2.** 20
- Design a converter to give output voltage 120 V at 1A load current. The input is 230 V 50 Hz ac supply. Use UJT 2N2646.
 $V_{BBmax} = 35 \text{ V}$ for $V_{bb} = 16 \text{ V}$, $C = 0.1 \mu\text{F}$, $\eta_{min} = 0.56$, $\eta_{max} = 0.75$, $\eta_{type} = 0.63$
 $I_v = 4 \text{ mA}$, $I_p = 25 \mu\text{A}$ Consider temperature compensation.
- Q3**
- with the help of a neat diagram and associated waveforms discuss the operation of Buck converter. Also list the advantages and disadvantages of this type of converter. 10
 - Explain variable frequency I.M. drive. 10
- Q4**
- Describe the working of 1phase fully controlled bridge converter in the following two modes.
 - Rectifying mode 10
 - Inversion mode. 10
 Also sketch the following waveforms for $\alpha = 45^\circ$ & $\alpha = 120^\circ$
 - Write a note on control strategies used in chopper. 10
- Q 5**
- Explain the application of power electronics in industrial heating process. 10
 - Explain application of triac as an ac regulator. Draw relevant waveforms. 10
- Q6**
- Explain PWM inverter with appropriate waveforms 10
 - Explain full bridge inverter with R-L load. Also explain purpose of feedback diodes in these inverters. 10