

[3 Hours]

[Total Marks: 80]

- N.B. :** 1. **Question 1 is compulsory.**
 2. Solve **any three** from remaining.
 3. Assume suitable data if required and justify it.



Q.1) Attempt any four

[20]

- Explain Punch through IGBT
- Explain class C commutation circuit
- Write short note on reduction of harmonic distortion.
- List out advantage and disadvantages of series inverter and parallel inverter.
- Explain Type B chopper

Q.2) Design a converter to give output voltage 180 V at 1A load current. The input is 230 V 50 Hz ac supply. Use UJT 2N2646. $V_{BBmax} = 35 V$ for $V_{bb} = 16 V$, $C = 0.1 \mu F$, $\eta_{min} = 0.56$, $\eta_{max} = 0.75$, $\eta_{type} = 0.63 I_V = 4 mA$, $I_p = 25 \mu A$ Consider temperature compensation. [20]

Q.3)

- Explain variable AC induction motor drive. [10]
- Explain basic principle of Dielectric heating. List its advantages and applications. [10]

Q.4)

- Explain fan regulator using diac-triac scheme. [10]
- What are the different PWM techniques? Explain with neat waveforms. [10]

Q.5)

- With the help of a neat diagram and associated waveforms discuss the operation of Buck-Boost regulator [10]
- Explain symmetric semiconverter. [10]

Q.6)

- Draw the neat diagram and waveforms and explain Jones Chopper [10]
- Explain circuit diagram of full bridge inverter with free-wheeling diode. [10]