

Duration – 3 Hours

Total Marks - 80

- N.B.:** - (1) Question No.1 is compulsory.  
(2) **Attempt** any **Three** questions out of the remaining **five** questions.  
(3) Assume suitable data if necessary and justify the same.


Q 1. Answer **all** questions.

- A) Define with suitable example i) Tree and Co-tree ii) Graph and Oriented graph. **05**  
B) Find poles and zeroes of following function and plot pole zero diagram. (05) **05**


$$F(s) = \frac{s^2+4}{(s+2)(s^2+9)}$$

- C) State and explain maximum power transfer theorem **05**  
D) Obtain Y parameters in terms of Z parameters.

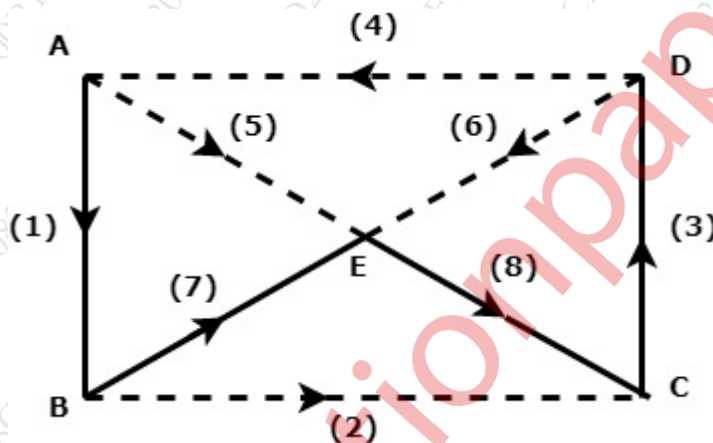
Q2a) For the graph shown below, write f-tieset and f-cutset matrix.



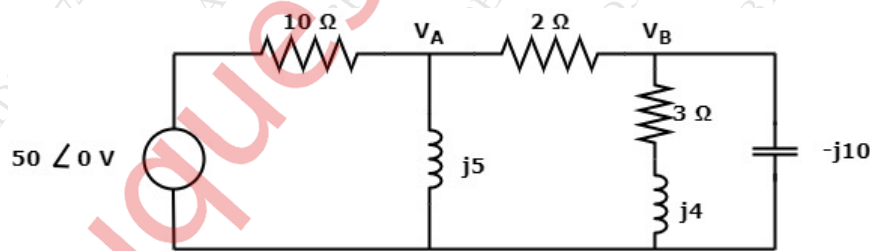Q2b) Determine  $V_A$  and  $V_B$  in the network shown below. **05**




Q 3a)

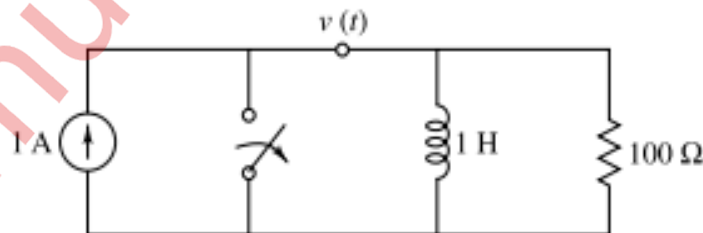


Find  $v$ ,  $\frac{dv}{dt}$ ,  $\frac{d^2v}{dt^2}$  when switch is opened at  $t=0$

Q3 b)

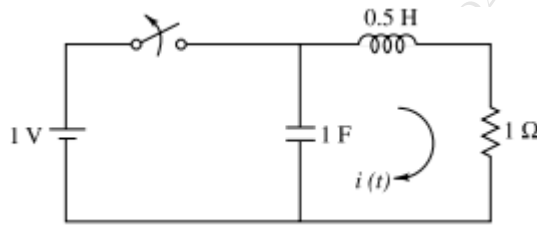


Switch is opened at  $t=0$ , steady state condition is reached before  $t=0$ . Find  $i(t)$  using laplace transform.

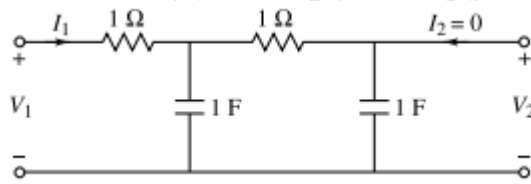Q4 a) For the network shown in, determine transfer function  $v_2/v_1$




Q4 b) Obtain h parameters in terms of ABCD parameters

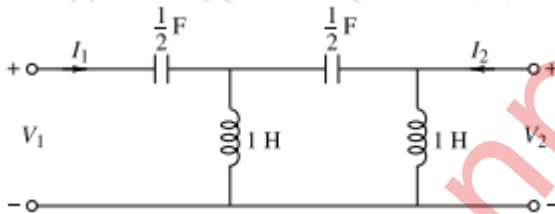Q5 a) Determine Y-parameters for the network shown



Q5 b) Write down restrictions on Pole and Zero Locations for Driving-Point Functions and Transfer Functions.

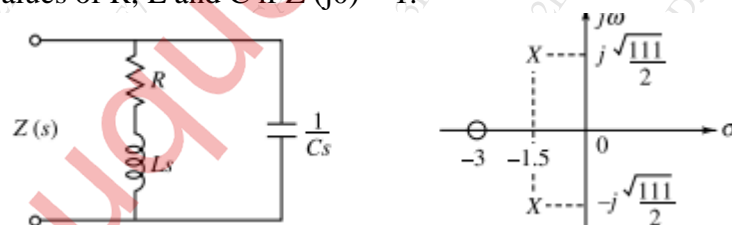
Q 6a) A network and its pole-zero configuration are shown in Fig. 10.53. Determine the values of R, L and C if  $Z(j0) = 1$ .



10

Q 6b) Calculate mesh currents in the circuit shown below.

10

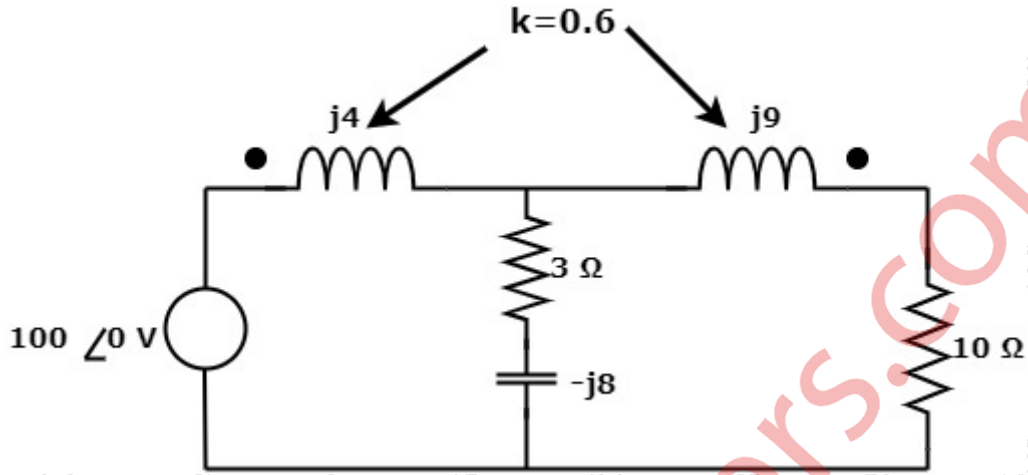

\*\*\*\*\*