

Time: 3 Hours

Marks: 80

Instructions:

- Question No: 1 is compulsory.
- Answer any three from the remaining five questions.
- Figures to the right indicate full marks.
- Answers to questions should be grouped and written together.

- Q1** a) Illustrate with neat diagram the mono polar and bipolar links of HVDC system. What are the main features of these links? **20**
- b) Illustrate the causes of over voltages in HVDC system and over voltage protection method used in HVDC system?
- c) Show that the expression for the power factor of an HVDC converter with grid control and overlap angle less than 60° is $\frac{1}{2}(\cos \alpha + \cos(\alpha + \mu))$
- d) Illustrate with block diagram the operation of HVDC Transmission for Offshore Wind Farms?
- Q2** a) Illustrate the relative merits of AC and DC mode of transmission based on economics of transmission and power flow through a conductor **10**
- b) Derive the equivalent circuit of three phase rectifier with grid control and overlap angle less than 60° . **10**
- Q3** a) Illustrate the control characteristics of HVDC and explain how power reversal is possible in HVDC. **10**
- b) Illustrate with neat diagram the equidistant pulse generation schemes used in HVDC system control method and mention its advantages and disadvantages? **10**
- Q4** a) What are the causes and effects of harmonics in HVDC system? How harmonics is classified? **10**
- b) Explain the transfer of current to bypass valve in rectifier operation. **10**
- Q5** a) Describe with neat diagrams single commutation failure of converters. **10**
- b) Calculate the secondary line voltage, active power, power factor and reactive power of the transformer for a three phase bridge rectifier to provide a DC voltage of 120 kV. Assume $\alpha = 30^\circ$, $\mu = 15^\circ$. What is the effective reactance X_L , if the rectifier gives 800 A of DC output current **10**
- Q6** a) What are the features of ground return used in HVDC systems? **10**
- b) With neat diagram explain components of HVDC system. **10**
