


Please Check whether you have got right question paper

- N.B.:
1. Question one is Compulsory.
  2. Answer any three questions from the remaining five.
  3. Assume suitable data if required.


**Q1 All Questions are Compulsory**

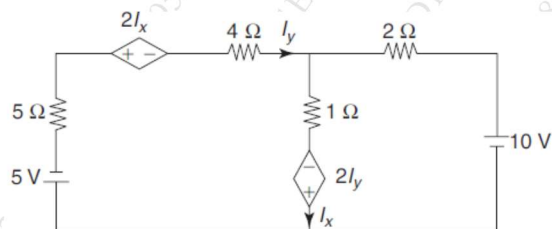**5 marks each**


a Find the Currents  $I_x$  and  $I_y$  of the Network shown in Figure-



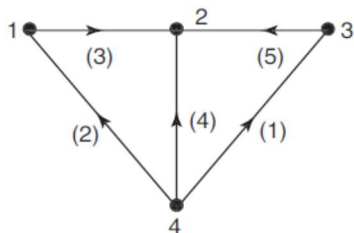b For the graph given, Obtain the Incidence Matrix and Find the number of possible trees.



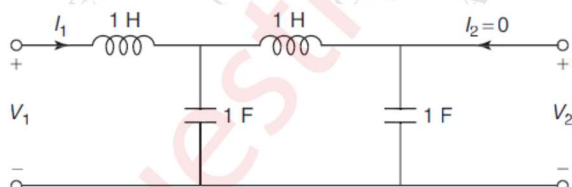c Find the Network function  $\frac{V_1}{I_1}$ ,  $\frac{V_2}{I_1}$  and  $\frac{V_2}{I_2}$  for the network shown-




d Check whether  $P(s) = S^4 + 5S^3 + 5S^2 + 4S + 10$  is Hurwitz.

**Q2**

**(20 Marks)**


a Find Norton's Equivalent Network at the terminal A and B of Figure shown-

**10M**

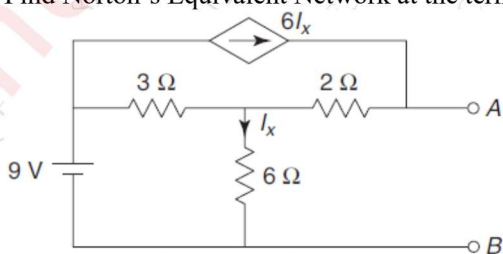


b In the Network Shown, the switch is changed from position 'a' to 'b' at  $t = 0$ . **10M**

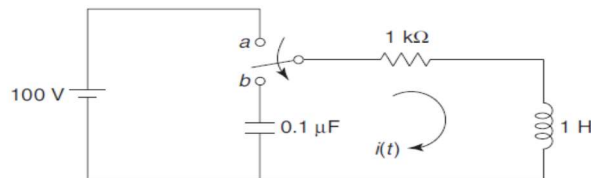Find  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$




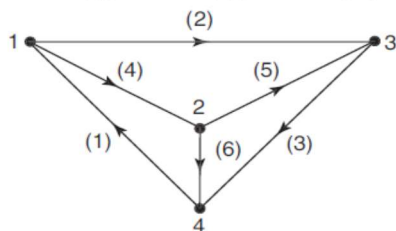**Q3** **(20 Marks)**

a The Graph of a Network is shown in Figure. Find Tieset Matrix and  $f$ -cutset Matrix **5M**



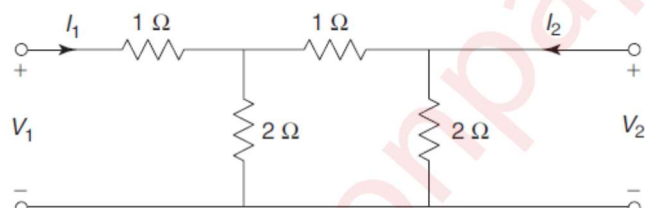b Find the ABCD parameters of the Network shown in Figure- **5M**




c Realise the Foster form- I and Foster form- II of RC Impedance Function. **10M**

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$$

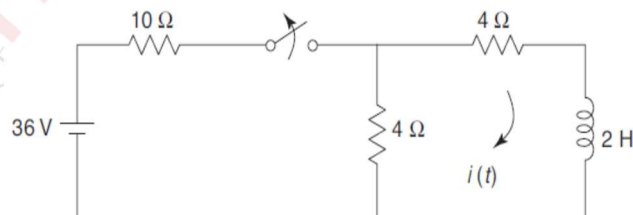
**Q4** **(20 Marks)**

a Test whether  $F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$  is positive real function. **5M**

b The Network Shown in figure has acquired steady state for switch closed at  $t < 0$ . At  $t = 0$ , the switch is opened. Obtain  $i(t)$  for  $t > 0$ . **5M**




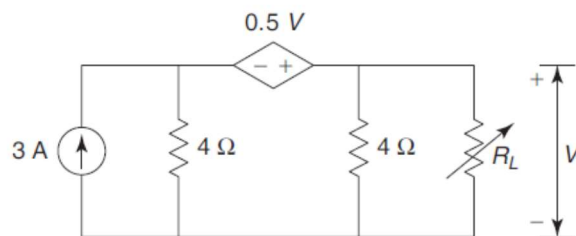- c What will be the value of  $R_L$  in the figure to get maximum power Delivered to it? What is the value of this power? **10M**




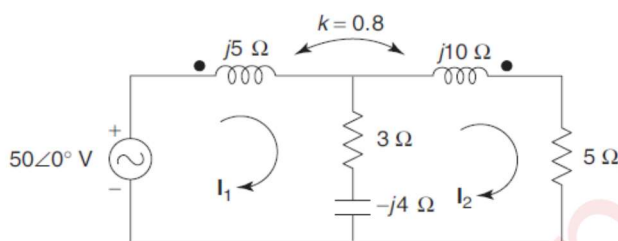**Q5 (20 Marks)**

- a Find the Voltage across  $5\Omega$  resistor using Mesh Analysis- **10M**




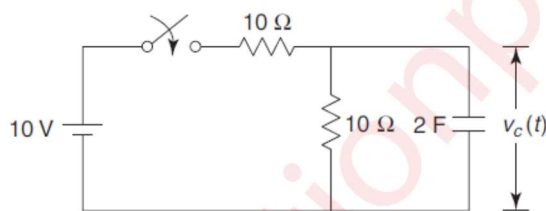- b The switch in the Network shown is closed at  $t = 0$ . Determine the Voltage across the capacitor  $V_C(t)$  for  $t > 0$  using Laplace Transform. **10M**



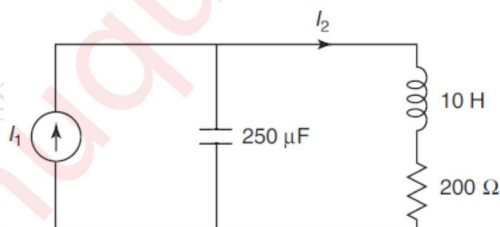**Q6 (20 Marks)**

- a Draw Pole-Zero diagram of  $\frac{I_2}{I_1}$  for the Network Shown in Figure **5M**



- b Find the Condition of Symmetry and Reciprocity of Two port Network Using Z-parameter **5M**

- c A network and its pole zero diagram shown in figure. Determine the Values of R , L and C if  $Z(j0) = 1$  **10M**

