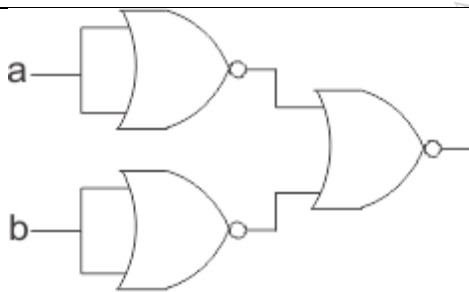


<b>Q1.</b>	<b>Choose the correct option for following questions. All the Questions are compulsory and carry equal marks</b>
1.	Which of the following gates is known as Universal Gate?
Option A:	XOR
Option B:	NOT
Option C:	AND
Option D:	NAND
2.	 <p>If Y is the output for the above figure, determine the output expression for the given logic diagram.</p>
Option A:	$Y=AB$
Option B:	$Y=A'B'$
Option C:	$Y=A+B$
Option D:	$Y=A\oplus B$
3.	Which of the following law is not correct?
Option A:	$A + 1 = 1$
Option B:	$A + A = A$
Option C:	$A.A = A$
Option D:	$A + A' = 0$
4.	Which of the following is NOT considered for forming groups in K-map?
Option A:	Rolling
Option B:	Diagonal
Option C:	Vertical
Option D:	Horizontal
5.	Which of the following is not an example of sequential circuit?
Option A:	Flip flop
Option B:	Counter
Option C:	Magnitude Comparator
Option D:	Shift Register
6.	2's complement representation of 23 is_____.
Option A:	1101000
Option B:	1101001
Option C:	1100100
Option D:	1101010

7.	A ____ is composed of a group of flip flops to store a group of bits.
Option A:	Counter
Option B:	Decoder
Option C:	Demultiplexer
Option D:	Register
8.	Shift register application includes_____
Option A:	Ring counter
Option B:	Decade counter
Option C:	Bounce elimination switch
Option D:	BCD to 7-segment decoder
9.	Which of the following is true about PAL?
Option A:	Both OR & AND array are programmable.
Option B:	AND array is programmable & OR array is fixed.
Option C:	AND array is fixed & OR array is programmable.
Option D:	Both OR & AND array are fixed.
10.	A declaration of a module's inputs and outputs in VHDL is_____
Option A:	VHDL entity
Option B:	VHDL architecture
Option C:	VHDL Interface
Option D:	VHDL Conceptual Model

<b>Q2</b> <b>(20 Marks)</b>	<b>Solve any Four out of Six</b>	<b>5 marks each</b>
A	Perform the given conversion, $(FBE6)_{16} = (?)_{10} = (?)_2 = (?)_8$	
B	What are universal gates? Why they are called universal gates? Justify with example.	
C	Write basic laws for Boolean algebra.	
D	Give Comparison for TTL and CMOS logic families.	
E	Compare decoder and demultiplexer.	
F	List different types of flip-flops with their characteristic equations.	

<b>Q3</b> <b>(20 Marks)</b>	<b>Solve any Two Questions out of Three</b>	<b>10 marks each</b>
A	Get the minimal expression using Quine McClusky method for the following logic function: $f(A,B,C,D) = \sum m(1, 3, 5, 8, 9, 11, 15) + d(2,13)$	
B	Design & implement 4-bit Binary to Gray code converter.	
C	What is modulus of a digital counter? Design a synchronous counter with irregular binary count sequence 1----2----5----7. Use JK flips flop.	

<b>Q4</b> <b>(20 Marks)</b>	<b>Please delete the instruction shown in front of every sub question</b>	
A	<b>Solve any Two</b>	<b>5 marks each</b>

i.	Convert D flip flop to T flip flop
ii.	Write a VHDL code for 4:1 MUX.
iii.	Give classification of semiconductor memories and explain about DRAM in brief.
<b>B</b>	<b>Solve any One</b> <span style="float: right;"><b>10 marks each</b></span>
i.	Draw the block diagram of BCD adder using IC 7483 and show with example the addition of two BCD numbers
ii.	Explain different application of sequential circuits with relevant diagrams.

muquestionpapers.com