

# University of Mumbai

## Examinations Summer 2022

Program: Electronics and Telecommunication Engineering


Curriculum Scheme: Rev2019

Examination: SE Semester III

Course Code: ECC302 and Course Name: Electronic Devices and Circuits

Time: 2 hour 30 minutes

Max. Marks: 80

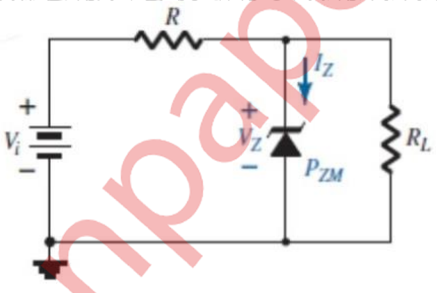Q1.	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
1.	The reverse saturation current of a transistor increases with the increase of temperature at the rate of:
Option A:	doubles in value for every 1°C increase in temperature
Option B:	doubles in value for every 25°C increase in temperature
Option C:	doubles in value for every 10°C increase in temperature
Option D:	quadruples in value for every 100°C increase in temperature
2.	Calculate the voltage across $R_L$ . $V_i = 9\text{ V}$ , $V_Z = 3\text{ V}$ , $R = 6.8\text{ KOhms}$ , $R_L = 2.2\text{ KOhms}$ 
Option A:	3 V
Option B:	2.2 V
Option C:	9 V
Option D:	4.4 V
3.	For a JFET self bias circuit, if the source resistance is increased keeping all other parameters constant, what is the effect on the operating point?
Option A:	Can't change Source resistance
Option B:	Remains same
Option C:	It moves towards $I_D = I_{DSS}$ , $V_{GS} = 0$
Option D:	It moves towards $I_D = 0$ , $V_{GS} = V_P$
4.	Adding a Resistor between emitter of BJT and Ground terminal of a CE BJT amplifier
Option A:	Decreases the stability of the amplifier
Option B:	Improves the stability of the amplifier
Option C:	Increases the Gain of the amplifier
Option D:	Has no effect
5.	To operate as an amplifier, BJT and MOSFET should operate in _____ & _____ regions respectively
Option A:	Active and Saturation

Option B:	Saturation and linear
Option C:	Cutoff and Linear
Option D:	Saturation and Cutoff
6.	For the fixed bias circuit shown, calculate the small signal input impedance, $Z_i$ in Ohms. $\beta=120$ . $R_B=240K\Omega$ , $R_C=1.2K\Omega$ , $V_{CC} = 12 V$ , $V_{BE} = 0.7 V$ ,
Option A:	1.2 KOhm
Option B:	240 Kohm
Option C:	551 ohm
Option D:	1 KOhm
7.	High cutoff frequency of an amplifier depends on
Option A:	Output Coupling capacitor
Option B:	bypass capacitor
Option C:	Input Coupling capacitor
Option D:	Parasitic capacitor
8.	For a direct coupled amplifier, if $f_H = 200$ KHz then calculate the bandwidth of the amplifier.
Option A:	1 KHz
Option B:	100 KHz
Option C:	200 KHz
Option D:	400 KHz
9.	If output is measured between two collectors of transistors, then the Differential amplifier with two input signal is said to be configured as
Option A:	Dual Input Balanced Output
Option B:	Dual Input Unbalanced Output
Option C:	Single Input Balanced Output
Option D:	Single Input Unbalanced Output
10.	Power amplifier directly amplifies _____
Option A:	Voltage of signal but not Current
Option B:	Current of the signal but not Voltage
Option C:	Power of the signal but not Voltage and Current
Option D:	Voltage, Current and Power of the signal

<b>Q2.</b>	<b>Solve any Two Questions out of Three 10 marks each</b>
A	<p>Determine the following for the network given below Fig. 1 Voltage gain, Current gain, input impedance and output impedance</p> <p style="text-align: center;">Fig. 1</p>
B	With neat diagram derive the efficiency of transformer coupled class –A power amplifier? State its uses.
C	Explain construction and working of n-channel E-MOSFET with output characteristics

<b>Q3</b>	
A	<b>Solve any Two 5 marks each</b>
i.	For a Class B amplifier providing an 18 V peak signal to a 20 Ω load (Speaker) and a power supply of VCC = 20 V, determine the output power, input power and efficiency.
ii.	Why should be Rc as large as possible in design of CE amplifier?
iii.	Explain Zener diode as a voltage regulator.
B	<b>Solve any One 10 marks each</b>
i.	Let $V_{DD} = 5V$ , $V_{TH,1} = 1V$ , $k_{n,1}' = 20\mu A/V^2$ and $R = 1K\Omega$ . What should be $(W/L)_1$ needed for creating $I_{ref} = 1mA$ ? What should be $(W/L)_2$ if we want $I_o = 7mA$ , 10 mA and 15 mA? Refer Fig. 2
	<p style="text-align: center;">Fig. 2</p>

ii.	<p>For the circuit shown in Fig. 3, the transistor parameter are <math>V_{BE}(\text{on}) = 0.7\text{V}</math>, <math>\beta = 200</math>, <math>V_A = \infty</math>,</p> <ol style="list-style-type: none"> <li>Derive the expression for lower cutoff frequency due to input coupling capacitor.</li> <li>Determine lower cut-off frequency and voltage gain</li> </ol>
-----	---

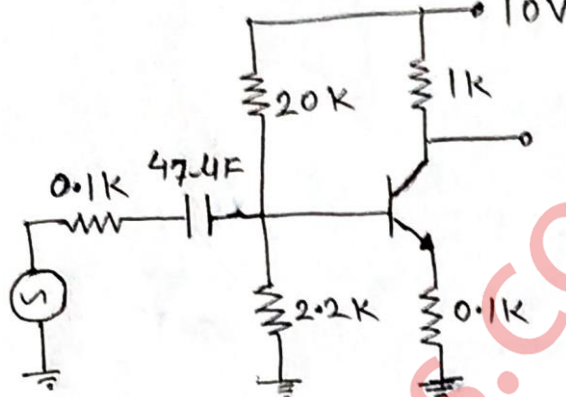


Fig.3

Q4	Solve any Two	10 marks each
A	Explain the operation of a Differential amplifier for common mode signals and differential input signals. Also explain CMRR.	
B	<p>Determine <math>f_L</math>, <math>f_H</math>, <math>f_T</math>.</p> <p>Given: <math>k_n' = \mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2</math>, <math>V_{Tn} = 0.5\text{V}</math>  <math>W = 1.8 \mu\text{m}</math>, <math>L = 180\text{nm}</math>, <math>\gamma_d = \infty</math></p> <p><math>C_{gd} = 2\text{pF}</math>, <math>C_{gs} = 4\text{pF}</math>, <math>C_{ds} = 0.5\text{pF}</math>, <math>C_{Wi} = 5\text{pF}</math>, <math>C_{Wo} = 6\text{pF}</math></p>	

C Design a voltage divider bias circuit operating at ( $V_{CEQ} = 12\text{ V}$ ,  $I_{CQ} = 2\text{ mA}$ ) for  $S(I_{CQ}) \leq 5$ . Given:  $\beta = 100$ ,  $V_{CC} = 20$

