

Duration: 3hrs

[Max Marks:80]

- N.B. :** (1) Question No 1 is Compulsory.
 (2) Attempt any three questions out of the remaining five.
 (3) All questions carry equal marks.
 (4) Assume suitable data, if required and state it clearly.

- 1 Attempt any FOUR [20]
- 1-bit 5 stage shift register
 - Explain the working of floating gate transistor in Flash memory.
 - For enhancement type NMOS transistor threshold voltage $V_T=0.7V$, $\mu_n C_{ox} = 40 \mu A/V^2$, $W = 30 \mu m$, $L = 10 \mu m$. Calculate I_D if for $V_{GS} = 2$, $V_{DS} = 2V$
 - Explain clock distribution in VLSI design.
 - Draw HLSM of soda dispenser machine
- 2 a Consider a CMOS inverter with following parameters: [10]
- | | | | |
|------|-------------------|-------------------------------|----------------|
| nMOS | $V_{TN} = 0.6 V$ | $\mu_n C_{ox} = 60 \mu A/V^2$ | $(W/L)_n = 8$ |
| pMOS | $V_{Tp} = -0.7 V$ | $\mu_p C_{ox} = 25 \mu A/V^2$ | $(W/L)_p = 12$ |
- Calculate the V_{IL} and V_{TH} . The power supply voltage is $V_{DD} = 3.3 V$.
- Explain pWell fabrication process with neat diagrams. [10]
- 3 a Realize SR flip flop using CMOS logic and draw its layout. [10]
- Explain 6T SRAM with its read and write operation. [10]
- 4 a Realize the expression $Y=A(B+C) D$ using the following logic style. [10]
- CMOS logic
 - Pseudo NMOS
 - Dynamic Logic
 - Domino Logic
- b Implement the following [10]
- 3x3 Array multiplier
 - 4:1 mux using TG
- 5 a Implement the following [10]
- 4 bit carry lookahead adder carry using dynamic logic
 - 8-bit carry bypass adder

- b Draw 4 *4 bit NAND based array and NOR based array to store the following data [10]
in respective memory locations.

Memory address	Data
1000	0101
0100	1101
0010	0010
0001	1011

- 6 a Design a 'serial FIR filter' using the RTL design process. Draw HLSM,FSM, [10]
interface and Datapath
- b Realize the expression $Y = A + BC(D+E) + F$ using CMOS logic. Find equivalent [10]
CMOS inverter for simultaneously switching of all input. Assume $\left(\frac{W}{L}\right)p = 15$,
 $\left(\frac{W}{L}\right)n = 10$
