

Duration: 3hrs

[Max Marks:80]

- N.B. : (1) Question No 1 is Compulsory.
 (2) Attempt any three questions out of the remaining five.
 (3) All questions carry equal marks.
 (4) Assume suitable data, if required and state it clearly.

1 Attempt any FOUR [20]

- What are the advantages & disadvantages of negative feedback?
- Draw block diagram of oscillator. State and explain Barkhausens criteria
- Write a short note on current mirror circuit
- Derive efficiency of Class A transformer coupled power amplifier
- Compare voltage amplifier and power amplifier

2 a Determine the lower cut off frequency due to the effect of coupling and bypass [10]

capacitors for an amplifier in figure 1 with the following specifications:

$V_{cc} = 20V$, $R_1 = 40K\Omega$, $R_2 = 10K\Omega$, $R_c = 4K\Omega$, $R_E = 2K\Omega$, $R_L = 2.2K\Omega$

$CC1 = 10\mu F$, $CC2 = 1\mu F$, $C_E = 20\mu F$, Assume $r_o = \infty$ and $\beta = 100$

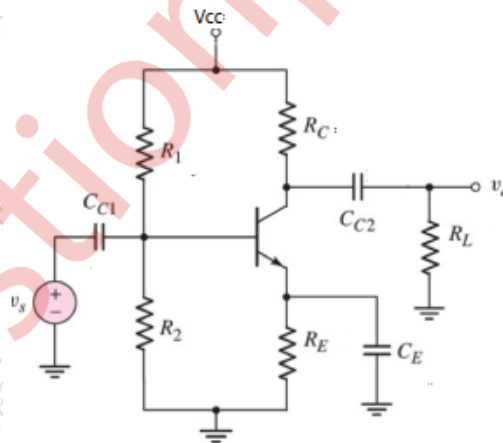


Figure. 1

b Write a short note on FET Cascode amplifier (CS-CG). [10]

3 a Explain voltage series negative feedback amplifier with help of block diagram [10]

and derive expression for R_{if} , R_{of} and A_f .

b Explain the Hartley oscillator with neat labelled diagram. Describe its [10]

advantages, disadvantages and applications.

- 4 a Explain in brief MOSFET differential amplifier with active load and small signal analysis of MOSFET active load circuit [10]
- b Explain Class-B power amplifier and crossover distortion. Drive expression for its efficiency. [10]
- 5 a Explain the Low frequency response of CS amplifier with proper equations. [10]
- b Write a short note on types of coupling used in multistage amplifiers [10]
- 6 a For the differential amplifier in Figure 2, the parameters are: $V^+ = 5\text{ V}$, $V^- = -5\text{ V}$, $R_1 = 80\text{ k}\Omega$, and $R_D = 40\text{ k}\Omega$. The transistor parameters are $\lambda = 0$ and $V_{TN} = 0.8\text{ V}$ for all transistors, and $K_{n3} = K_{n4} = 100\mu\text{A}/\text{V}^2$ and $K_{n1} = K_{n2} = 50\mu\text{A}/\text{V}^2$. Determine the range of the common-mode input voltage. [10]


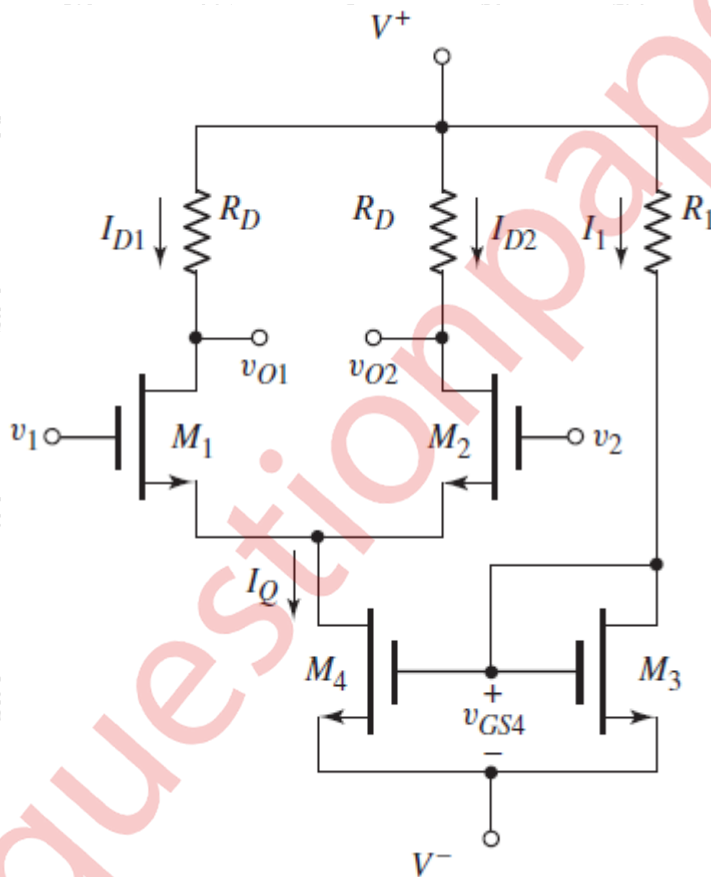


Figure 2.

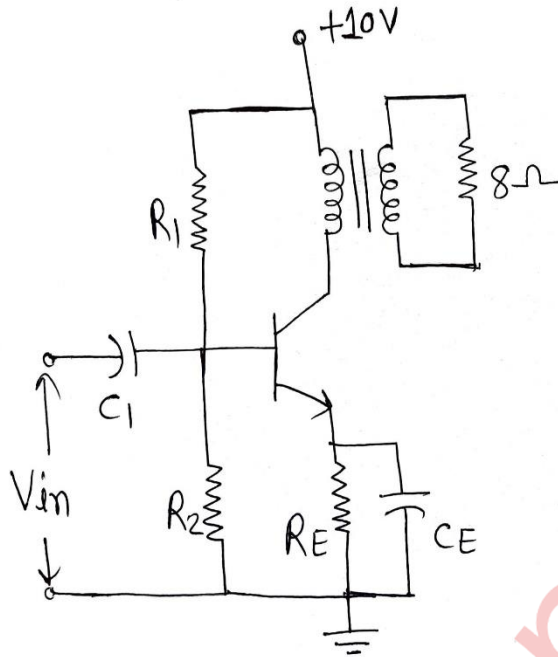- b Calculate AC Power delivered to the 8Ω speaker, DC input power, power dissipated by the transistor and efficiency of the circuit shown in figure 3. [10]



$$V_{CEQ} = 10V$$

$$I_{CEQ} = 140\text{ mA}$$

$$V_{CEmin} = 1.7V$$

$$V_{CEmax} = 18.3V$$

$$I_{Cmin} = 25\text{ mA}$$

$$I_{Cmax} = 255\text{ mA}$$

Figure 3.