

Time: 3 Hrs

Max. Marks: 80

- N.B.:** - (1) Question number 1 is compulsory.  
 (2) Solve any Three from remaining five questions.  
 (3) Draw neat logic diagram & assume suitable data whenever necessary.


**Q.1 Solve any four**

**Marks**

- a List any six features of VHDL. 05
- b Differentiate between Mealy and Moore machine. 05
- c Write a VHDL code for Half adder circuit. 05
- d Explain Booth's multiplication with example. 05
- e Write a short note on Register transfer level (RTL). 05

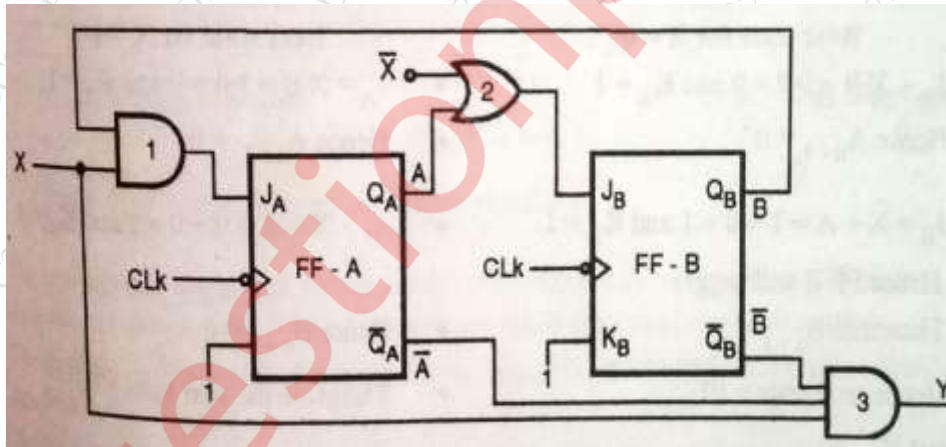**Q.2**

- a Analyze the sequential circuit shown below. Hence derive the state table and state diagram. 10



- b Write a VHDL code for JK flip flop 10


**Q.3**

- a Design a Mealy sequence detector circuit to detect an overlapping sequence "1010" using D flip flop and logic gates. 10
- b Write a VHDL code for Traffic light controller system. 10

 **Q.4**

- a Write a VHDL code for 4 bit UP-DN counter using asynchronous reset. 10

- b For a given state diagram obtain a reduced state diagram using state reduction technique. 10



**Q.5**

- a List the features of XC4000 FPGA family and discuss it with the help of neat block diagram. 10
- b Write a VHDL code for Booth's multiplier. 10

**Q.6 Solve any Four**

- a Write a short note on different modelling styles used in VHDL. 05
- b List the features of complex programmable logic devices. 05
- c Write a VHDL code for 2-bit parallel multiplier in data flow modelling. 05
- d Write a short note on functional and timing simulation. 05
- e Explain VHDL operators with example. 05

\*\*\*\*\*