

Circuit Theory

19-11-2013-DTP-P-7-RA-10

Con. 8952-13.


GX - 12149

(3 Hours)

[ Total Marks : 80


- N. B. :**
- (1) Question No. 1 is compulsory.
  - (2) Attempt any **three** questions from remaining.
  - (3) **Figures** to the right indicate full marks.
  - (4) Assume **suitable data** if required.
  - (5) Use Smith Chart for transmission line problems.

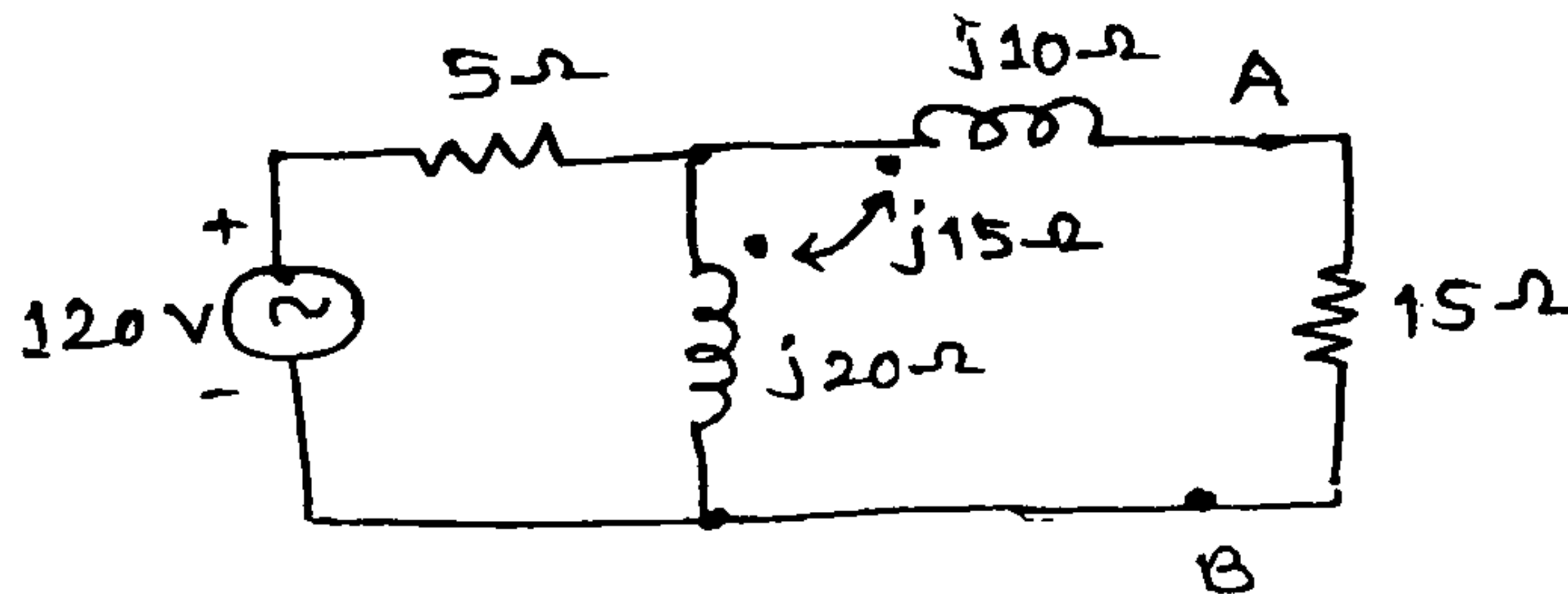1. (a) Find the current through  $15\Omega$  resistor. 4



- (b) Obtain the voltage response of series R-L circuit. 4

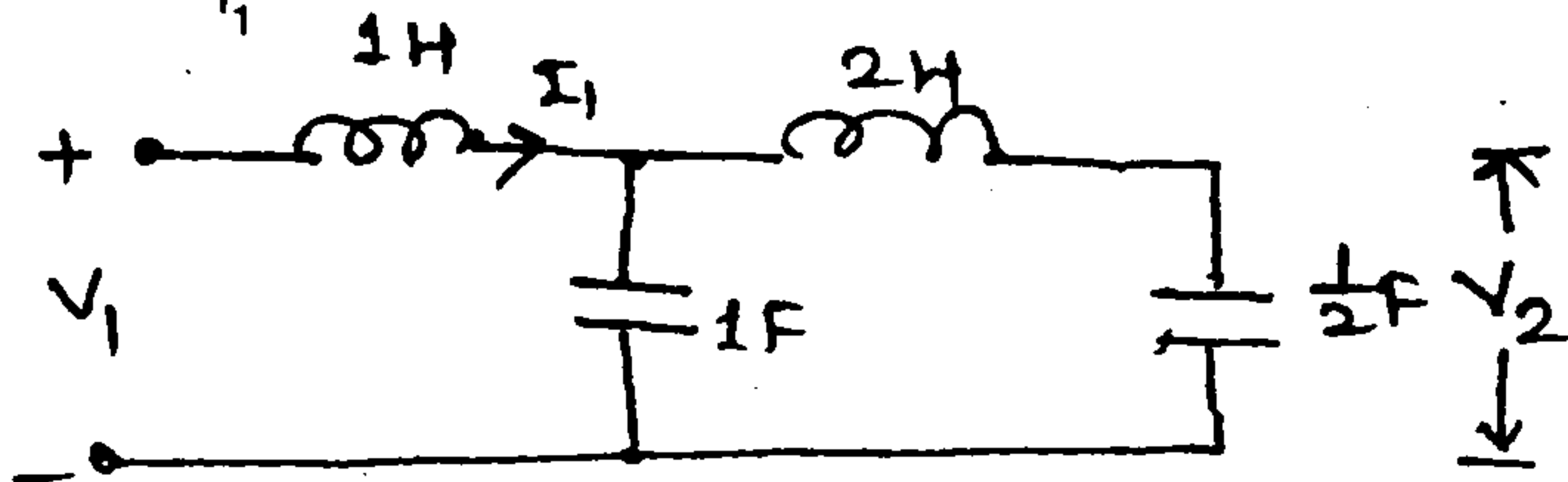- (c) Determine  $\frac{V_1}{I_1}$  and  $\frac{V_2}{I_1}$  for the given network. 4




- (d) What are standing waves? Define reflection coefficient and VSWR of a transmission line. 4

- (e) A  $\Pi$ -section filter network consists of a series arm conductor of 20 mH and two shunt arm capacitors of 160 nF each. 4

Calculate : (i) cut off frequency (ii) attenuation (iii) Phase shift at 15kHz.  
Also obtain the nominal impedance in pass-band.

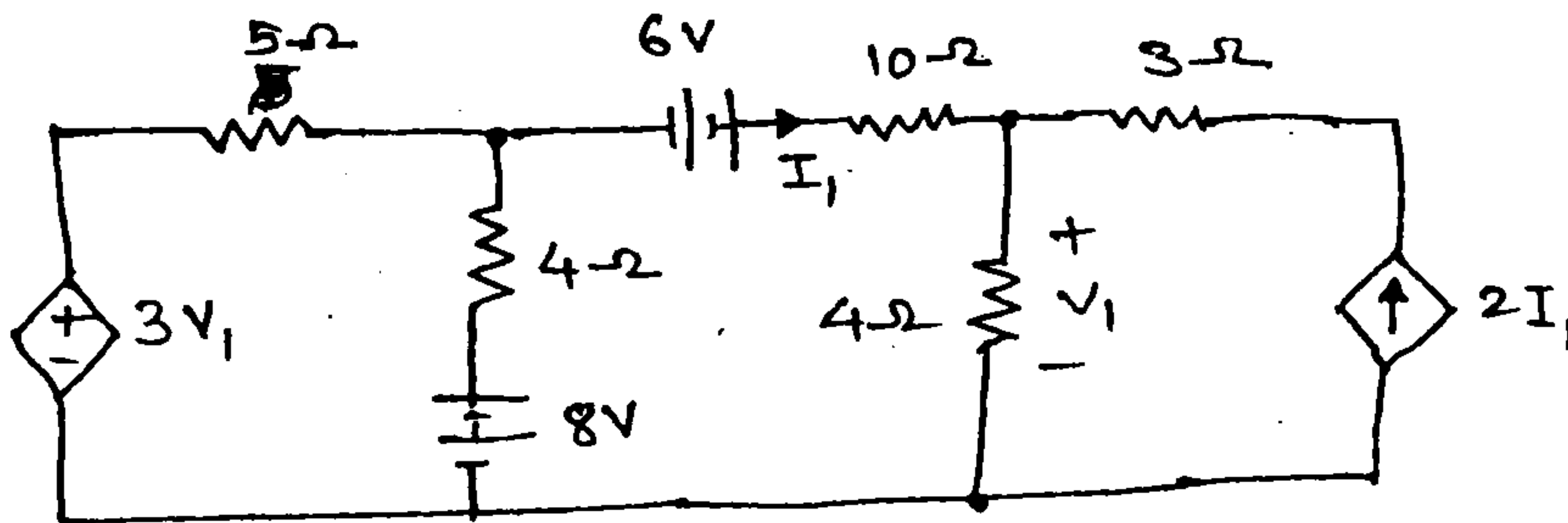
2. (a) Find  $I_1$  through  $10\Omega$  by Thevenin's theorem. 6



[ TURN OVER

(b) Find  $I_c$  and  $V_c$  for  $t > 0$

8

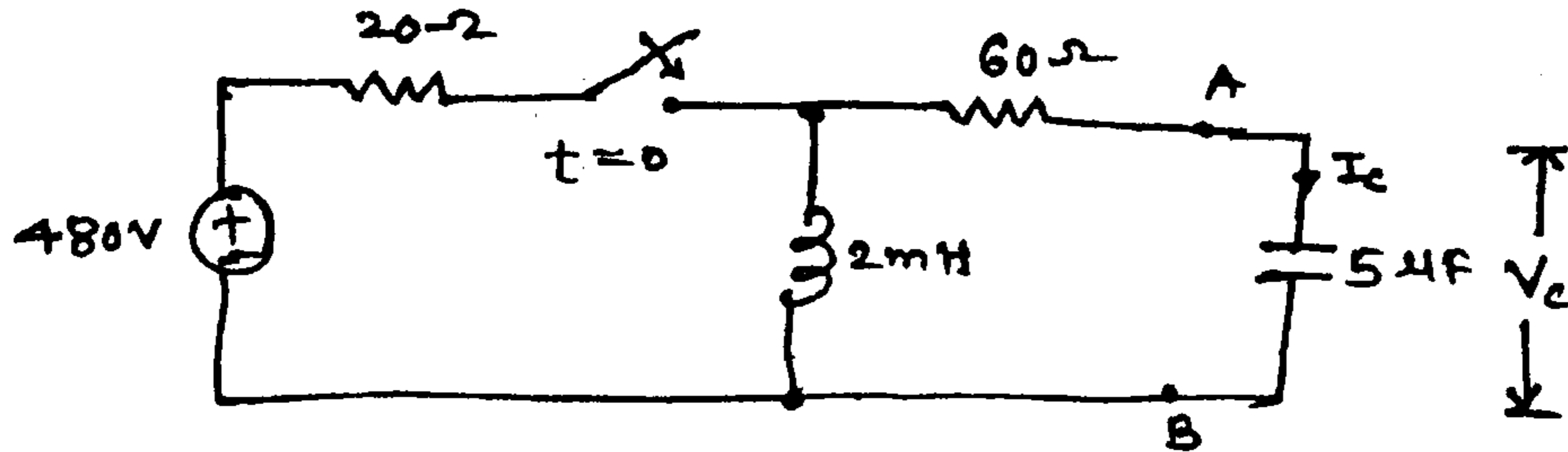

(c) Use Nodal analysis to find the voltage drop across  $4 \Omega$  and  $10 \Omega$  ref Qu. 2(a)

6

3. (a) Design a single stub match for a load of  $150 \Omega + j 232.5 \Omega$  for  $75 \Omega$  line at 500 MHz using Smith Chart.

8

(b) Compare foster realization with caurer realizations.

8

(c) State the properties of Hurwitz polynomial.

4

4. (a) Define T-parameters and relate them to other parameter as indicated.

8

(i) A and C interms of z-parameters

(ii) B interms of y-parameters

(iii) D interms of h-parameter.

(b) Test whether the following functions are positive real functions with proper reasons.

12

(i)  $F_1(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$

(ii)  $F_2(s) = \frac{s^2 + 1}{s(s^2 + 4)}$


5. (a) What are scattering parameters ? State their properties.

6

(b) Derive an expression of m-derived  $\Pi$  section network starting from a constant k section.

6

(c) For given circuit,

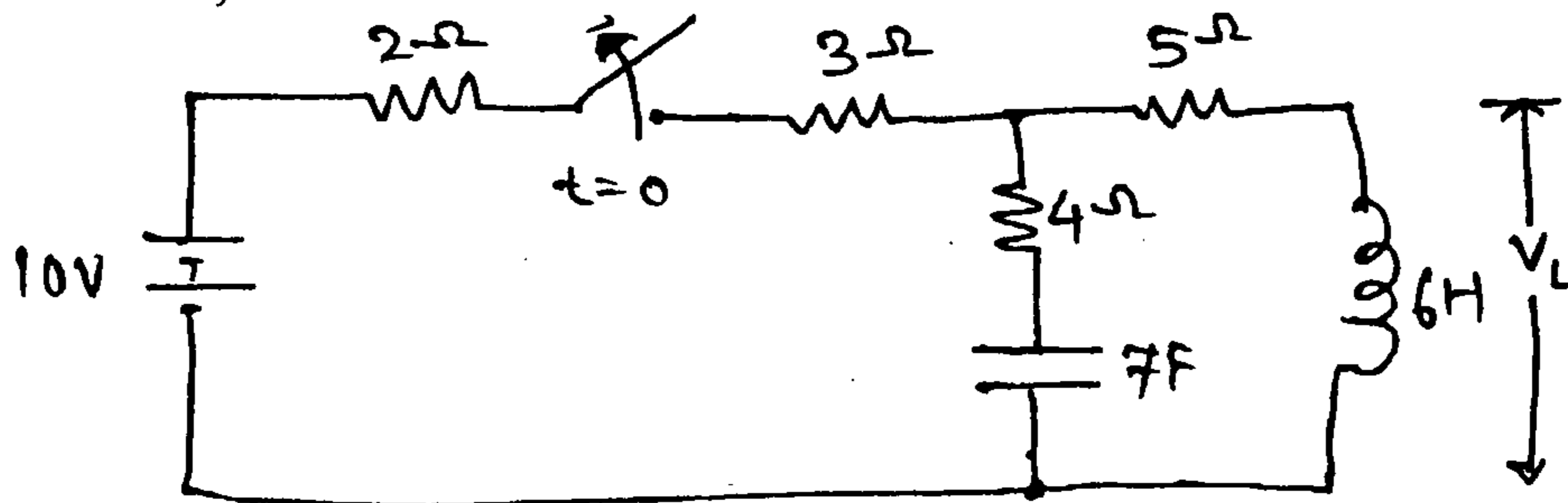

8

switch 's' is opened at  $t=0$ . Switch 's' was on for long time.

Determine  $V_L(0^+)$ ,  $\frac{dV_L}{dt}(0^+)$  and  $\frac{d^2V_L}{dt^2}(0^+)$

[ TURN OVER

6. (a) Explain the graphical representation of series resonance circuit. 6
- (b) Test whether following polynomials are Hurwitz 8
- (i)  $P(s) = s^4 + s^3 + 5s^2 + 3s + 4$
- (ii)  $P(s) = s^6 + 6s^4 + 4s^2 + 2$
- (c) Find the characteristic impedance, cut off frequency and pass band for the network 6  
shown :

