
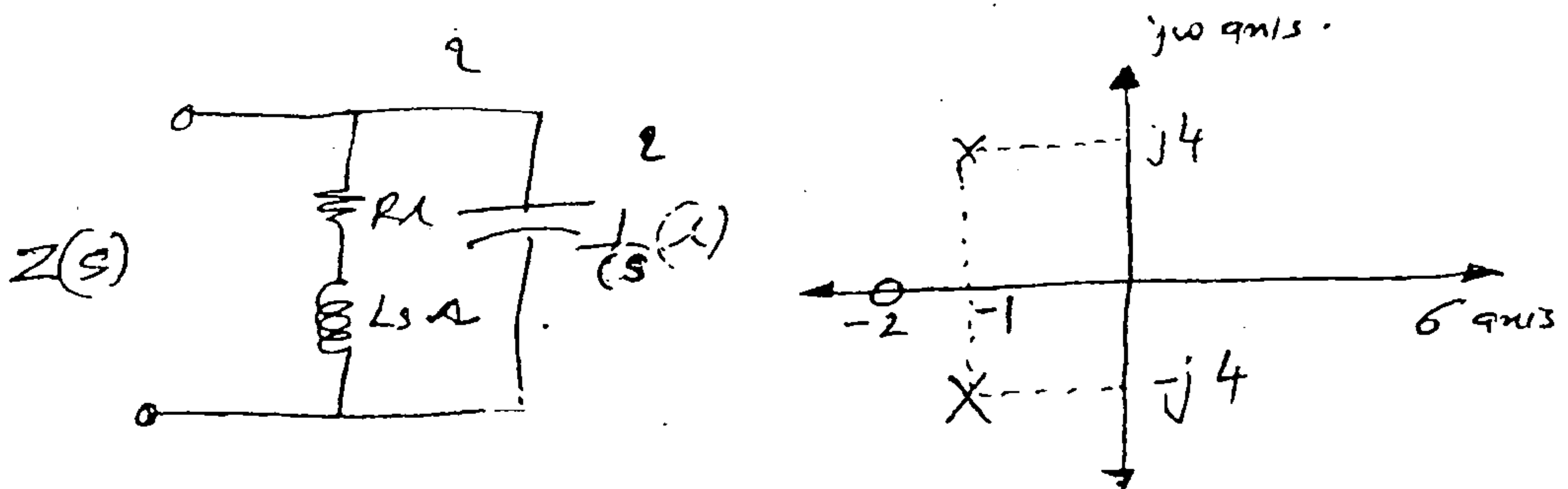


- N.B. : (1) Question No. 1 is Compulsory
 (2) Attempt any three questions from the remaining
 (3) Figures to the right indicate full marks.
 (4) Assume suitable data if required
 (5) Use Smith Chart For transmission line problem.

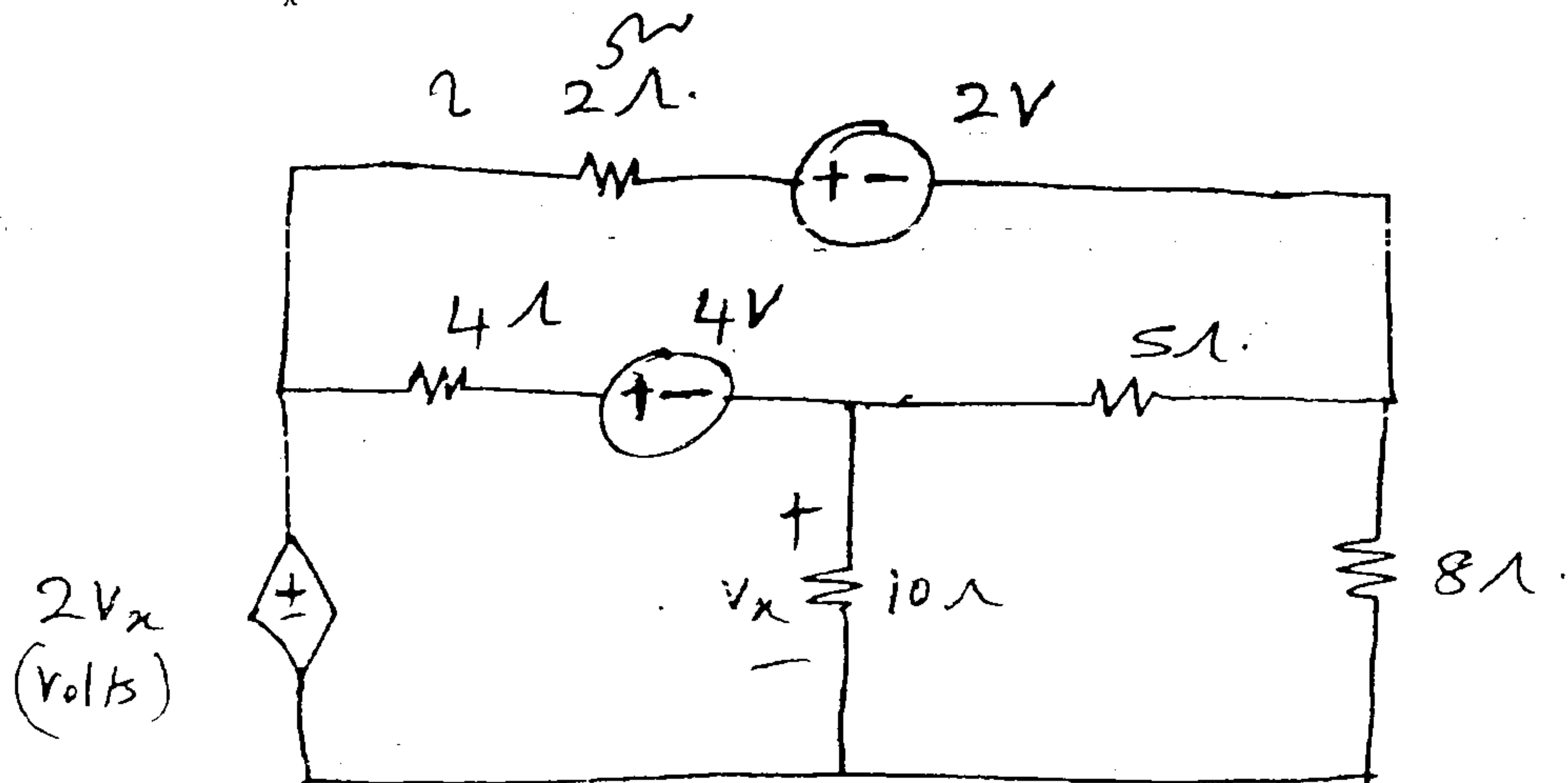1. (a) Test for following polynomal using continued fraction expansion only 20
 $F(s) = s^6 + 2s^5 + 3s^4 + 4s^3 + 3s^2 + 2s + 1$
- (b) Obtain s-domain equailant model at inductor and capacitor with non-zero inital condition.
- (c) The paranelex of a transmission line are $G = 2.25 \text{ m } \Omega / \text{km}$, $R = 65 \text{ } \Omega / \text{km}$, $L = 1.6 \text{ m H} / \text{km}$, $C = 0.1 \text{ } \mu \text{F} / \text{km}$ find charteristic impedance and the propogation constant of the line at a frequency of 1 KHz. $C = 0.1 \text{ } \mu \text{F} / \text{km}$
- (d) The ploer-zero diagram of driving point impedacne funtion is shown At d.c. the input impedance is resistive and equal to $2 \text{ } \Omega$ Determine value of R, Land C.




2. (a) Determine voltage V_x by Source shifting and Source transformation. 8



(b) Find $i_1(t)$, $i_2(t)$ and $i_3(t)$ at $t = 0^-$

8

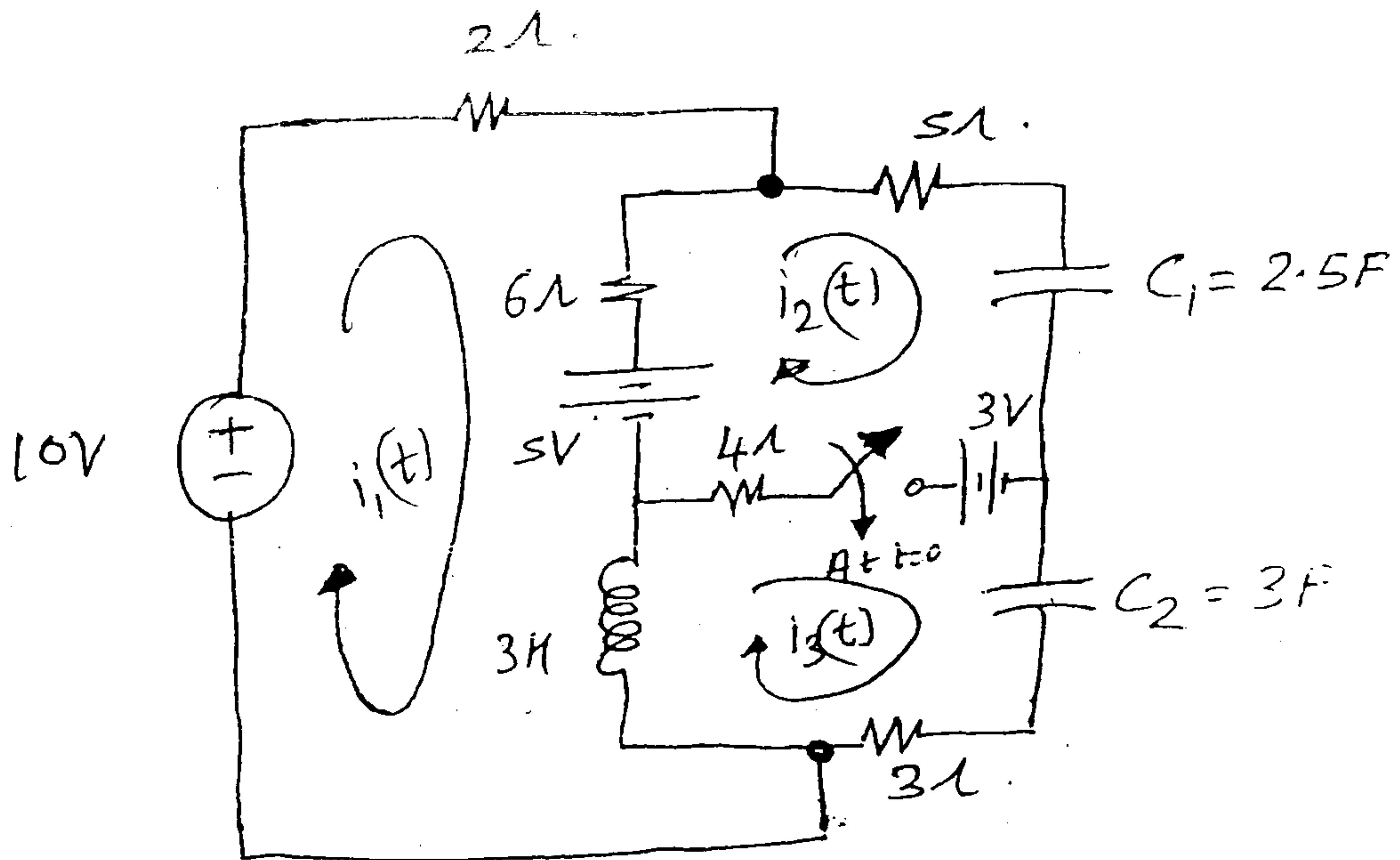

(c) Compare Foster form I and Foster Form II of an LC N/W

4


$$z(s) = \frac{6s(s^2 + 4)}{(s^2 + 1)(s^2 + 64)}$$

M eqn Hertz

3. (a) Design a short circuit shunt stub match for $Z_L = 150 - 200j (\Omega)$ for a line of $z_0 = 100 \Omega$ and frequency at $f = 20$ MHz use Smith chart.
- (b) Obtain Power associated with dependent voltage source by using Nodal analysis.

8

8

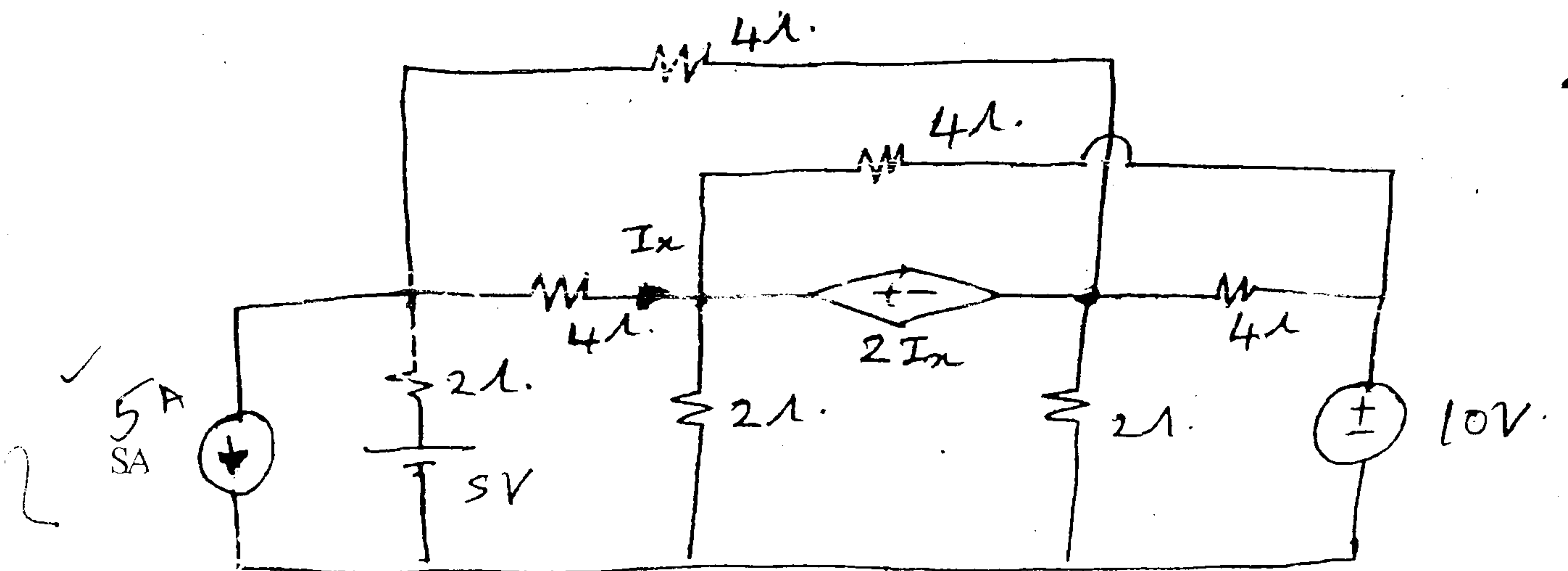


(c) Explain various types of filter's

4


4. (a) Obtain hybrid parameter of the inter connected network.

10

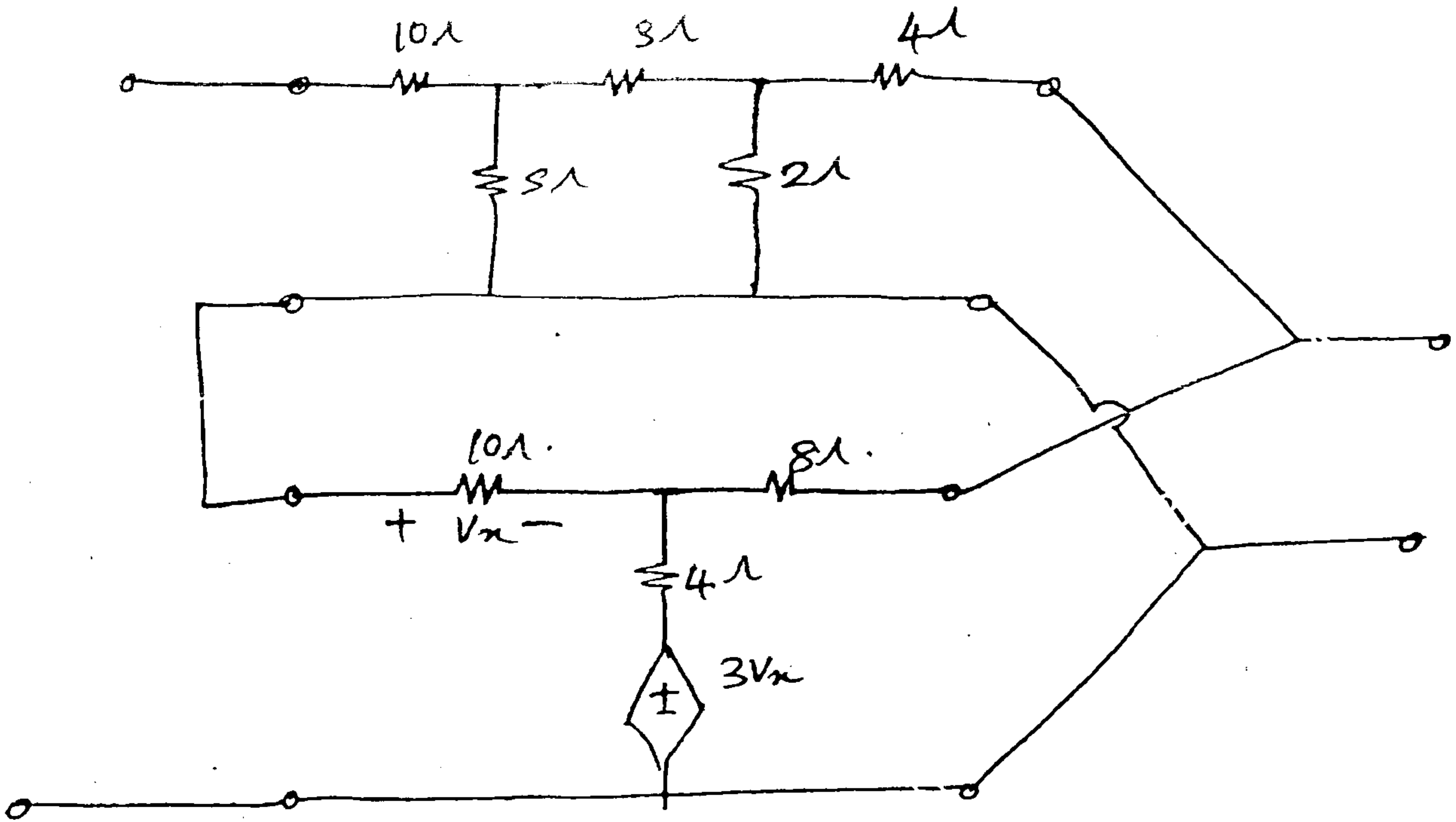

(b) Obtain $v(t)$ for $t \geq 0$ Use Laplace Transform method.

10

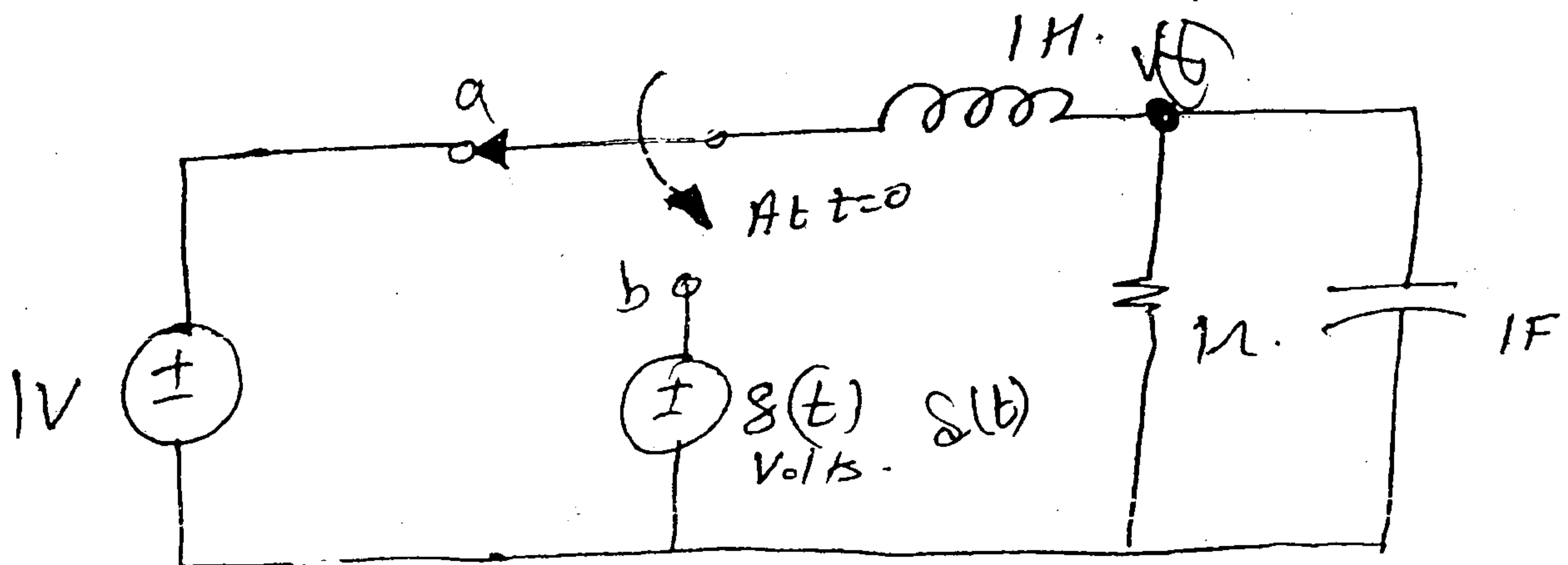


5. (a) Check for p.r.f.

8

$$a) F(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$$


$$b) F(s) = \frac{s^2 + 2s + 1}{s^3 + 2s^2 + 2s + 3}$$

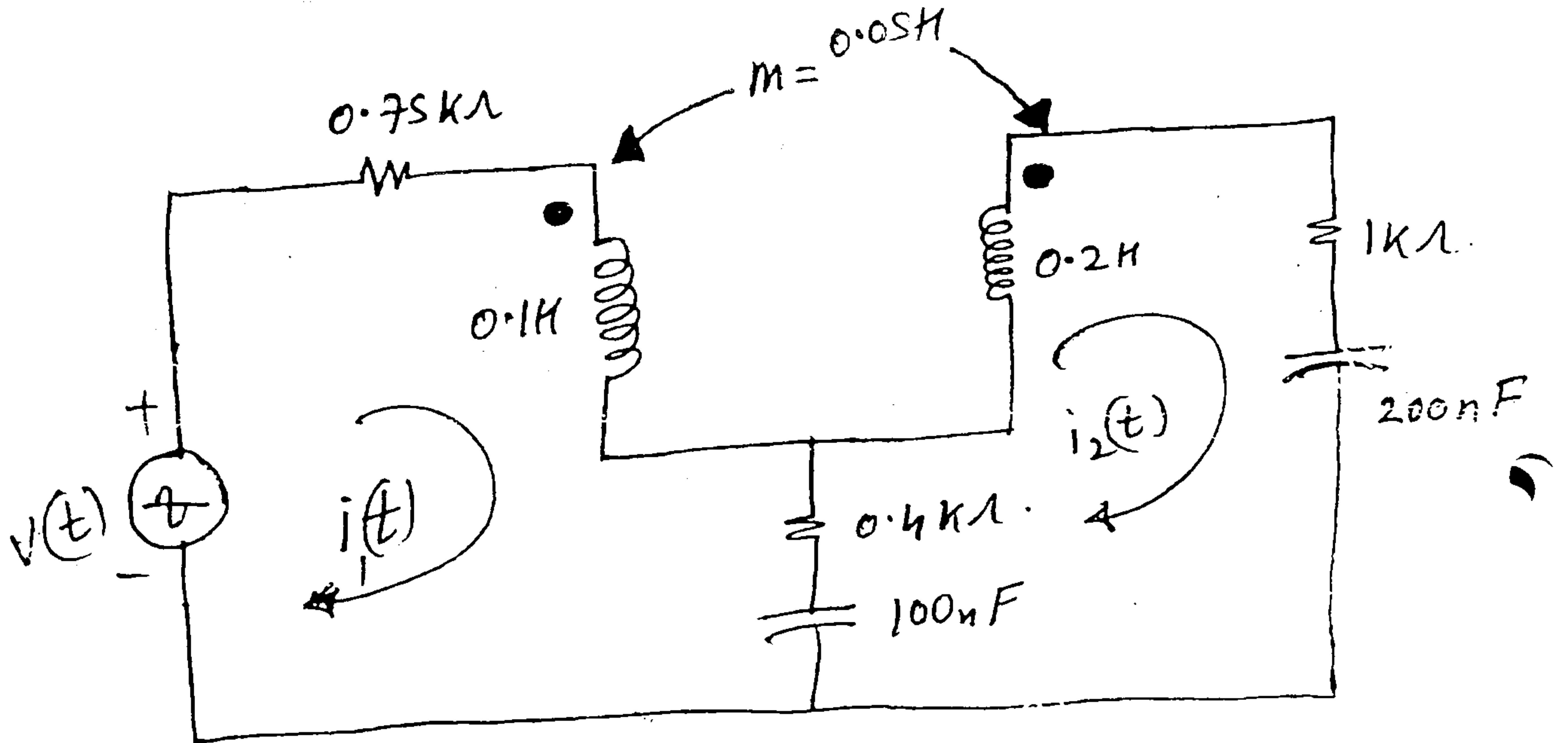- (b) Find current flowing in both coils. If applied input voltage is $v(t) = 230 \sqrt{2} \sin [5000t - 30^\circ]$




5. (C) Obtain pole-zero plot for $\frac{I_2}{I_1}$

$$2 = \frac{I_2}{I_1}$$

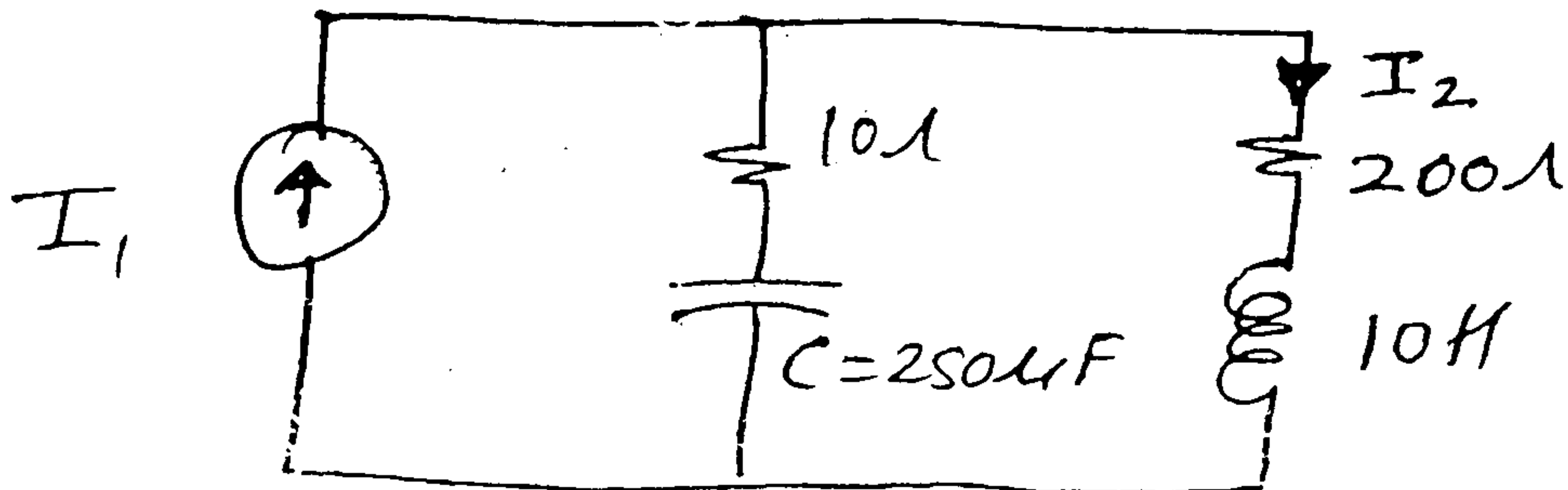


6. (a) For the Network shown below determine R_L for maximum power transfer and also determine P_L

TURN OVER

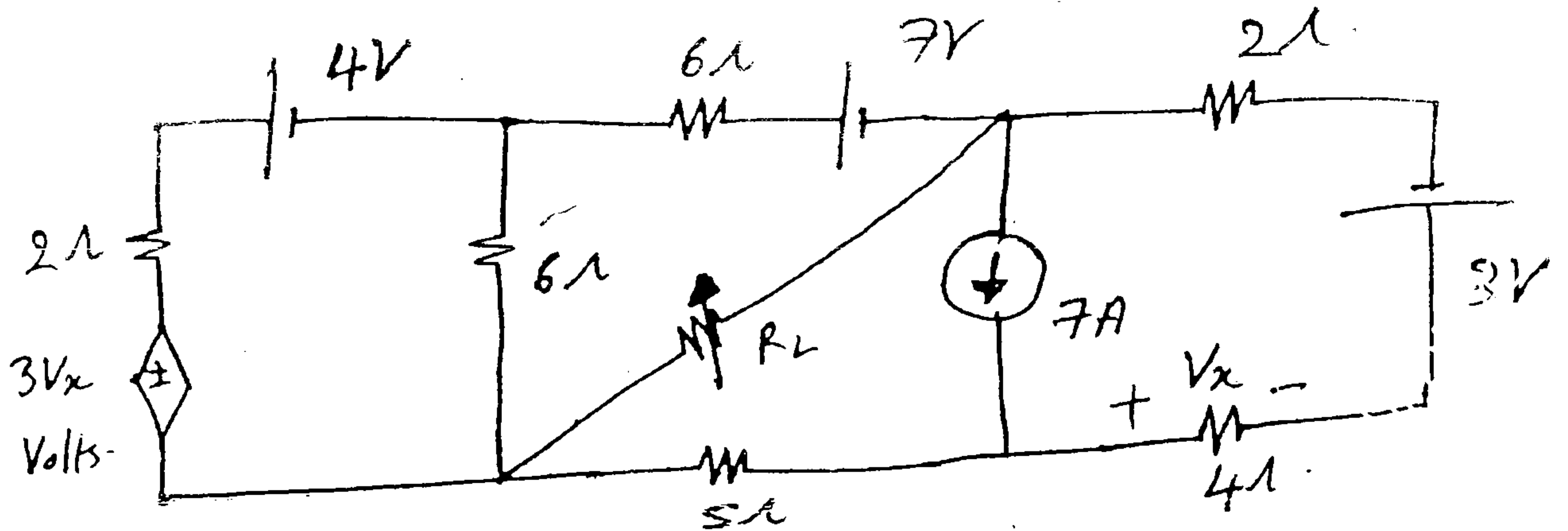

6. (b) Find $i_1(t)$, $i_2(t)$, $\frac{di_1(t)}{dt}$ and $\frac{di_2(t)}{dt}$ at $t=0^+$ if switch k is opened at $t=0$

8

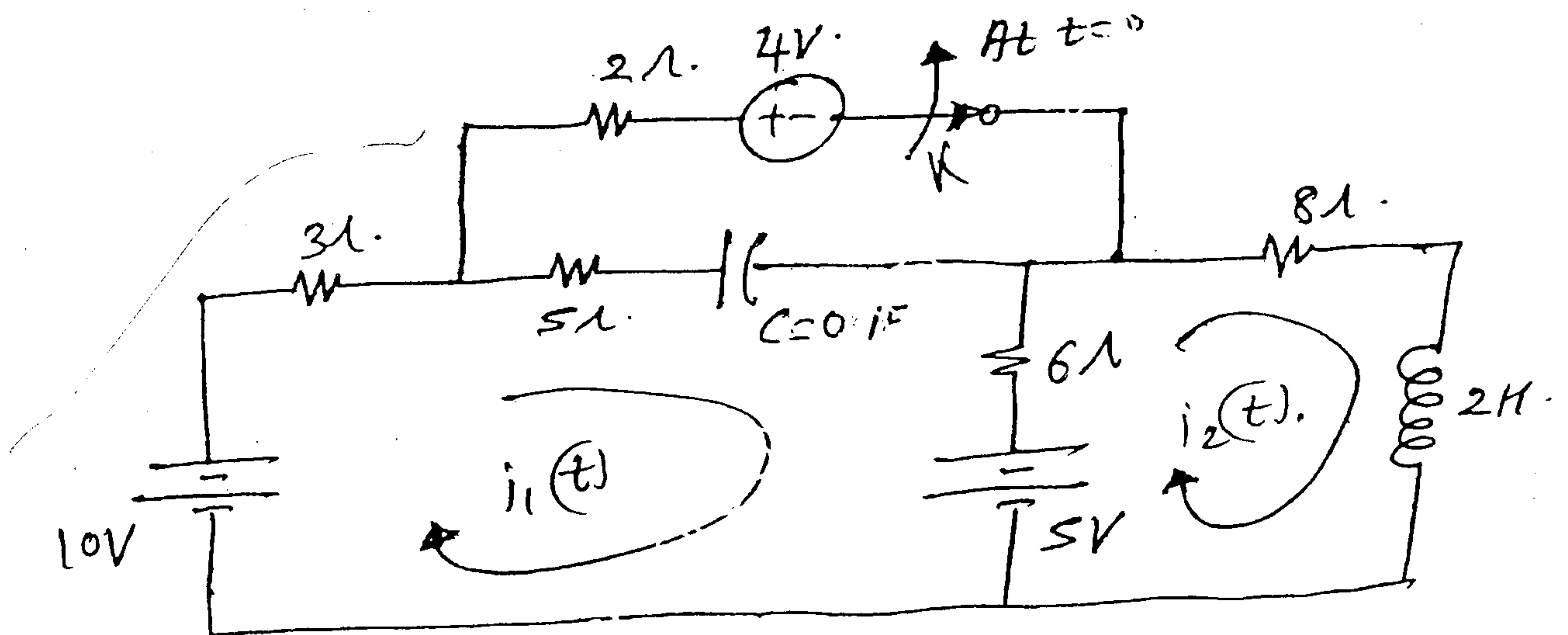

6. (c) Compare Cauer form I and Cauer form II for RC N/W

4

$$z(s) = \frac{4(s+1)(s+3)}{s(s+2)}$$