


QP Code : 4821

(3 Hours)


[ Total Marks : 80

- N. B. : (1) Question No. 1 is compulsory.  
 (2) Attempt any **three** questions from remaining.  
 (3) **Figures** to the **right** indicate **full** marks.  
 (4) Assume suitable data if required.  
 (5) Use smith chart for transmission line problem.

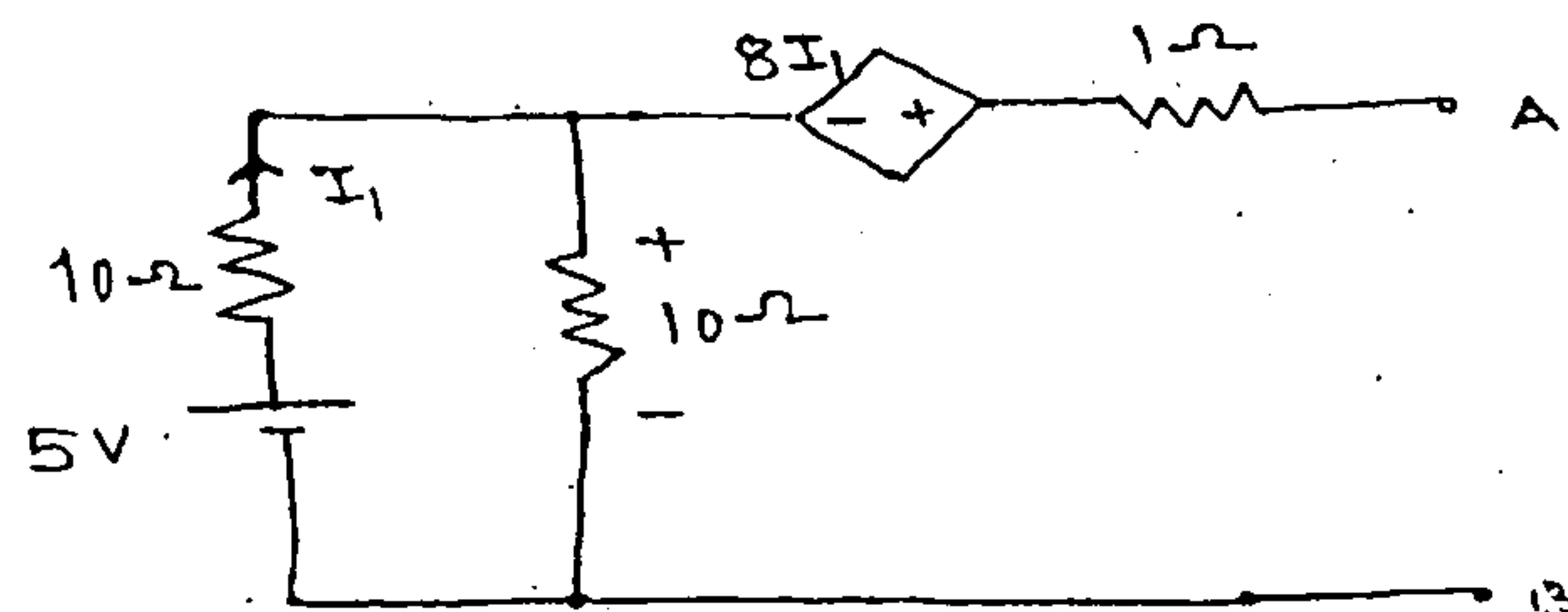1. (a) Find the thevenin's equivalent network for terminals A and B. 4




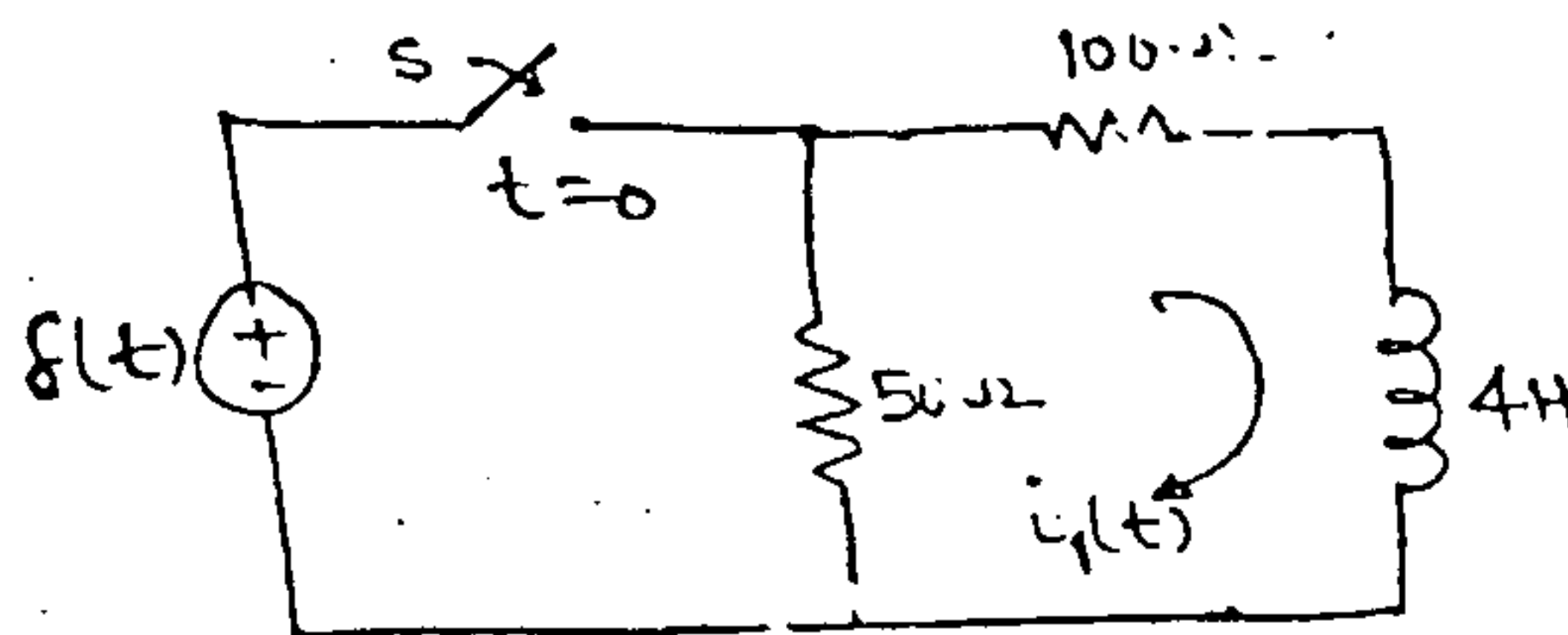- (b) For the network shown, the switch is closed at  $t = 0$ . Find the current  $i_1(t)$  for  $t > 0$  4




- (c) State the condition for reciprocity of h-parameter and prove it. 4  
 (d) Obtain S-domain equivalent circuit of an inductor and capacitor having non-zero initial conditions. 4  
 (e) What are scattering parameters. State their properties. 4

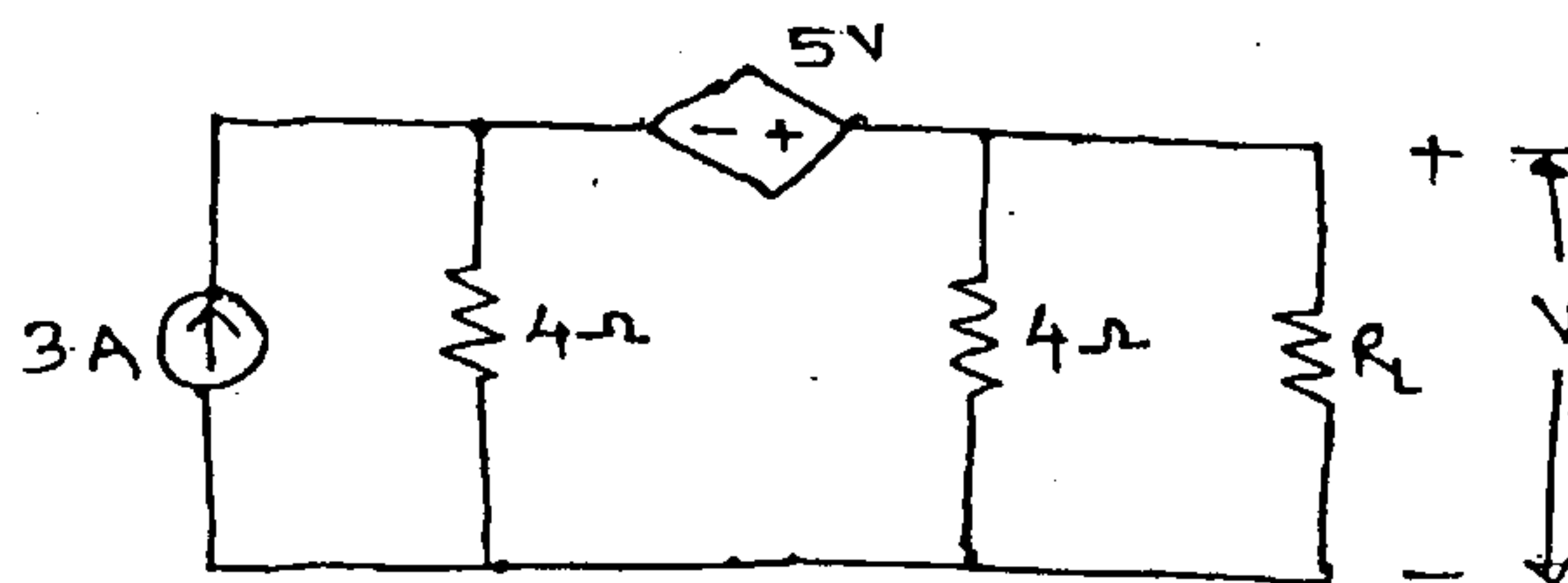2. (a) In the given network, what will be the  $R_L$  to get maximum power delivered to it. Calculate power. 8



[ TURN OVER

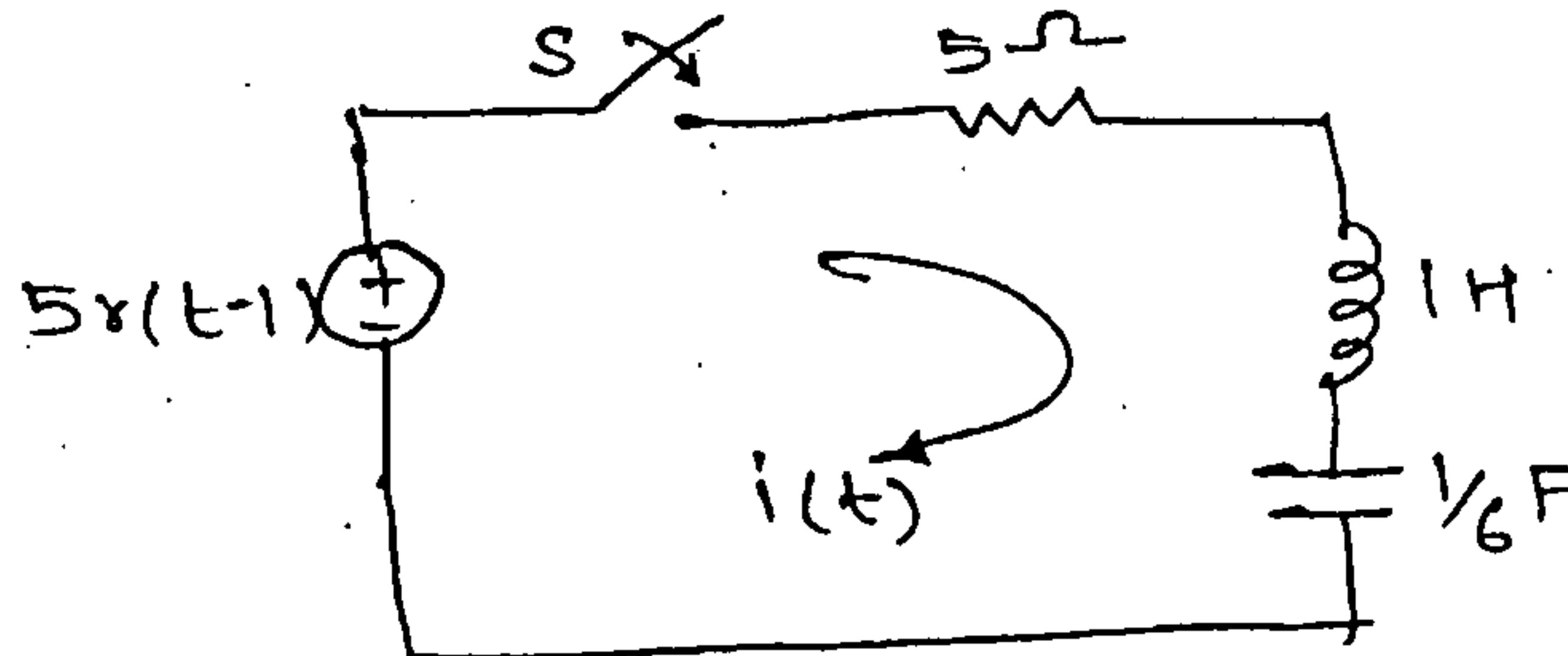- (b) For the network shown, determine the current  $i(t)$  when the switch is closed at  $t = 0$  with zero initial conditions. 8



- (c) List the types of damping in series R-L-C circuit and mention the condition for each damping. 4
3. (a) Design a single stub match for a load of  $(150 + j232.5) \Omega$  for  $75\Omega$  transmission line at 500 MHz using smith chart. 8
- (b) Define T-parameters and relate them to other parameter as indicated. 6
- (i) A and C in terms of z-parameters
- (ii) B in terms of y-parameter
- (c) Compare Foster form-I and Foster form-II of an L.C. network. 6

$$Z(s) = \frac{6s(s^2 + 4)}{(s^2 + 1)(s^2 + 64)}$$

4. (a) Check the positive real functions – 8


(i)  $F(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$  and

(ii)  $F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$


- (b) Derive an expression for characteristic equation of a transmission line. Also obtain  $\alpha$ ,  $\beta$  and  $\gamma$  of the line. 8
- (c) What are standing waves. Define reflection coefficient and V.S.W.R. of a transmission line. 4
5. (a) Test whether the following polynomials are Hurwitz, use continuous fraction expansion 10
- (i)  $s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$
- (ii)  $s^4 + 2s^2 + 2$

[ TURN OVER

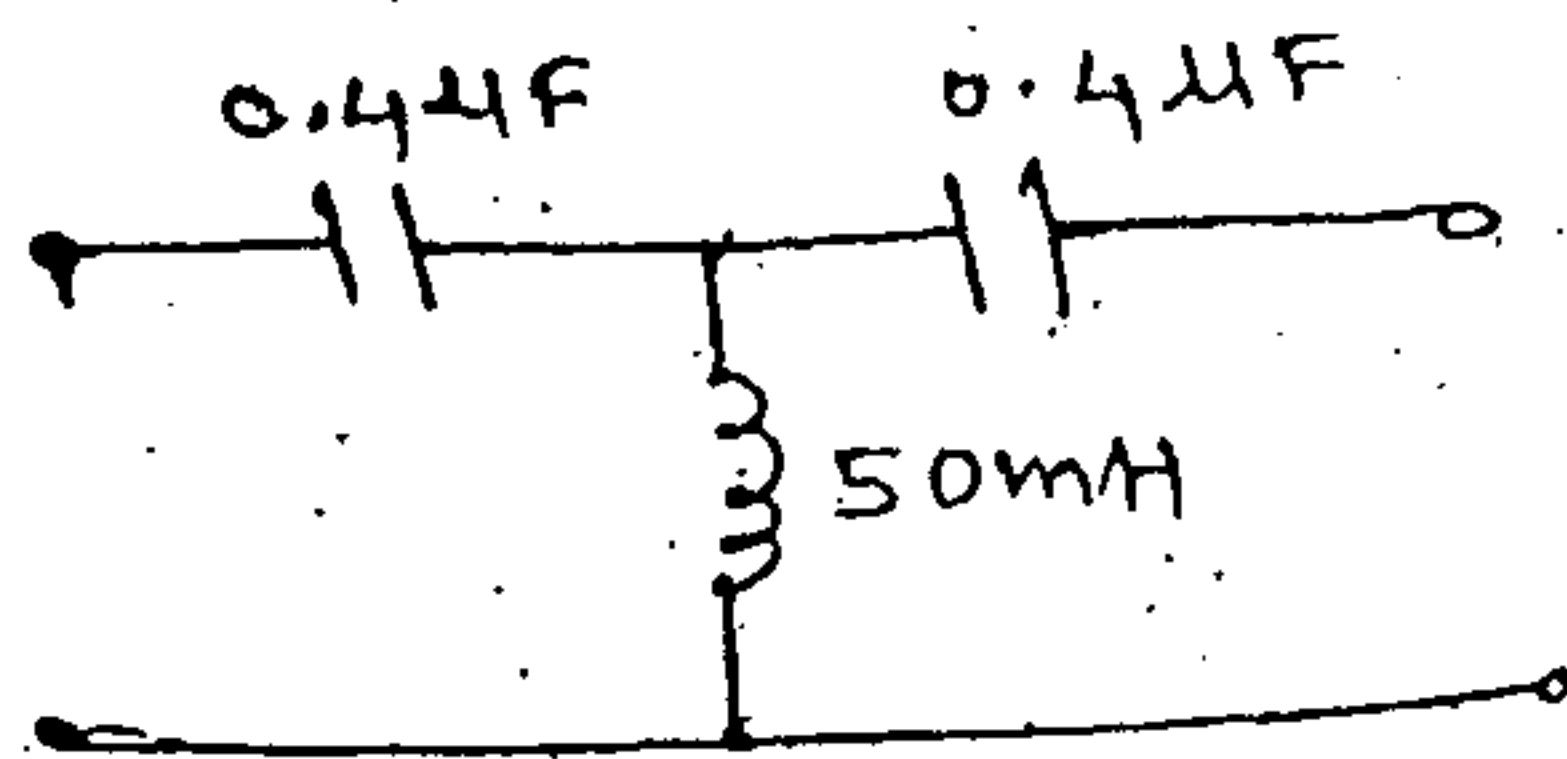
- (b) Find the characteristic impedances, cut off frequency and passband frequency for given network. 5



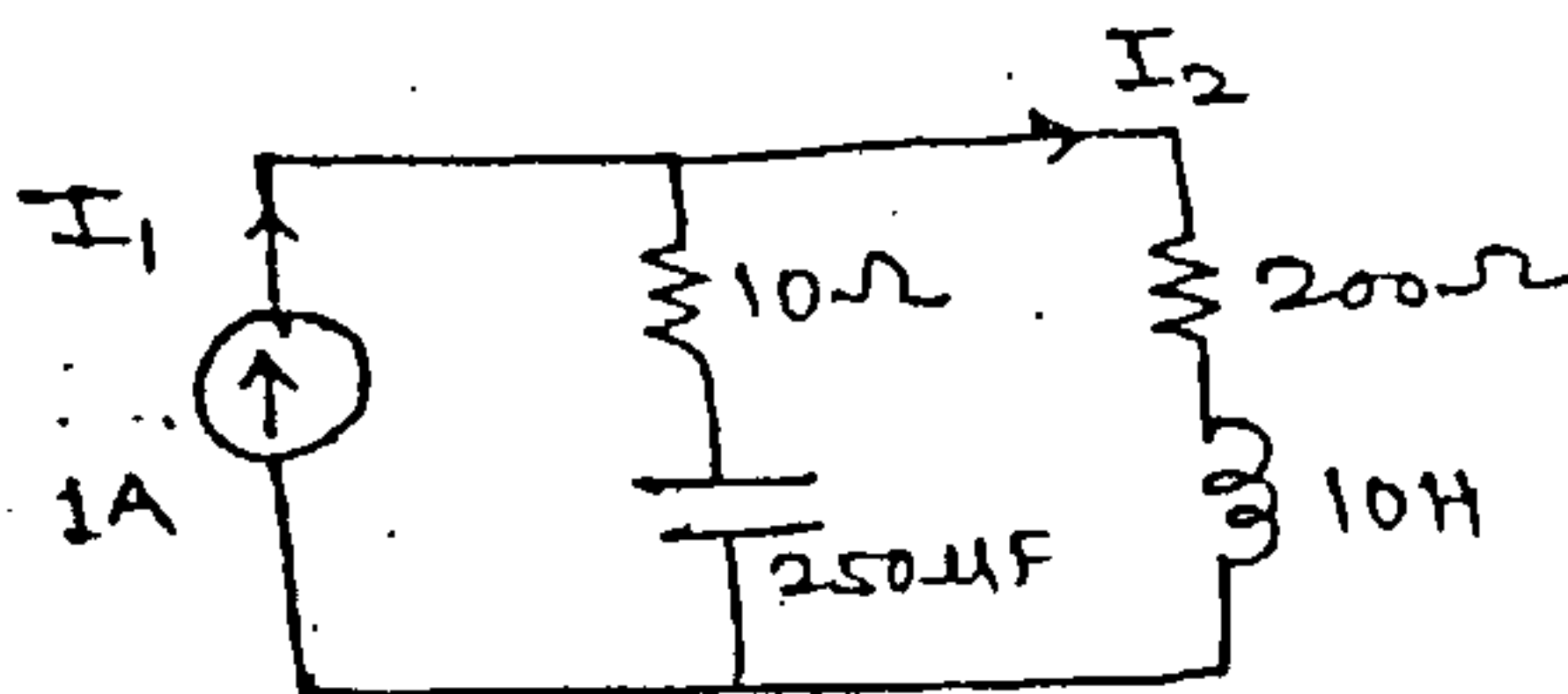
- (c) Obtain pole-zero plot for  $I_2/I_1$  5



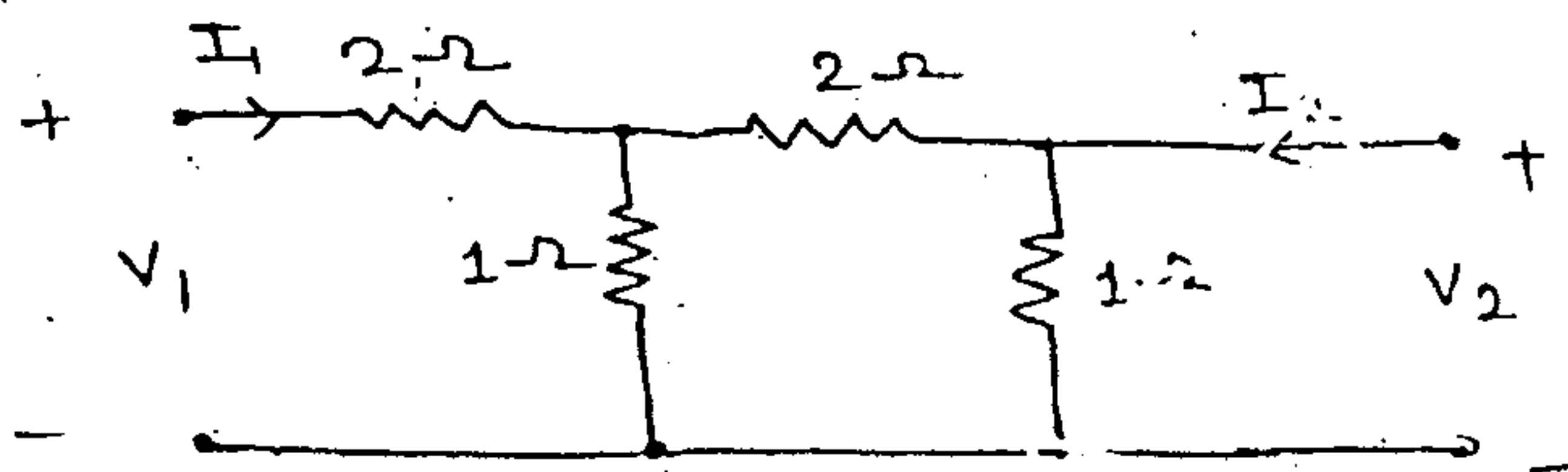6. (a) Two identical sections of the network shown are connected in cascade manner. Obtain the transmission line parameters of over all connection. 8



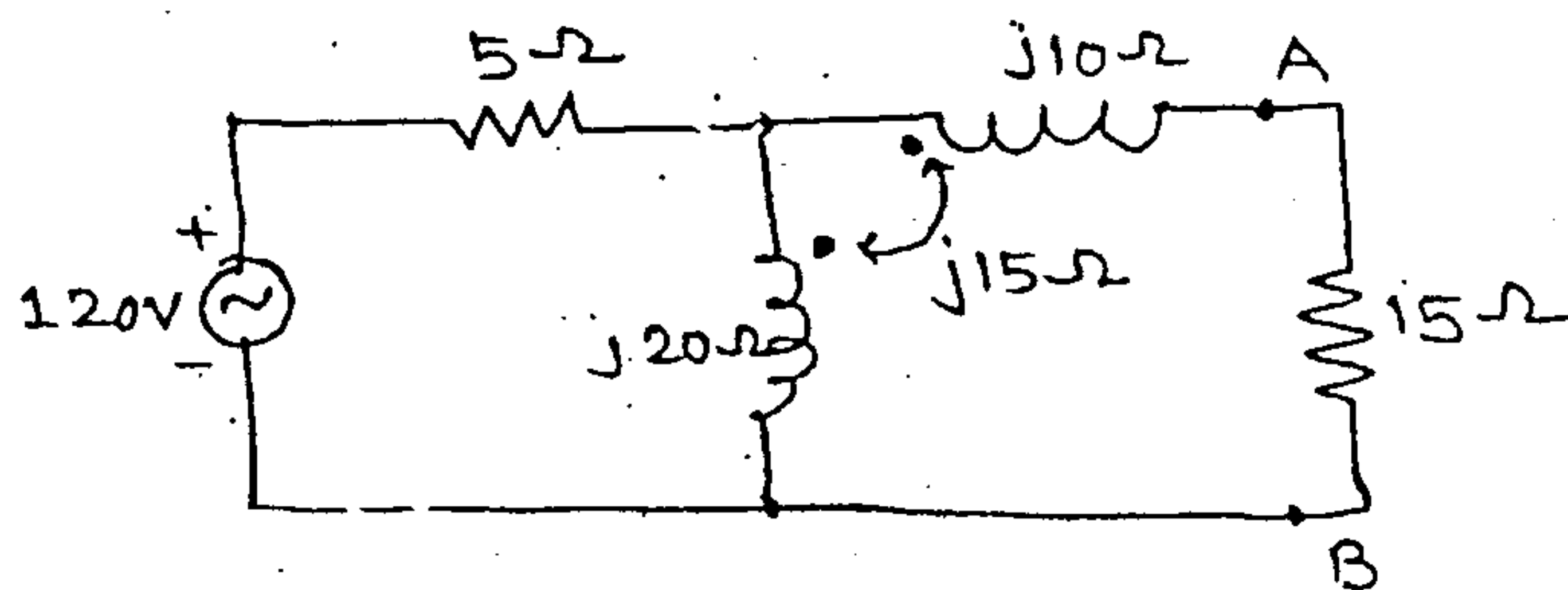- (b) Find the current through 15-Ω resistor 6



- (c) Compare Cauer form - I and Cauer form - II of RC Network 6

$$Z(s) = \frac{3(s+2)(s+6)}{s(s+4)}$$