

Q.P. Code :13161

[Time: Three Hours]

[Marks:80]

Please check whether you have got the right question paper.

- N.B:
1. Question.No.1 is compulsory.
 2. Solve any three questions from the remaining.
 3. Assume suitable data if necessary.
 4. Figures to the right indicate full marks.

- Q.1**
- a) Compare integrator & differentiator. 05
 - b) Define input offset voltage, output offset voltage, input bias current & input offset current for op-amp. 05
 - c) Explain any five specifications of the digital to analog converter (DAC). 05
 - d) Describe the basic block diagram of the phase locked Loop (PLL). 05
- Q.2**
- a) Derive the expression of inverting & the non-inverting amplifier using op-amp (A_v) & design them both for $|A_v|=10$ 10
 - b) Derive the output voltage (V_o) expression of op-amp three input averaging circuit. 10
- Q.3**
- a) Design 2nd order KRC Low pass filter (LPF) for cut-off frequency $f_o=10$ kHz with quality factor (Q) of 5. 10
 - b) Design 1st order high pass filter for a cut-off frequency $f_o=2$ kHz with unity gain. How will you modify the design to achieve low pass filter (LPF) operation? 10
- Q.4**
- a) Describe the parallel comparator/ flash type analog to digital convertor (ADC) with a neat diagram. 10
 - b) Explain the operation of inverting Schmitt Trigger with neat diagram, input & output waveforms with transfer characteristics. 10
- Q.5**
- a) Design Monostable multivibrator using IC 555 to generate a time delay of $T=500$ ms. Assume $+V_{cc}=10V$. 10
 - b) Design a positive voltage regulator to generate $V_o=+5V$ with $I_o = 50mA$ by using IC LM 723. Draw neat diagram of the designed circuit. 10
- Q.6** Write short notes on (any four):-
- a) 3 stage R-C phase shift oscillator using op-amp.
 - b) Triangular waveform generator using op-amp.
 - c) Precision Rectifier using op-amp.
 - d) Log-Antilog amplifier using op-amp.
 - e) Voltage controlled oscillator (VCO)
-