


[Time: 3 Hours]

[Total Marks: 80]

Note: 1) Question ONE is compulsory

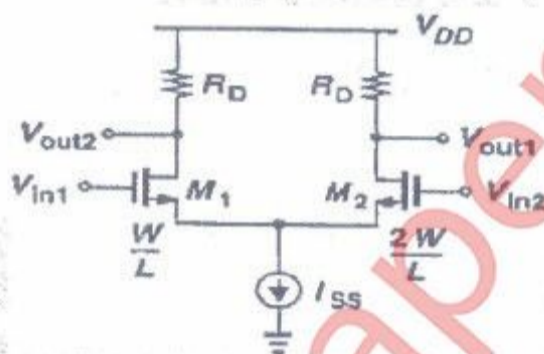- 2) Solve any THREE out of remaining questions
- 3) Draw neat and clean diagrams, wherever necessary
- 4) Assume suitable data, if required

- 1 (a) Analyze following circuit to get voltage gain equation if M_2 is twice wide as that of M_1 and $V_{in1}=V_{in2}$ 5



- (b) Explain importance of Miller Theorem 5
 - (c) Explain input output characteristics of phase detector (PD) circuit 5
 - (d) Draw and explain AMS design flow 5
- 2 (a) Derive expression for Voltage gain A_v and output resistance R_o of Source follower stage. 10
- (b) Explain in detail how to generate temperature independent references. 10
- 3 (a) Explain qualitative analysis of differential pair. 10
- (b) Explain concept of switched capacitor circuits and hence explain switched capacitor amplifiers in detail 10
- 4 (a) Explain common mode response of differential pair with necessary derivations 10
- (b) Explain White & Flicker noise in MOSFET. Derive equation for output and input referred noise voltage of CS stage 10

TURN OVER

- 5 Design two stage Operational Transconductance Amplifier (OTA) to meet following specifications- 20
- $A_v > 4000 \text{ V/V}$, $V_{DD} = 2.5\text{V}$, $V_{SS} = -2.5\text{V}$ $\text{GBW} = 6\text{MHz}$, $C_L = 10\text{pF}$,
 $\text{SR} > 10\text{V}/\mu\text{s}$, 60° phase margin, $-2\text{V} \leq V_{\text{out range}} \leq 2\text{V}$.
 $\text{ICMR} = -1.125\text{V to } 2\text{V}$, $P_{\text{diss}} \leq 2.5\text{mW}$
- Use, $K_N = 110\mu\text{A}/\text{V}^2$, $K_P = 50\mu\text{A}/\text{V}^2$, $V_{TN} = |V_{TP}| = 0.7\text{V}$, $\lambda_N = 0.04\text{V}^{-1}$,
 $\lambda_P = 0.05\text{V}^{-1}$, $C_{ox} = 2.47\text{fF}/\mu\text{m}^2$. Verify that the designed circuit meets required Voltage Gain and Power Dissipation specifications.
- 6 (a) Give comparison between Full-custom and Semi-custom design 5
 (b) Compare various opamp topologies 5
 (c) Explain in detail charge pump PLL 5
 (d) Write a short note on Gilbert Cell 5

muquestionpapers.com