

(3 Hours)

[Total Marks : 80

- N.B. : (1) Attempt questions No. 1 and any 3 from remaining questions. In all 4 questions are to be attempted.
 (2) All sub-questions of the same question should be answered at one place only in their serial orders, and not scattered.
 (3) Assume suitable data with justification if missing.

1. (a) Determine Y - parameters for the network shown in fig 1 (a)

5

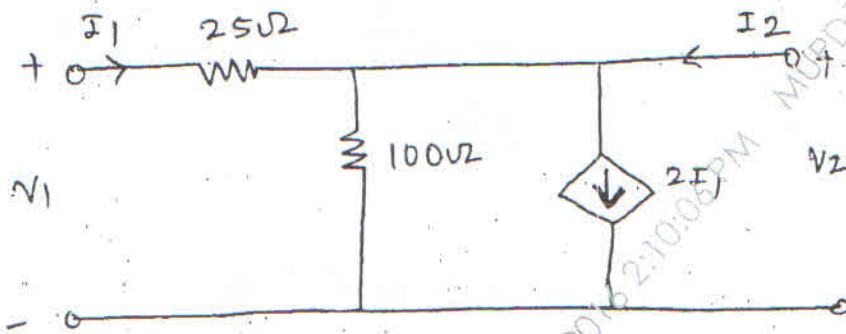


Fig 1 (a)

- (b) Test if $F(s) = S^4 + S^3 + 5S^2 + 3S + 4$ is a Hurwitz polynomial. 5
 (c) Two coils connected in series have self inductance 80 mH & 20 mH respectively. The total inductance of the circuit is found to 140 mH. Determine the 5
 (i) mutual inductance between two coils and
 (ii) The coefficient of coupling
 (d) Synthesize the following function into a network. 5

$$z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1} \text{ using cauer-1 form.}$$

[TURN OVER]

2. (a) Find the Thevenin's equivalent across the terminals XY for the circuit shown in fig 2 (a) 10

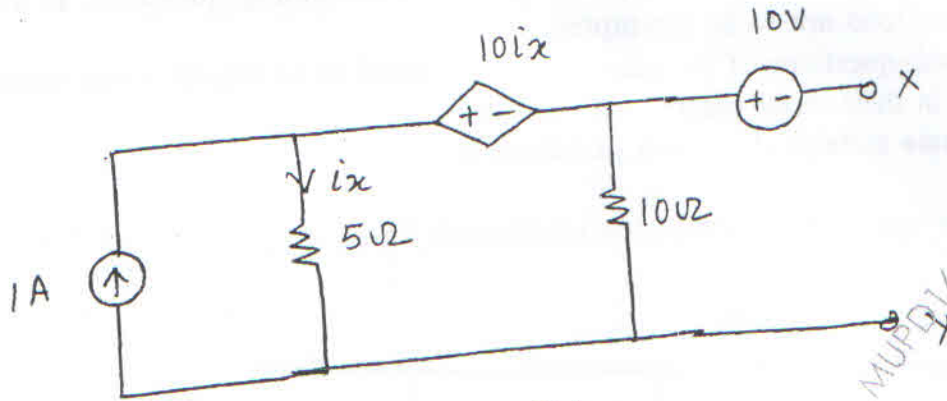


Fig 2(a)

- (b) Determine the node voltage at node (1) & (2) of the Network Shown in fig 2(b) by using nodal analysis. 5

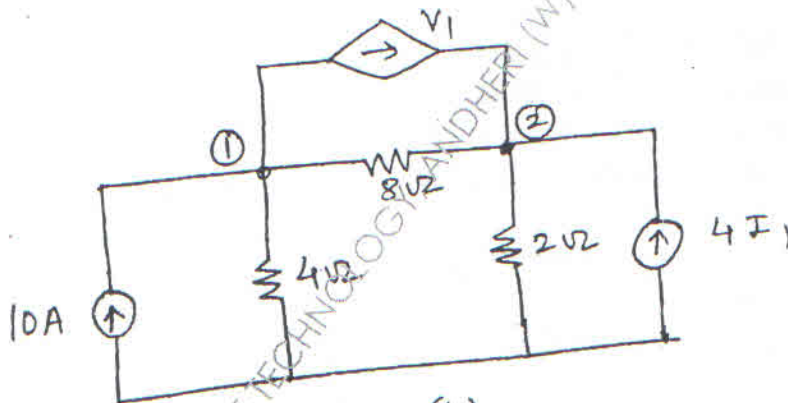


Fig 2(b)

- (c) Test Whether

$$F(s) = \frac{s(s+3)(s+5)}{(s+1)(s+4)}$$

is a positive real function.

[TURN OVER]

3. (a) Synthesize the driving point function using Foster -I and Foster -II form.

10

$$z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

(b) State and prove Initial value theorem.

(c) A Transmission line has distributed parameters $R=6$ Ohms / km, $L= 2.2$ mH/km

$C=0.005 \mu F / km$ & $G = 0.005 \mu mho/km$

Determine characteristics impedance and propagation constant at 1KHz frequency.

4. (a) Find ABCD parameters for the two port Network shown in fig 4 (a).

10

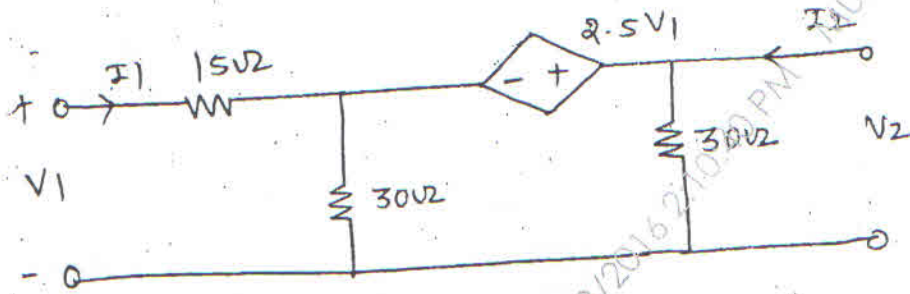


Fig 4(a)

- (b) Find the Network functions $\frac{V_1}{I_1}, \frac{V_2}{I_1}, \frac{V_2}{V_1}$ for the network shown in fig 4 (b)

5

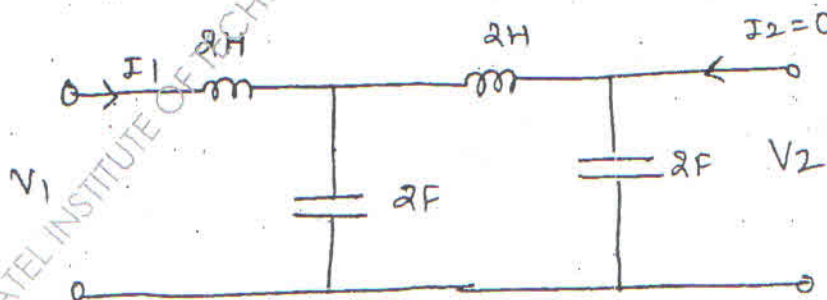


Fig 4(b)

[TURN OVER]

- (c) A Transmission line has a characteristics impedance of $50 + j 100 \Omega$ and is terminated in a load impedance of $73 - j 42.5 \Omega$. Calculate
- The reflection coefficient.
 - The standing wave ratio

5. (a) The Network shown in fig 5 (a), switch K is closed at $t = 0$, Assume all initial conditions as zero. Find i , $\frac{di}{dt}$ & $\frac{d^2i}{dt^2}$ at $t = 0^+$

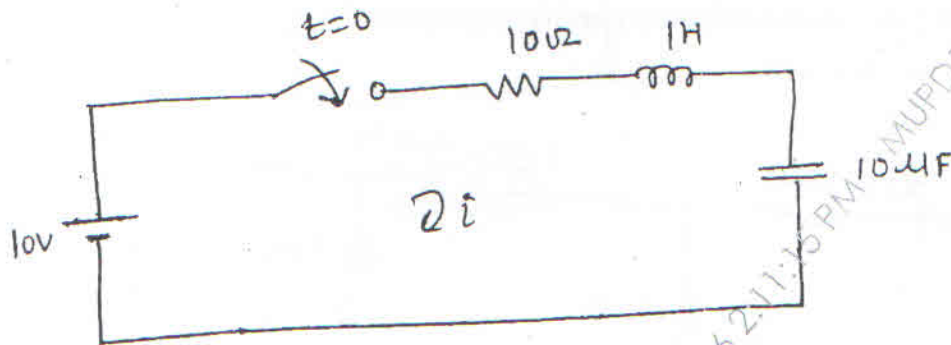


Fig 5(a)

- (b) Write the KVL equations in standard form for the N/W shown in fig 5(b)


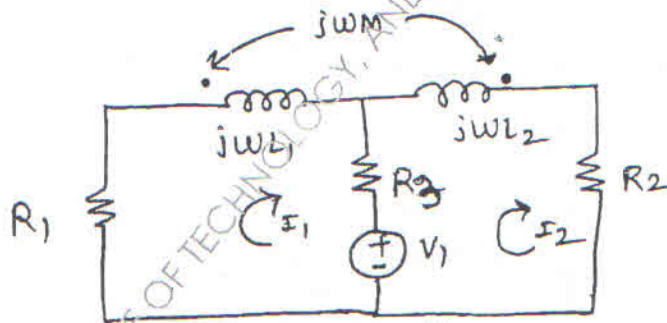


Fig 5(b)

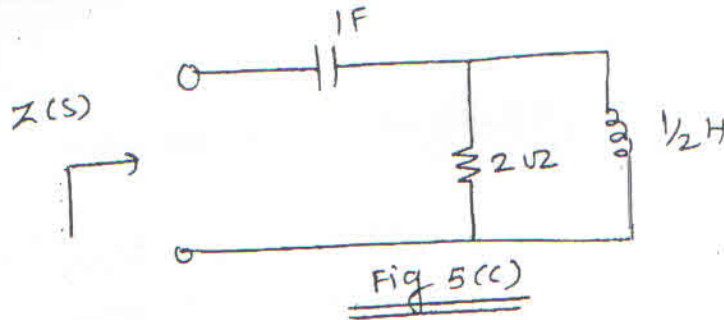(c) Find poles and zero of the Impedance $Z(s)$ for the Network Shown in fig 5 (c) 5



6. (a) Why is the Impedance matching required? Draw the following normalized quantities on the smith chart. 10

(i) $(3+i3) \Omega$

(ii) $(1.0) \Omega$

(iii) $(2-j1) \Omega$

(i) $j 1.0 \Omega$

(b) Write short note on :

Time domain analysis using Laplace Transform. 5

(c) Define the following terms 5

- (i) Phase Velocity
- (ii) Characteristic impedance
- (iii) Reflection coefficients