


- N.B. : (1) Question No. 1 is compulsory.
 (2) Solve any three questions from the remaining questions.
 (3) Assume & mention suitable data, if required.
 (4) Figures to the right indicate full marks.




20

1. Solve any four :


(a) Find I_1 for the given circuit.

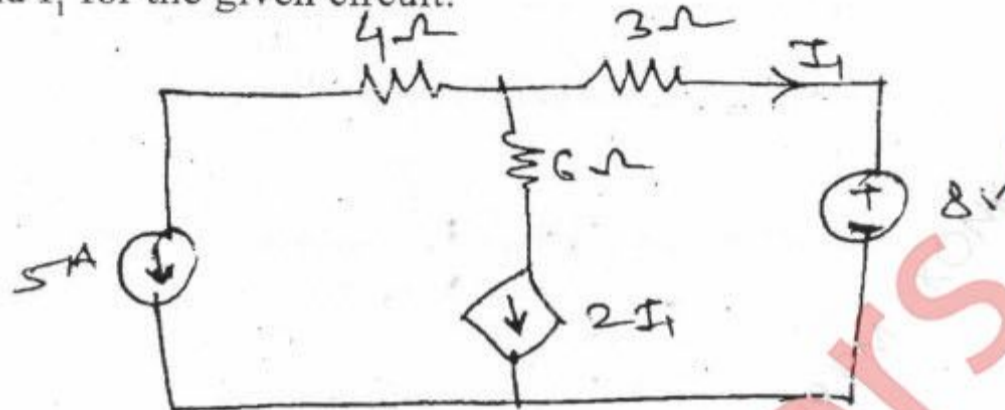


(b) Find I_x by superposition theorem

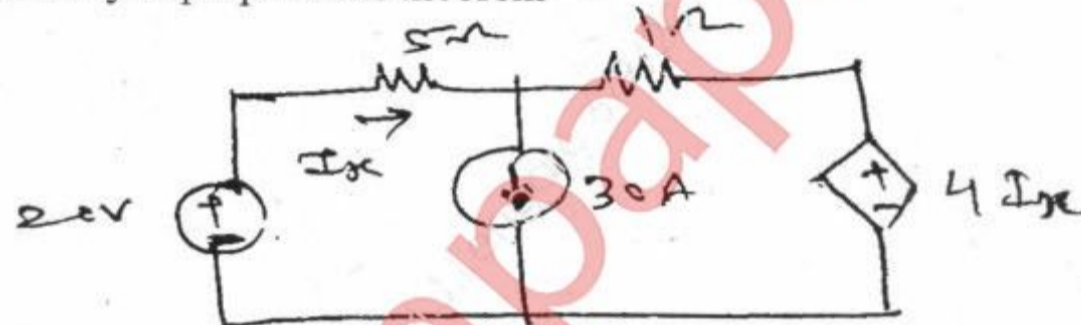

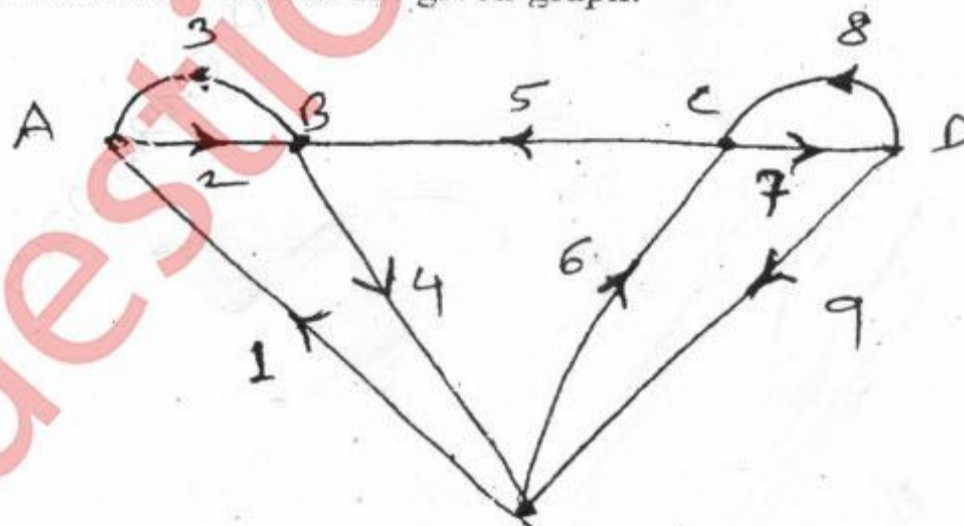(c) Find Incidence matrix for given graph.




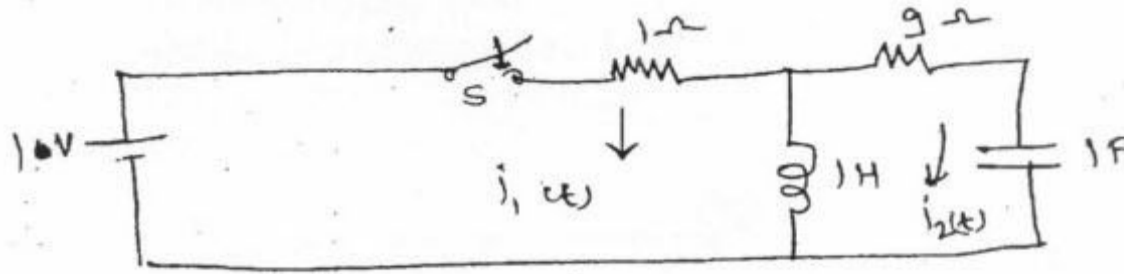(d) Find $i_1(0^+)$ & $i_2(0^+)$ for given circuit. Switch is closed at $t = 0$




(e) What are the properties of a positive real function?

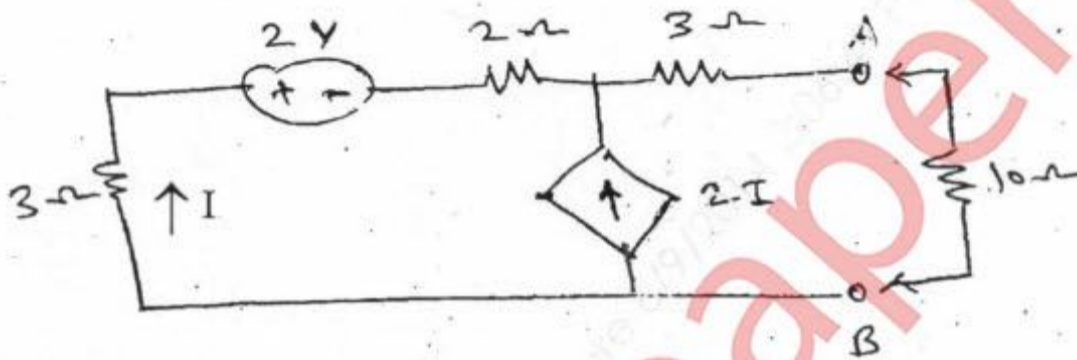
2. (a) Find the Norton's equivalent circuit across terminals A-B, for the given circuit. Also find current through $10\ \Omega$ resistor. 10




(b) Find I_2 by mesh analysis 10

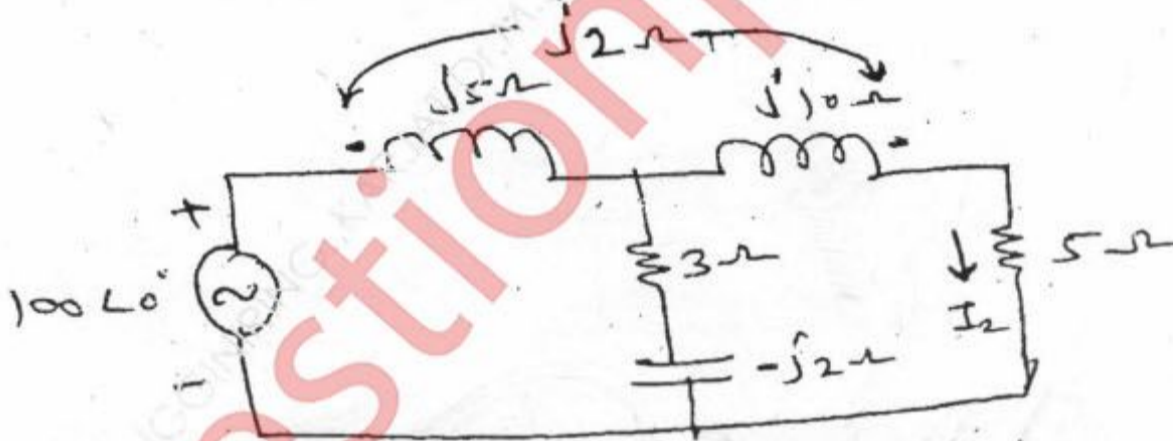

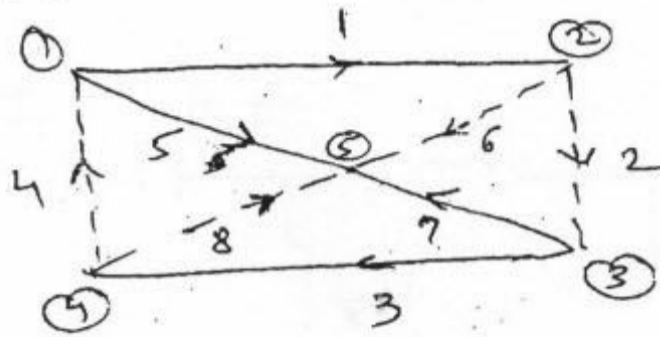
3. (a) Write 10
 (i) Incidence matrix [Aa]
 (ii) Reduced Incidence matrix [A]
 (iii) Tieset matrix
 for the graph shown below



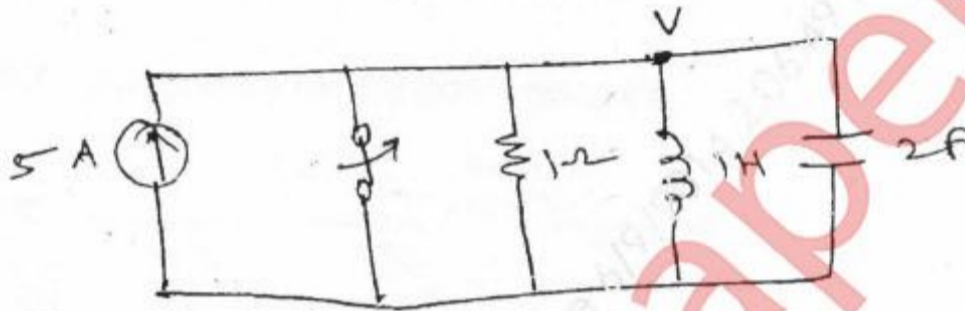
- (b) find V , $\frac{dV}{dt}$, $\frac{d^2V}{dt^2}$ for given circuit. if switch is opened at $t=0$. 10



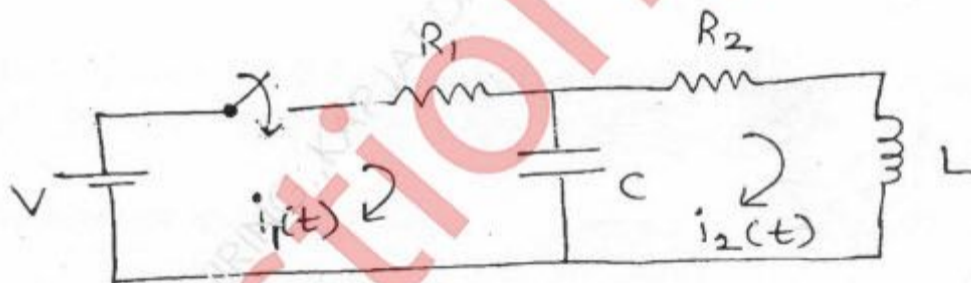4. (a) For the network shown below assume all the initial conditions to be zero. 10
 Find $i_1(0^+)$, $i_2(0^+)$, $\frac{di_1}{dt}(0^+)$, $\frac{di_2}{dt}(0^+)$ and $\frac{d^2i_1}{dt^2}(0^+)$.




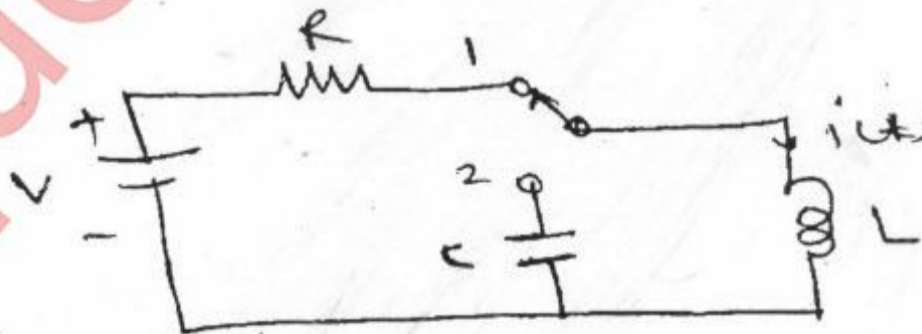- (b) The given network has reached steady state when switch is in position 1. 10
 At time $t=0$ switch is moved from position 1 to position 2. Determine $i(t)$




5. (a) Find the network functions $\frac{V_2}{V_1}$, $\frac{V_1}{I_1}$ and $\frac{V_2}{I_1}$ for the network shown below :-

10

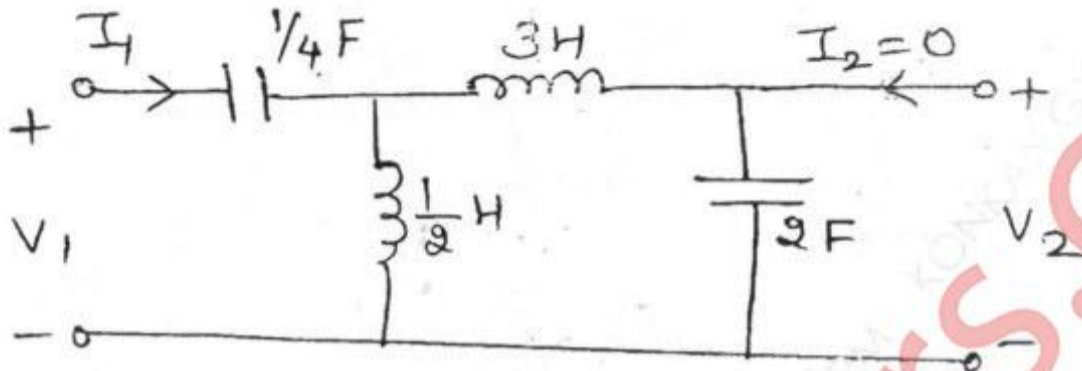

10

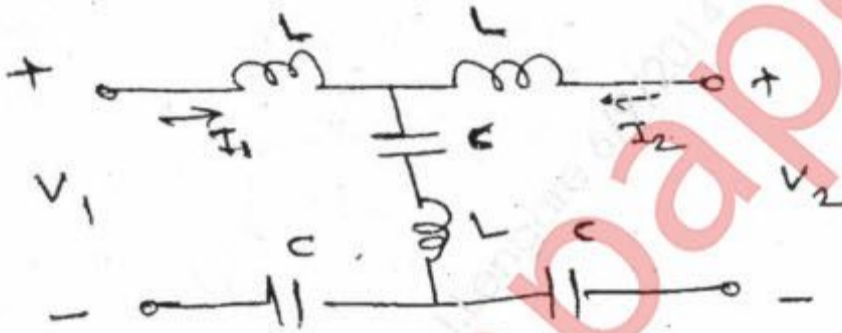- (b) Find Z - parameters for the given network.



10

6. (a) Test whether the following polynomial is Hurwitz or not $s^7 + 3s^6 + 8s^5 + 15s^4 + 17s^3 + 12s^2 + 4s$

10

- (b) Synthesize in foster II form

$$Z(s) = \frac{6s^4 + 42s^2 + 48}{s^5 + 18s^3 + 48s}$$