


Note: 1. Question no.1 is compulsory.

2. Solve any three from the remaining questions.



Q1.

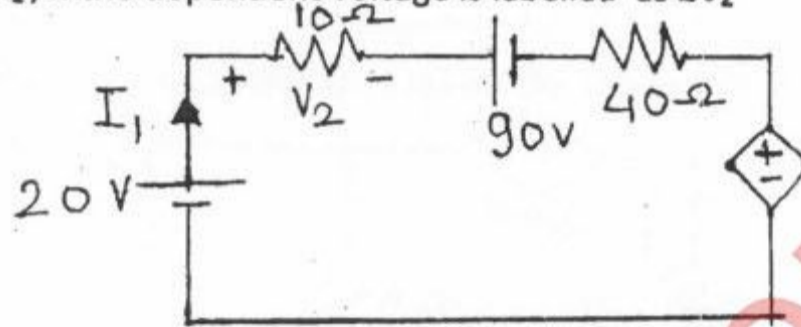
a) Find I_1 , if the dependent voltage is labelled as $2V_2$



b) Draw oriented graph for the given incidence matrix

$$A = \begin{bmatrix} -1 & 1 & 0 & -1 \\ 0 & 0 & 1 & 1 \end{bmatrix}$$

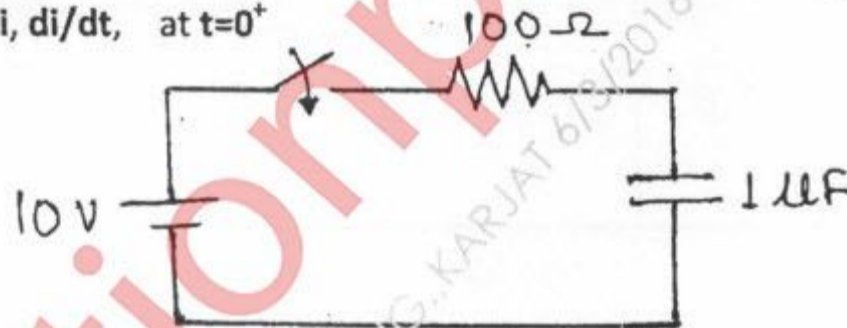c) In the network shown the switch is closed at $t=0$. With the capacitor uncharged, find value for i , di/dt , at $t=0^+$




d) Test whether the polynomial is Hurwitz

1) $P(s) = s^6 + 3s^5 + 8s^4 + 15s^3 + 17s^2 + 12s + 4$

2) $P(s) = s^8 + 5s^6 + 2s^4 + 3s^2 + 1$


Q2.

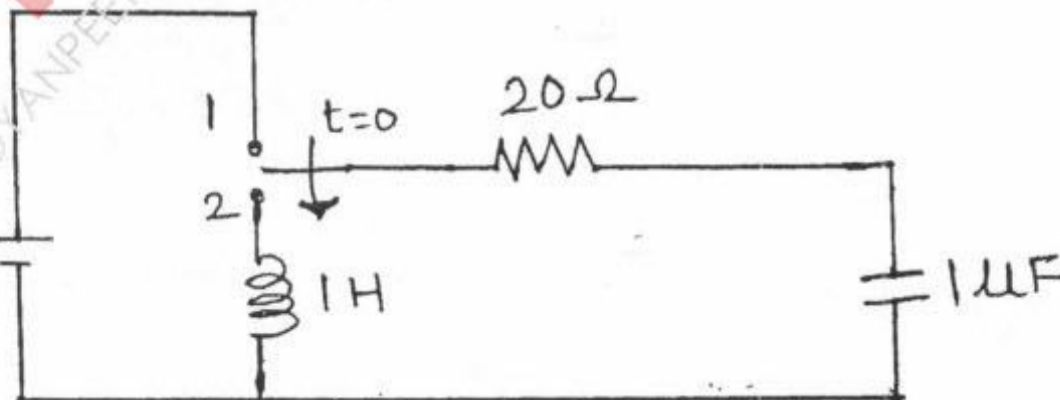a) In the network shown the switch is changed from position 1 to 2 at $t=0$. Steady state condition having reached before switching, find value for i , di/dt , & d^2i/dt^2 at $t=0^+$




[TURN OVER

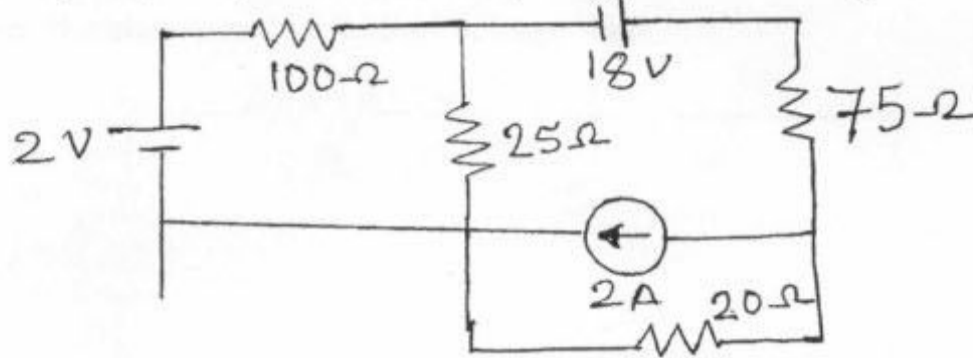b) Using the principle of network topology, find I in the fig. (10)




Q3.

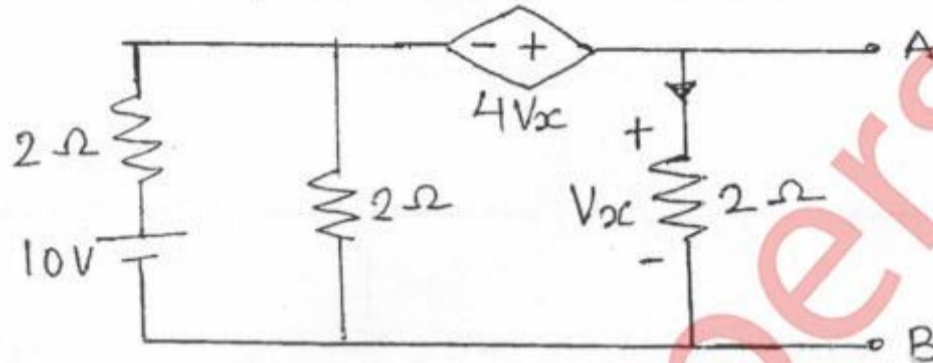a) Determine thevenin's equivalent ckt for the shown network (10)




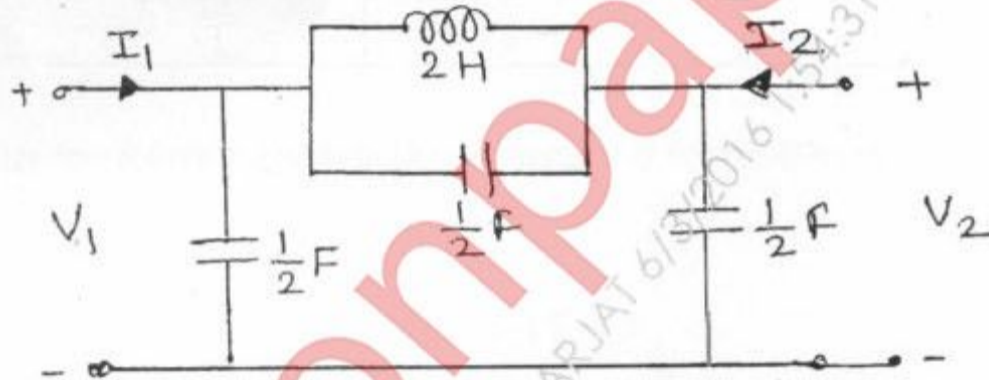b) For the network shown, determine V_2/V_1 & V_2/I_1 (10)



Q4.

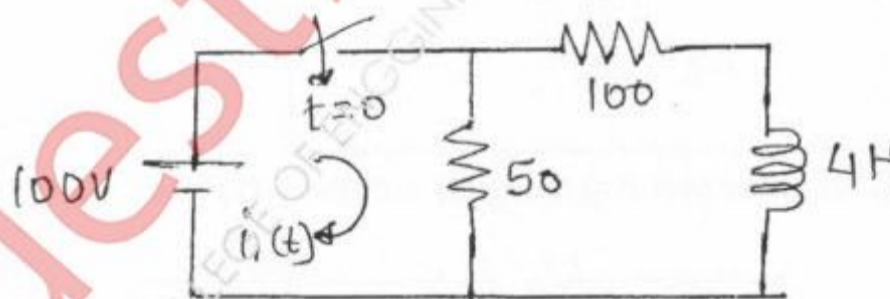a) For the shown network, switch is closed at $t=0$. Find current i_1 for $t>0$ (10)




b) Check the positive realness of the given functions (10)

- 1) $F(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$
- 2) $F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$

Q5.


a) For the shown network, find voltage V_{ab}

(10)

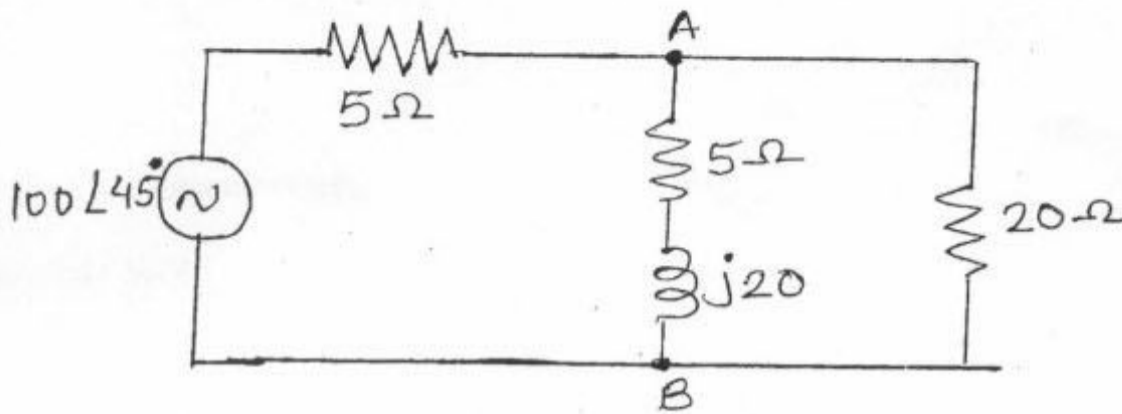

b) Determine Y parameters for the shown network. Also write Z-parameters from Y-parameters

(10)

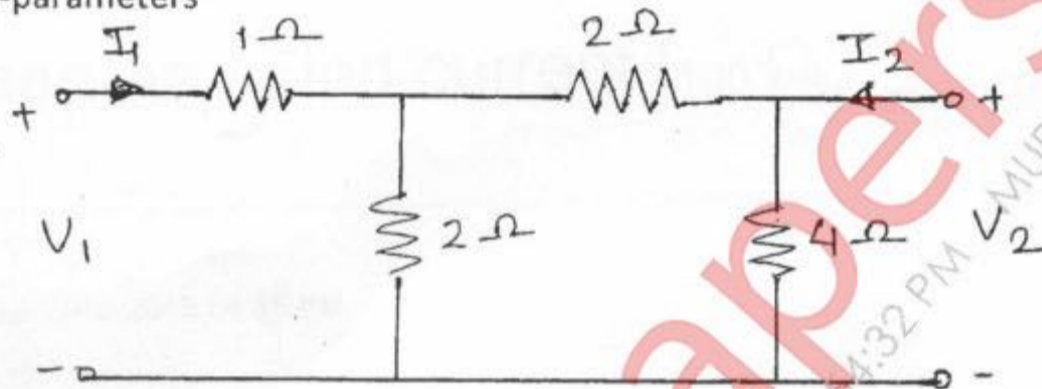

Q6.


a) Synthesize the following RL function in Foster-I & Foster-II form

(10)

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$


b) Find I_1 using mesh analysis

(5)

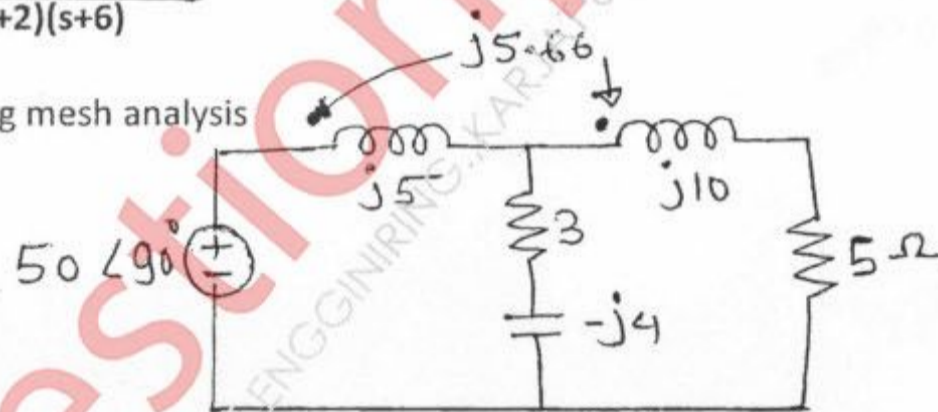

c) For the shown network, switch is closed at $t=0$. find value for i , di/dt

(5)

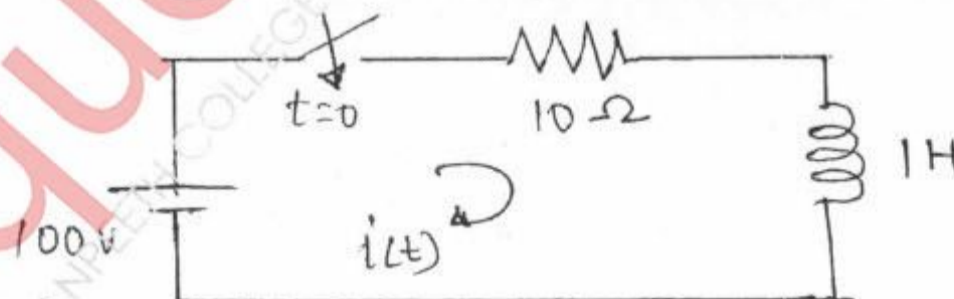

Course: SE (Instrumentation)

QP Code 30748

Correction

Q. 2(b)

Read As : Find current $I_{100 \Omega}$

Date and Time 03/06/2016 04:35 PM

muquestionpapers.com