

FNIST/SCCD/A/CBGS /03/12/16

Q.P. Code : 597600

Signal Conditioning Circuit Design

3 Hours

[Total Marks : 80

- (1) Question no. 1 is compulsory.
- (2) Attempt any three questions from remaining five questions.
- (3) Assume suitable data wherever necessary.

- Q.1. (a) Explain the significance of all pass filter. 20
- (b) Draw and explain zero crossing detector circuit.
- (c) Design a high impedance amplifier with a voltage gain of 42.
- (d) Explain the terms:
- (i) Signal Level and Bias changes
  - (ii) Filtering and impedance matching
- Q.2. (a) Draw and explain circuit diagram of absolute value circuit using op-amp. 10
- Discuss its advantages over traditional diode rectifier.
- (b) What is a multivibrator? Design astable square wave generator using IC 555 and determine timing components for frequency of 10 kHz. 10
- Q.3. (a) List the applications of instrumentation amplifier. Explain any one in detail. 10
- (b) Discuss problems associated with ideal integrator. Draw the circuit for practical integrator. Determine the output voltage for an input step (dc) voltage of 2V and  $R_1 C_f = 1$  second. Assume that the op amp is initially nulled. Sketch the input and output waveform. 10
- Q.4. (a) A sensor outputs a voltage ranging from -2.4 to -1.1V. For interface to an analog-to-digital converter, this needs to be 0 to 2.5V. Develop the required signal conditioning. 10
- (b) What are the advantages of active filters over passive filters. Design a second order low pass Butterworth filter for a high cut-off frequency of 1kHz. 10
- Q.5. (a) Draw and explain the principal and construction of metal strain gauges. What is the signal conditioning associated with it? 10
- (b) A strain gauge with  $GF = 2.03$  and  $R = 350\Omega$  is used in the bridge. The bridge resistors are  $R_1 = R_2 = 350\Omega$  and the dummy gauge has  $R = 350\Omega$ . If a tensile strain of  $1450\mu\text{m/m}$  is applied, first the bridge offset voltage if  $V_s = 10.0\text{V}$ . Find the relation between bridge off-null voltage and strain. How much voltage results from strain of 1micro? 10

[TURN OVER]

Q.6. Write short notes on any four of the following.

20

- (a) SMPS
  - (b) Data acquisition system
  - (c) Sample and hold circuit
  - (d) PLL
  - (e) Dual Slope A to D converter
  - (f) V to F converter
- 

muquestionpapers.com