



(3 Hours)

QP Code : 3513

[Total Marks : 80

- N.B. (1) Question no. 1 is compulsory.
(2) Answer any three out of remaining questions.
(3) Each question carry 20 marks.

1. Solve ^{all} any four of the following :-

- (a) Discuss the advantage of solid state relays over electromagnetic relays. 20
(b) Write the working principle of DC generator and derive emf equation for the same.
(c) Explain the block diagram of programmable logic controller.
(d) Explain the Torque-speed characteristics 3 phase Induction motor.
2. (a) Explain the working of multiplexer. Also implement the function $Y = A\bar{B} + BC$ using suitable multiplexer IC. 10
(b) Explain the SCR controlled resistance welding with suitable diagrams. 10
3. (a) Explain the Integrator and differentiator circuit using OP-amp with waveforms. 10
(b) Draw and explain the working of any ^{one} 10
(i) Counter IC
(ii) Shift register
4. (a) A 250 V shunt motor with armature resistance of 0.5Ω runs at 600 r.p.m. on full load takes an armature current of 20 A. If resistance of 1Ω is placed in the armature circuit, find the speed at (i) full load torque (ii) half full load torque. 10
(b) Explain the working principle of AC commutator motor. 10
5. (a) Explain application of SCR for speed control of DC Motor. 10
(b) A 20 kVA, 2200/220 V, 50 Hz transformer gave following test results : 10
O.C. Test : 220 V, 4.2 A, 148 W (LV side) 10
S.C. Test : 86 V, 10.5 A, 36 W (HV side)
Determine the regulation at 0.8 pf lagging and at full load.
6. Write short notes on the following (any three) :- 20
(a) Speed control of dc motor.
(b) Timer and its industrial applications.
(c) Overload protection circuits.
(d) Circuit Breaker.