## Sem VII / B. E / CBSus / Bio med / BMI- I

Q.P. Code: 613301

	(3 Hours) [ Total Marks :	80
N.B.	<ul> <li>(1) Question No.1 is compulsory.</li> <li>(2) Answer any three questions out of remaining five questions.</li> <li>(3) Figure to the right indicate full marks</li> </ul>	
1.(a) (b)	Draw and explain blood leak detector circuit used in Hemodialysis Explain using suitable waveform what is Atrial and Ventricular fibrillation. Explain how will you correct it.	5
(c) (d)	Explain the ICHD codes.	5
2 (a) (b)	Draw and Explain the block diagram of Hemodialysis machine.  Explain any one type of LASER used in medical application.	10 10
	Explain in detail with the help of a circuit diagram, the working of Ultrasonic therapy Unit along with its specifications  Explain in detail with the help of a circuit diagram, the working of short wave diathermy Unit along with its specifications	10 10
	Explain various modes of operation in electrosurgical unit. Also draw various electrodes used.  Explain using circuit diagram BICOAG modes of operation in solid state surgical diathemy.	10 10
5 (a) (b)	Draw the circuit diagram and explain INST mode of operation in defibrillator.  Draw and explain temperature controller circuit used in Hemodialysis	10 10
6.	Draw and explain the following circuit in pacemaker  (a) Rate generator  (b) Monostable multivibrator	20