

(3 Hours)

Total Marks: 80

- N.B. :** (1) Question number 1 is compulsory.
 (2) Attempt any three questions from remaining questions.
 (3) Figures to the right indicate full marks.
 (4) Assume suitable data wherever necessary and indicate the same.

- Q.1 Write a short note on following: [20]
 (a) Hybrid MICs versus Monolithic MICs.
 (b) Coupled Lines.
 (c) Dielectric Resonator Oscillator.
 (d) Noise correlation matrix.
- Q.2 (a) For a load impedance $Z_L = 60 - j80 \Omega$, design single-stub (short circuit) shunt tuning networks to match this load to a 50Ω line. Assuming that the load is matched at 2 GHz. [10]
 (b) Draw and explain in detail Single-Ended Diode Mixer. [10]
- Q.3 (a) What is phase noise in oscillators? Give a mathematical analysis of phase noise. [10]
 (b) How is Vector Network Analyzer used to measure periodic large signal waveform with all harmonics. [10]
- Q.4 Design an amplifier to have a gain of 11 dB at 4.0 GHz. Plot constant-gain circle for $G_S = 2$ and 3 dB, and $G_L = 0$ and 1 dB. Calculate and plot the input return loss and overall amplifier gain from 3 to 5 GHz. The transistor has the following scattering parameters ($Z_0 = 50 \Omega$): [20]

f (GHz)	S_{11}	S_{12}	S_{21}	S_{22}
3	$0.80 \angle -90^\circ$	0	$2.8 \angle 100^\circ$	$0.66 \angle -50^\circ$
4	$0.75 \angle -120^\circ$	0	$2.5 \angle 80^\circ$	$0.60 \angle -70^\circ$
5	$0.71 \angle -140^\circ$	0	$2.3 \angle 60^\circ$	$0.58 \angle -85^\circ$

- Q.5 (a) The s parameters for the HP HFET-102 FET at 2 GHz with a bias voltage $V_{gs}=0$ are given as follows ($Z_0=50 \Omega$) [10]

$$S_{11} = 0.894 \angle -60.6^\circ$$

$$S_{21} = 3.122 \angle 123.6^\circ$$

$$S_{12} = 0.020 \angle 62.4^\circ$$

$$S_{22} = 0.781 \angle -27.6^\circ$$

Determine the stability of this transistor by K- delta test and plot the stability circles on smith chart.

- (b) Explain nonlinear measurements of microwave circuits with reference to load and source pull. [10]
- Q.6 (a) Show that the reflection coefficient is larger than 1 for a load of negative resistance. Justify your answer using I2R relation. (10)
 (b) Write a short note on Field Surveys. [10]