 


QP Code : 5159

(3 Hours)

[ Total Marks : 80 ]

- N. B. :** (1) Question No. 1 is compulsory.  
 (2) Attempt any three out of the remaining four questions.  
 (3) Use suitable data, wherever necessary.

1. (a) Explain drawback of synchronous counter. 5  
 (b) Differentiate synchronous and asynchronous counter. 5  
 (c) Draw truth table and logical diagram of half adder. 5  
 (d) Explain Fan in, fan out, power dissipation and noise immunity with reference to digital ICs 5
  2. (a) Design MOD 12 asynchronous counter using T flip flop. 10  
 (b) Discuss Xilinx XC 9500 CPLD architecture. 10
  3. (a) Design MOD-60 counter using IC 74163. 10  
 (b) Analyze the sequential state machine shown in figure. Obtain state diagram for the same 10
- 
4. (a) Simplify following logic function and realize using NAND gates 10
    - (i)  $F_1 = \sum m(1, 2, 4, 7, 10, 11, 13) + d(9, 15)$
    - (ii)  $F_2 = \sum m(1, 2, 3, 5, 9, 11, 13, 15) + d(6)$
  - (b) Design a Mealy type sequence detector to detect a serial input sequence of 101. 10
  5. (a) Draw a circuit diagram of two input TTL NAND gate and explain its operation. 10  
 (b) Design 4 bit Johnson counter using J-K Flip Flop. Explain its operation using waveform. 10
  6. Write a short note on 20
    - (a) Fault Model.
    - (b) Multiplexers.
    - (c) Noise Margin.