

(3 hrs.)

Maximum Marks = 80

Q1. is compulsory.


Attempt any **three** question from **Q.2 to Q.6.**

Assume suitable data if necessary.

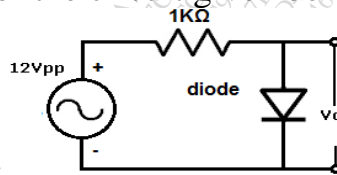Q.1 Write any **four**.

20

- Explain working of pn junction diode and its V-I characteristics.
- What is early effect in BJT?
- Explain Zener diode as a voltage regulator.
- Write short note on Tunnel diode.
- Draw output waveform for the circuit given below




Q.2

- Explain construction and working of solar cell and LED.
- Find Q point if $\beta=120$. Also draw dc load line.

10

10

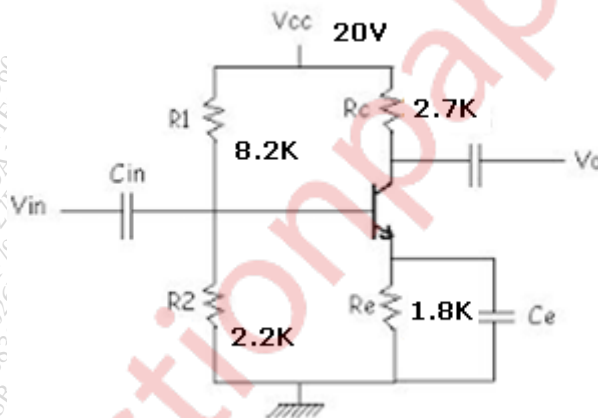


Q.3

- Explain with construction working and characteristic operation of n-channel D-MOSFET. Also compare it with E-MOSFET.
- Calculate dc load voltage, an ac ripple in output and ripple factor.


10

10

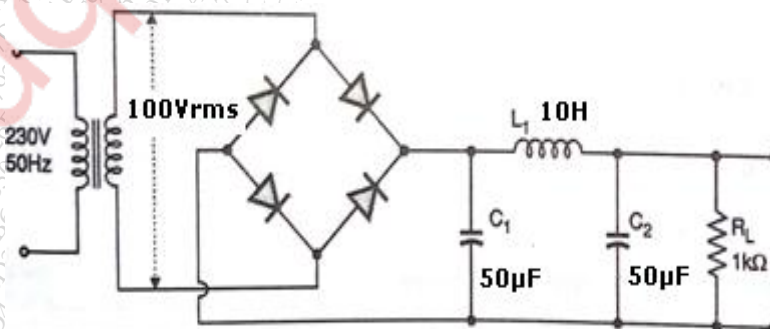

Q.4

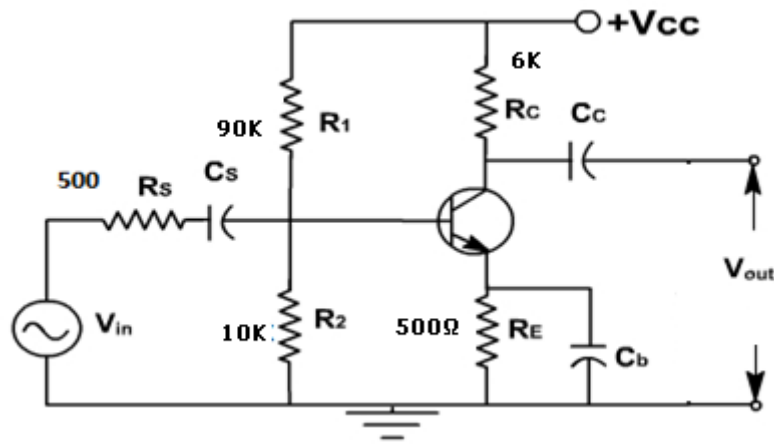a) Find Z_i , Z_o , A_v and A_{v_s} using Hybrid- π model ($V_{BE}=0.7V$, $\beta=100$) **10**



b) Explain working of Full wave rectifier with LC filter. Also draw output waveforms and derive expression for ripple factor. **10**


Q.5

a) Design single stage CE amplifier for $A_v \geq 180$, $h_{fe} = 220$, $V_{CC} = 18V$, $h_{ie} = 2.7K$, $S_{ICO} \leq 10$, $f_L \leq 20Hz$, $V_{CE\ sat} = 1V$, $V_{BE} = 0.7V$, $h_{re} = h_{oe} = 0$ **15**

b) Explain positive and negative clampers. **05**

Q.6

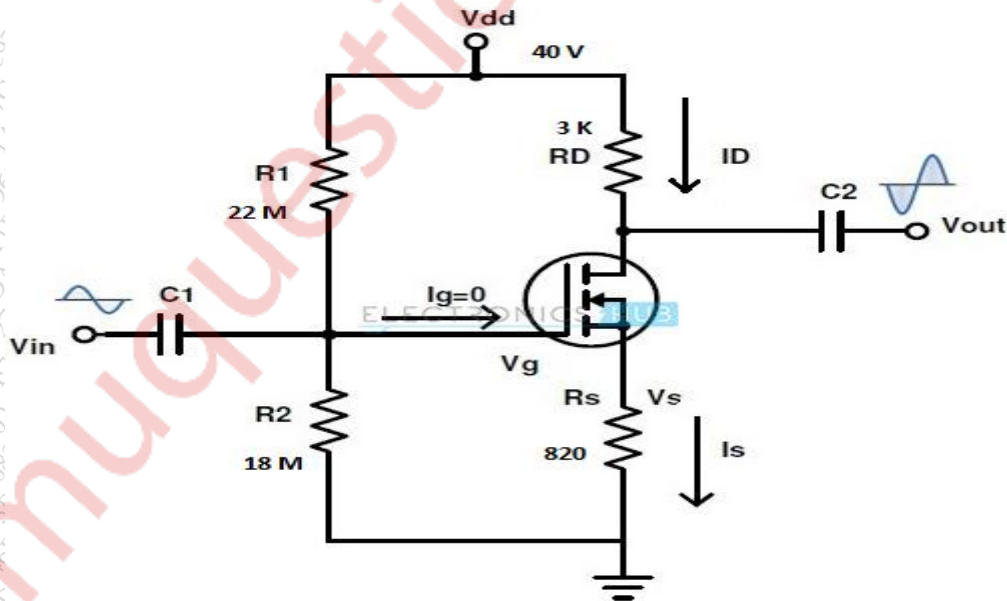a) Find I_{DQ} , V_{DSQ} and V_{GSQ} if $V_{GS\ TH} = 5V$, $I_{D\ ON} = 3mA$ and $V_{GS\ ON} = 10V$ **10**



b) Compare CE, CB and CC configuration of BJT amplifier. **10**

DBEC DATA SHEET

Transistor type	P _{max} Watts @ 25°C	I _{max} Amps @ 25°C	V _{CE} max. Vdc	V _{CE} max. Vdc	V _{CE} max. Vdc	V _{CE} max. Vdc	V _{CE} max. Vdc	V _{CE} max. Vdc	V _{CE} max. Vdc	T _{max} °C	D.C. current gain			Small Signal h _{fe}			V _{CE} max.	θ _{JA} °C/W	Derate above 25°C
											min.	typ.	max.	min.	typ.	max.			
2N 3053	115.5	15.0	1-1	100	60	70	90	1	200	20	50	70	15	50	120	1.8	1.5	0.7	
ECN 055	30.0	3.0	1.0	60	50	55	60	5	200	25	50	100	25	75	125	1.5	3.5	0.4	
ECN 149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	110	33	60	115	1.2	4.0	0.3	
ECN 100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	280	0.9	35	0.05	
BC147A	0.25	0.1	0.25	90	45	—	—	6	125	115	180	220	125	250	260	0.9	—	—	
2N 2950(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	65	—	45	—	—	—	—	
BC147B	0.25	0.1	0.25	50	45	—	—	—	125	200	450	240	240	330	500	0.9	—	—	

—V _{GS} volts	I _D max. mA	I _D typ. mA	I _D min. mA
0.0	0.2	0.4	0.6
1.0	9.0	8.3	7.6
2.0	6.0	5.4	4.6
3.0	3.0	2.2	1.6
4.0	—	—	—

Transistor type	N _{FE}	N _{DE}	N _{AE}	g _m
BC 147A	2.7 K Ω	180 Ω	1.5 × 10 ⁴	0.4°C/mV
2N 325 (PNP)	1.4 K Ω	250 Ω	3.2 × 10 ⁴	—
BC 147B	4.5 K Ω	300 Ω	2 × 10 ⁴	0.4°C/mV
ECN 100	50 Ω	—	—	—
ECN 149	15 Ω	—	—	—
ECN 055	12 Ω	—	—	—
2N 2055	6 Ω	—	—	—

Type	V _{GS} max. Volts	V _{DS} max. Volts	V _{DS} max. Volts	I _D max. @25°C	T _{max}	I _{DS}	g _m	-V _{GS} Volts	r _{ds}	Derate above 25°C	θ _{JA}
2N2932	50	50	50	300 mW	175°C	2 mA	3000 μΩ	6	50 KΩ	2 mW/°C	0.59°C/mW
BRF 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μΩ	2.5	50 KΩ	—	0.59°C/mW