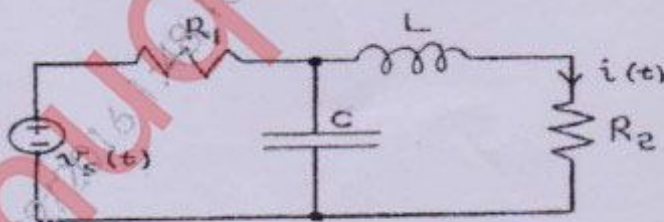


- N. B. :** (1) Question No. 1 is **compulsory**.  
 (2) Attempt any **three** questions from remaining.  
 (3) Assume suitable data if required. Justify your assumptions.

1. (a) What is back emf? Explain significance of back emf. 5
- (b) Voltage across capacitor  $C$  is exponentially increasing with time constant  $100\text{m/sec}$ . If supply voltage to series RC circuit is  $10\text{V}$ , determine  $V_c(t)$  at- 5  
 (i)  $t=50\text{ ms}$  (ii)  $t=100\text{ms}$  (iii)  $t=500\text{ms}$   
 Also find  $C$  if  $R=100\text{K}\Omega$
- (c) Explain the difference between BJT and FET. 5
- (d) Derive equation for transient current  $I_L$  with initial conditions in case of series RL circuit excited by DC supply (V) 5
- (e) What do you mean by synchronous speed of a 3-phase induction motor? 5
  
2. (a) Draw the structure of an N channel JFET & explain its principle of operation also draw its drain and transfer characteristics with the help of suitable circuit. 10
- (b) A 4 pole De shunt generator with Lap connected armature supplies a load of  $100\text{A}$  at  $200\text{V}$ . the armature resistance is  $0.1\Omega$  & Shunt field resistance is  $80\Omega$ . 10  
 Find (i) Total armature current  
 (ii) Current per armature path  
 (iii) emf generated  
 Assume a brush drop of  $2\text{V}$ .
  
3. (a) In the circuit shown the input voltage is  $V_s(t)$  and the output signal is the current  $i(t)$  10



Determine differential equation relating  $V(t)$  and  $i(t)$

- (b) Explain construction and working of 3 phase induction motor. 10

4. (a) Determine amplitude and phase of a network function given below at  $j4$ . 10

$$\frac{s^3 + 4s^2 + 3s}{s^2 + 6s + 8)(s^2 + 10s + 29)}$$

- (b) Explain Different methods of Starting Single phase induction Motor. 10
5. (a) Explain working of BJT CE amplifier with neat diagram and its characteristics. 10
- (b) What is meant by brushless DC motor? Explain unipolar BLDC with a neat diagram. 10
6. Write Short note on any **three** 20
- a) Transistor Region of operation as an amplifier and switch
  - b) Time domain analysis using Laplace transform
  - c) Speed control of DC series motor
  - d) Pinch-off voltage in a J FET