


QP Code : 726600

(3 Hours)

[Total Marks : 80

- N. B. :** (1) Question No. 1 is **compulsory**.
 (2) Solve any **three** questions from remaining **five** questions.
 (3) Draw neat diagrams and assume suitable data wherever necessary. Justify your assumptions.

 1. (a) Convert a SR flip flop to JK flip flop. 5
- (b) Define the term propagation delay and specify its value for a TTL gate and CMOS gate. 5
- (c) Explain the glitch problem of a ripple counter with a waveform. 5
- (d) Compare a PAL and PLA device. 5
2. (a) Design a MOD 10 synchronous up counter using T flip flops. 10
- (b) Write VHDL code for a 1:8 Demultiplexer. 10
3. (a) Design 8-bit BCD adder using 7483 and explain the operation with an example. 10
- (b) Analyze the clocked synchronous machine shown below and write excitation equations, excitation table and state table. Draw the state diagram. Assume $x = 0$ and 1. 10



4. (a) What is Multiplexer Tree? 10
 Implement the following using 8:1 MUX using only NAND gates
 $P(A,B,C,D) = \sum m(0, 1, 2, 4, 5, 7, 10, 13, 15) + d(3, 11)$
- (b) Design a circuit to implement the following functions with optimum utilization of PLA having 3 inputs, 3 product terms and 2 outputs. 10
 $F1(A,B,C) = \sum m(4, 5, 7)$
 $F2(A,B,C) = \sum m(3, 5, 7)$

[TURN OVER

5. (a) Implement a sequence detector using Mealy machine to detect a sequence ... 11 0 1... using D flip flop and logic gates. 10
- (b) Find reduced SOP form and implement the same using only NAND gates. 10
- (i) $f(A,B,C,D) = \sum m(0,6,7,9,12,15) + \sum d(1,4,11)$
- (ii) $f(W,X,Y,Z) = \pi M(0,1,2,8,9,10,12,13,15)$
6. Write short notes on (any three) 20
- (a) CMOS Inverter
- (b) Fault Model
- (c) Frequency division in asynchronous counters
- (d) Shift Registers