


Q.P. Code : 5606

(3 Hours)

[Total Marks : 80]

- N.B. :** (1) Question No.1 is compulsory.
 (2) Attempt any three questions from remaining five questions.
 (3) Assume suitable data if required.

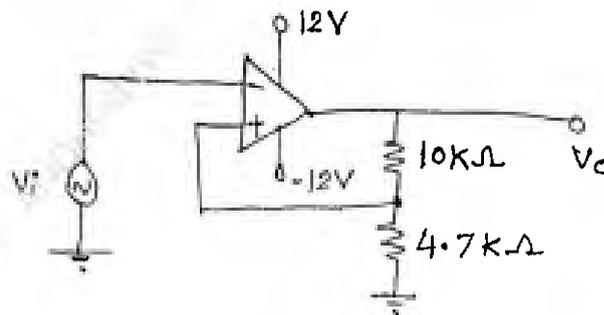1. Solve any four from the following :
- What do you mean by Input Bias current of an op-amp, How it can be measured practically. What should be its value ideally. 5
 - How to avoid false triggering in electronics, draw suitable diagram and explain with neat waveforms. 5
 - Assume that you have to use ADC with microcontroller, before using it which performance parameters of ADC you need to study. 5
 - What are the features of Regulator IC LM 337, Design voltage regulator using LM 337 to give output voltage of -7 volts. 5
 - Explain Inverting mode current amplifier circuit using op-amp. 5
 - What are the features of Multiplier IC 534, explain one of its application. 5
2. (a) State the important ideal characteristics of an op-amp, compare it with the values of IC 741 op-amp. 10
 (b) Design a wide band reject filter having $f_H = 400$ Hz and $f_L = 2$ kHz with a pass band gain of 2, Also draw frequency response of it. 10
3. (a) For the circuit shown below. Calculate the trigger points if supply voltage $V = \pm 12V$, Plot the output voltage V_o if V_i is a 100 Hz triangular wave of magnitude $\pm 10V$. 10



- (b) What are the features of Instrumentation amplifier, Draw neat diagram of three op-amp instrumentation amplifier and hence derive equation of output voltage. 10

TURN OVER

MD-Con. 8235-15.

4. (a) Explain the working of R/2R ladder D/A converter. 10
(b) What are the features of LM 380 Power Amplifier, explain any two applications of it. 10
5. (a) Design voltage Regulator to give $V_o = 9V$ at 600 mA using IC 723. 10
(b) Explain how IC 555 can be used as PWM. 5
(c) Explain Precision Half wave rectifier. 5
6. (a) Explain the Astable mutivibrator using op-amp. 10
(b) Explain current voltage converter using op-amp and hence state applications of it. 5
(c) What are the features of IC 78XX. Design voltage regulator using IC 78XX for $V_o = 20V$. (Adjustable Regulator). 5
-